

# Datapath Components-Part II

Jia Chen  
jiac@ucr.edu

# Datapath components

Multiplexer

Decoder

Adder

Subtractor

Register

Encoder

Shifter

Counter

Multiplier

Divider

Comparator

...

# Registers

# Registers


- **Register**: logic unit used to **store multiple bits** in a sequential logic circuit
  - A basic register can be built simply by using multiple **D-FFs**
  - Two common types of registers:

**Parallel load register**

**Shift register**
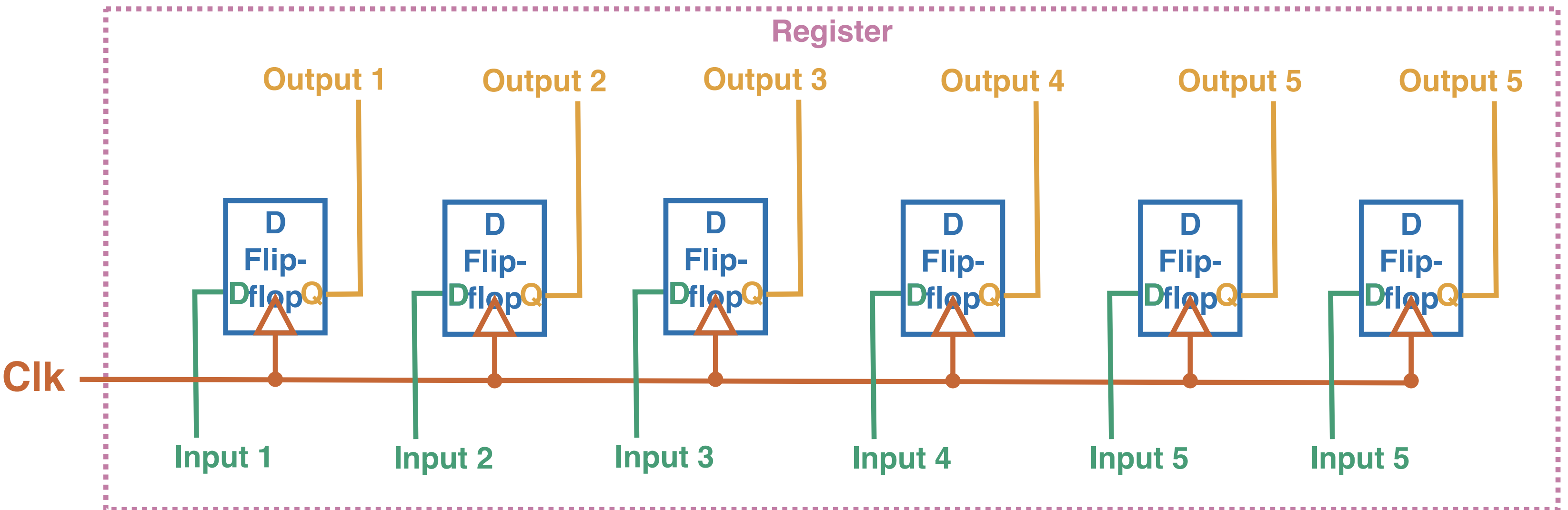
# Parallel load register


- **Parallel load register:** individual bit values in the register are loaded simultaneously.




# Shift register

- **Shift register:** a register that provides the ability to shift its contents
  - The D-FFs share a single clock signal, which causes the data stored in the system to shift from one location to the next

For example,

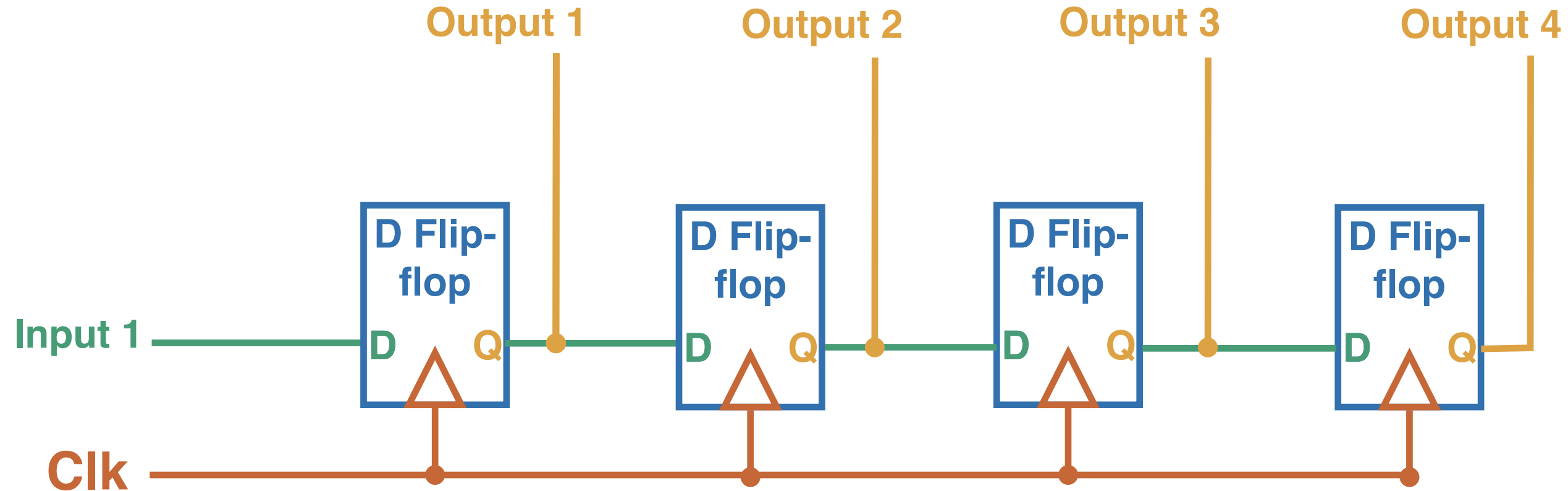


# What will we output 4 cycles later?

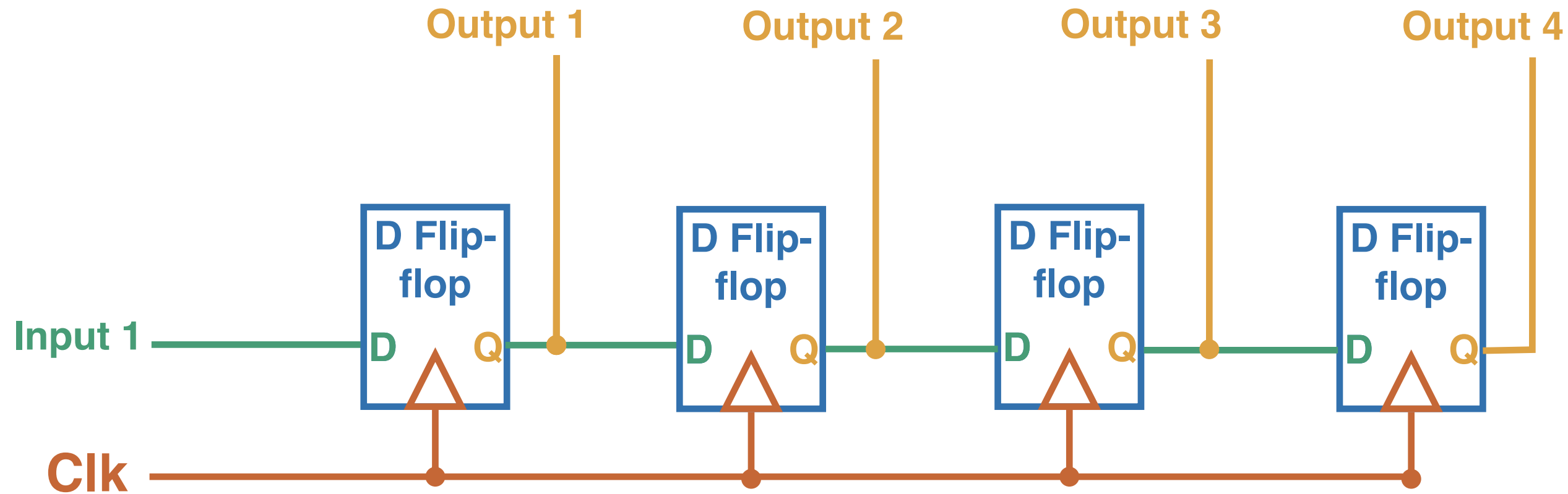

- For the above D-FF organization, what are we expecting to see in (O1,O2,O3,O4) in the beginning of the 5th cycle after receiving (1,0,1,1)?


# 1 cycle later?

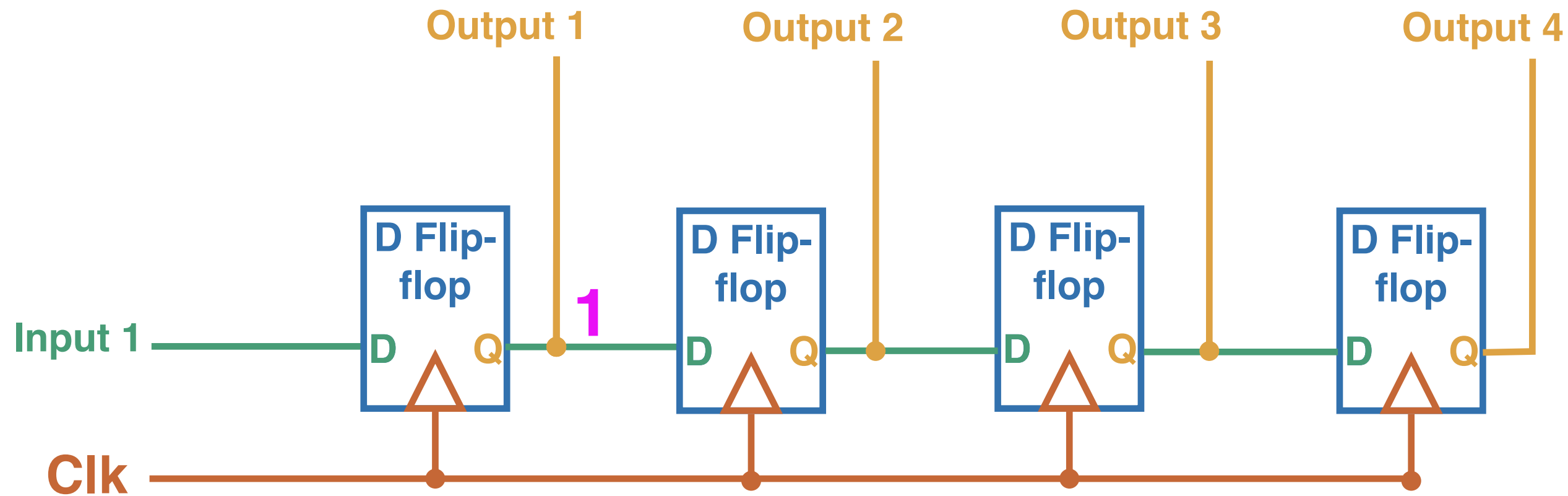

- For the above D-FF organization, what are we expecting to see in (O1,O2,O3,O4) in the beginning of the 5th cycle after receiving (1,0,1,1)?




# 2 cycles later?

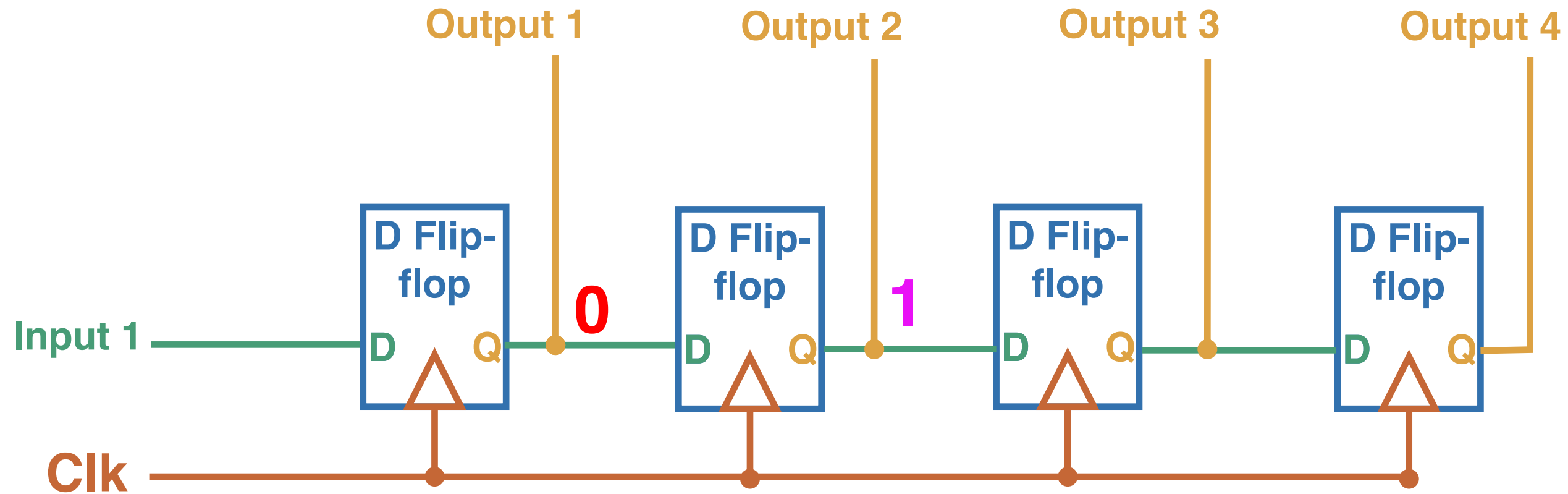


- For the above D-FF organization, what are we expecting to see in (O1,O2,O3,O4) in the beginning of the 5th cycle after receiving (**1**,**0**,1,1)?

# 3 cycles later?

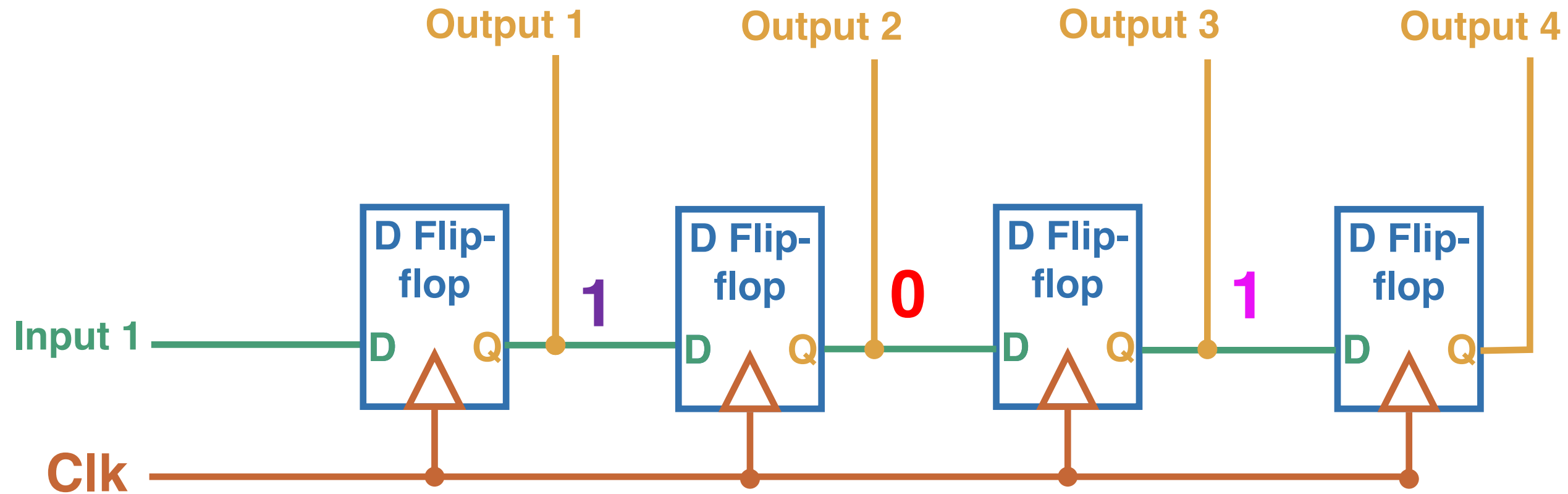


- For the above D-FF organization, what are we expecting to see in (O1,O2,O3,O4) in the beginning of the 5th cycle after receiving (1,0,1,1)?
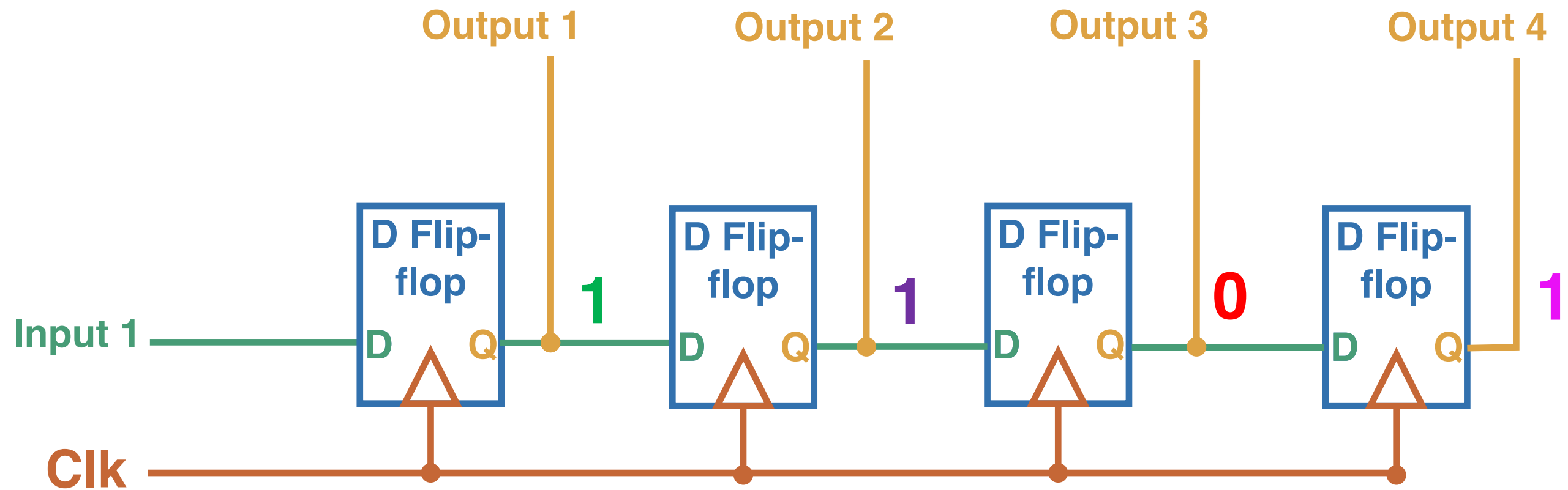
# 4 cycles later (aka the beginning of the 5<sup>th</sup> cycle)?



- For the above D-FF organization, what are we expecting to see in (O1,O2,O3,O4) in the beginning of the 5th cycle after receiving (1,0,1,1)?

# What will we output 4 cycles later?

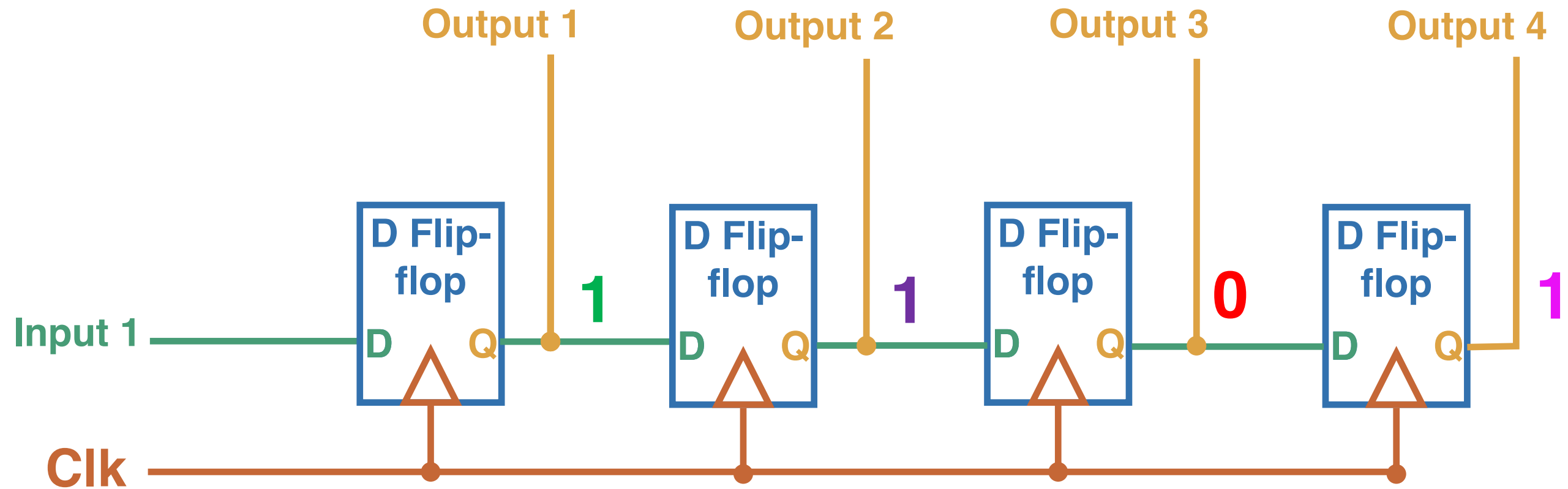

- For the above D-FF organization, what are we expecting to see in (O1,O2,O3,O4) in the beginning of the 5th cycle after receiving (1,0,1,1)?

(1,1,0,1)

# Let's play with the shift register more...

- For the extended shift register, what sequence of input will circuit output “1” after 4 clock cycles?


A. (1, 1, 1, 1)

B. (0, 1, 0, 1)

C. (1, 0, 1, 0)

D. (0, 1, 1, 0)

E. (1, 0, 0, 1)

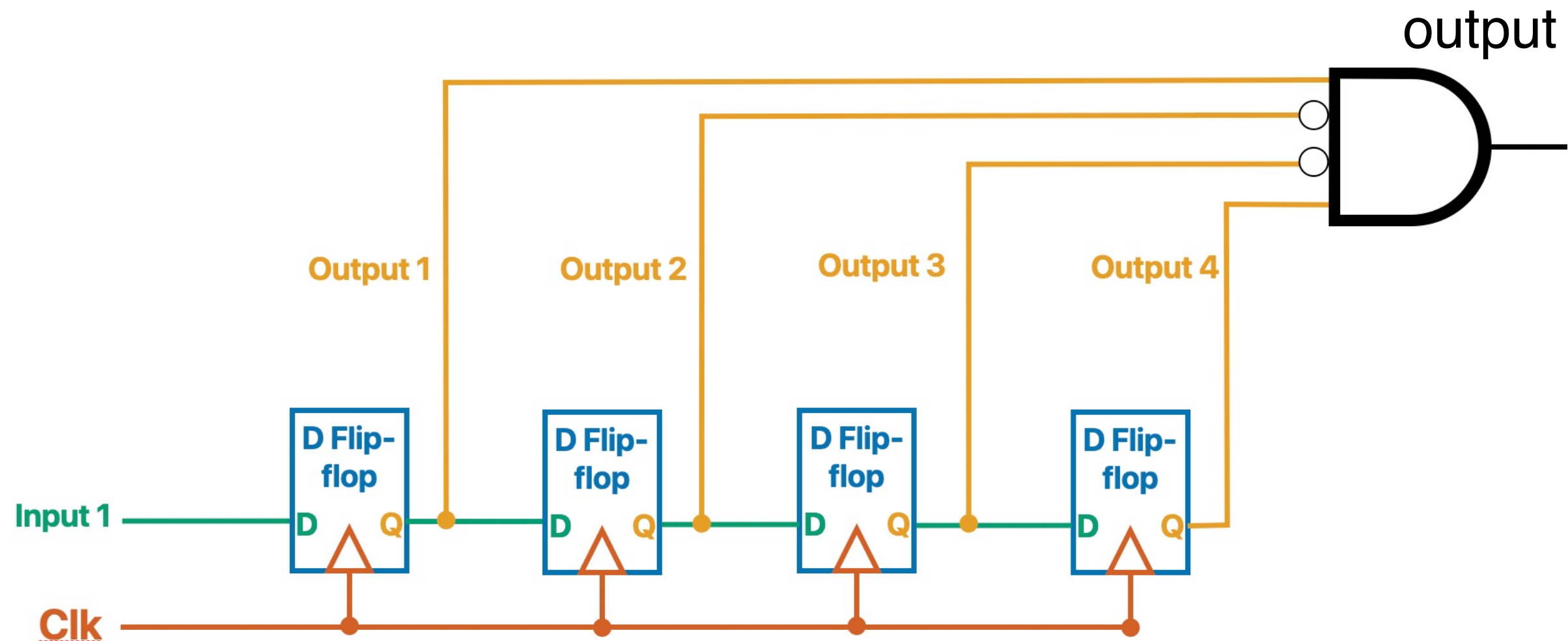

# Let's play with the shift register more...

- For the extended shift register, what sequence of input will the circuit output "1" after 4 clock cycles?


A. (1, 1, 1, 1)

B. (0, 1, 0, 1)

C. (1, 0, 1, 0)

D. (0, 1, 1, 0)


E. (1, 0, 0, 1)

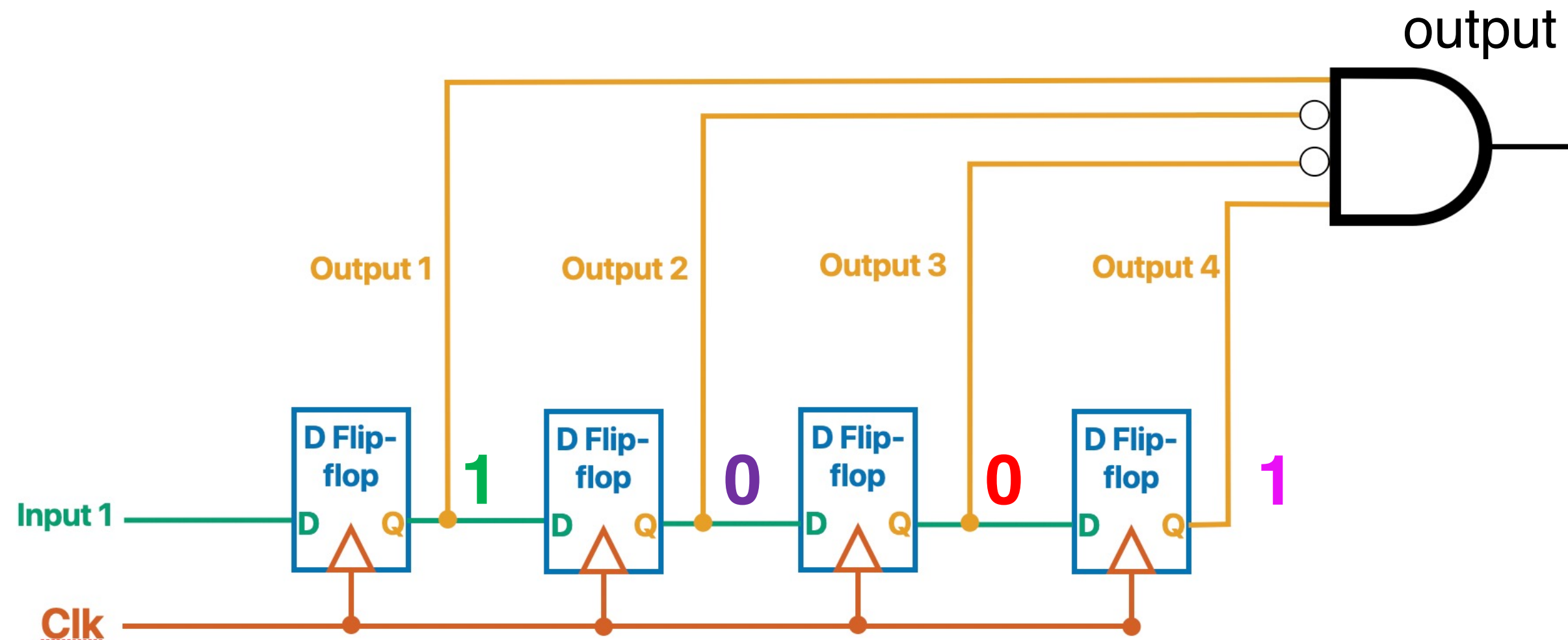
 
# 4-bit up-counter


Expectation:

Outputs  $Q_3Q_2Q_1Q_0$  count in the sequence 0, 1, 2, . . . , 14, 15, 0, 1, and so on



Timing diagram

# 4-bit up-counter

 

clock cycle	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1

Q<sub>0</sub> always changes


Q<sub>1</sub> changes only when Q<sub>0</sub> = 1

Q<sub>2</sub> changes only when Q<sub>1</sub> = Q<sub>0</sub> = 1

Q<sub>3</sub> changes only when Q<sub>2</sub> = Q<sub>1</sub> = Q<sub>0</sub> = 1



# Up-counter

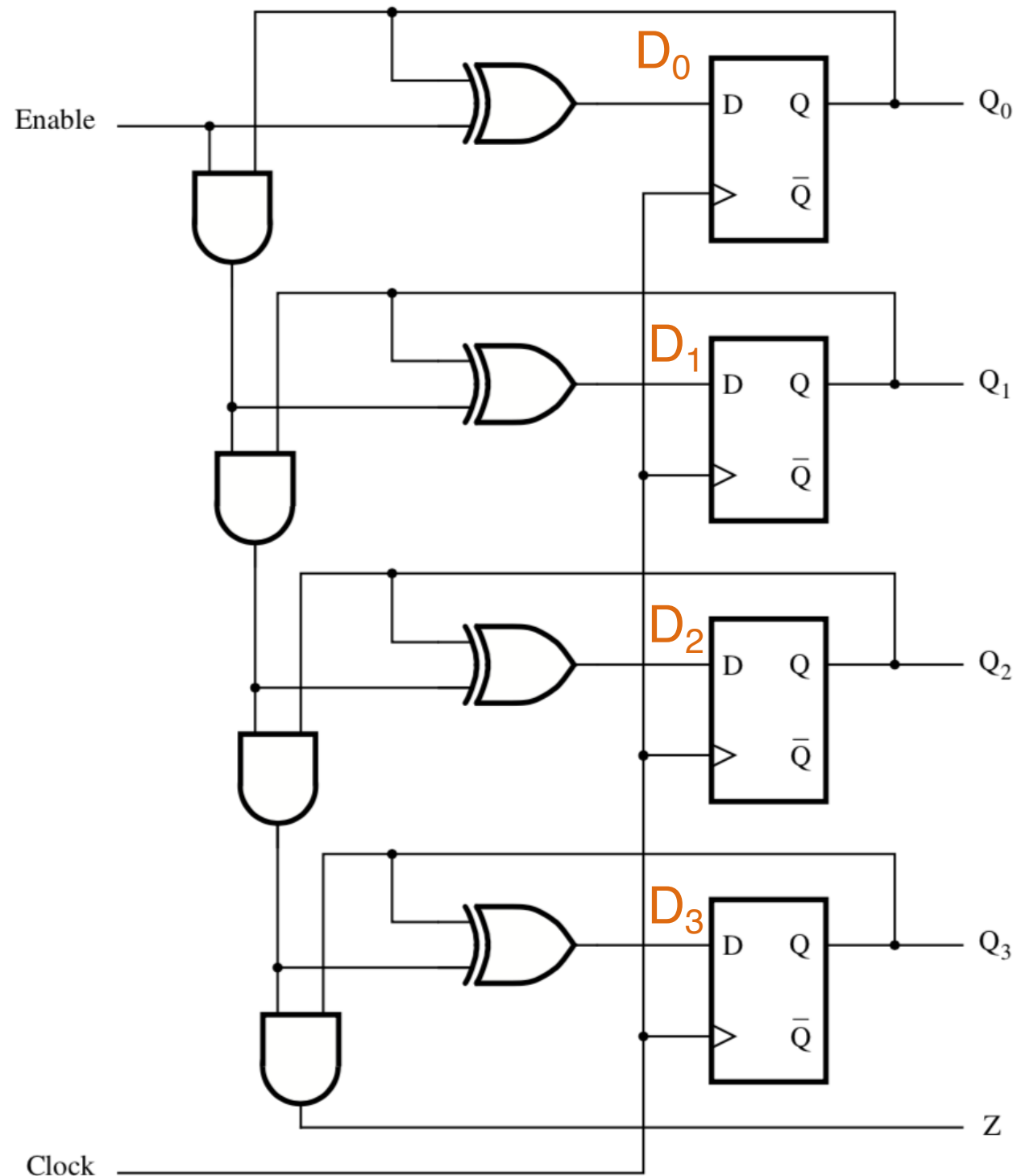

Counter counts the clock pulses only if *Enable* = 1.

$$D_0 = Q_0 \oplus Enable \longrightarrow Q_0(t+1) = \overline{Q_0(t)} \text{ if } Enable = 1$$

$$D_1 = Q_1 \oplus Q_0 \cdot Enable = Q_1 \oplus (Q_0 \cdot Enable)$$

$$D_2 = Q_2 \oplus Q_1 \cdot Q_0 \cdot Enable = Q_2 \oplus (Q_1 \cdot Q_0 \cdot Enable)$$

$$D_3 = Q_3 \oplus Q_2 \cdot Q_1 \cdot Q_0 \cdot Enable = Q_3 \oplus (Q_2 \cdot Q_1 \cdot Q_0 \cdot Enable)$$

$Q_0$  always changes

$Q_1$  changes only when  $Q_0 = 1$

$Q_2$  changes only when  $Q_1 = Q_0 = 1$

$Q_3$  changes only when  $Q_2 = Q_1 = Q_0 = 1$


**Z:**

1) Status indicator, all 1s

2) Makes it easy for concatenating

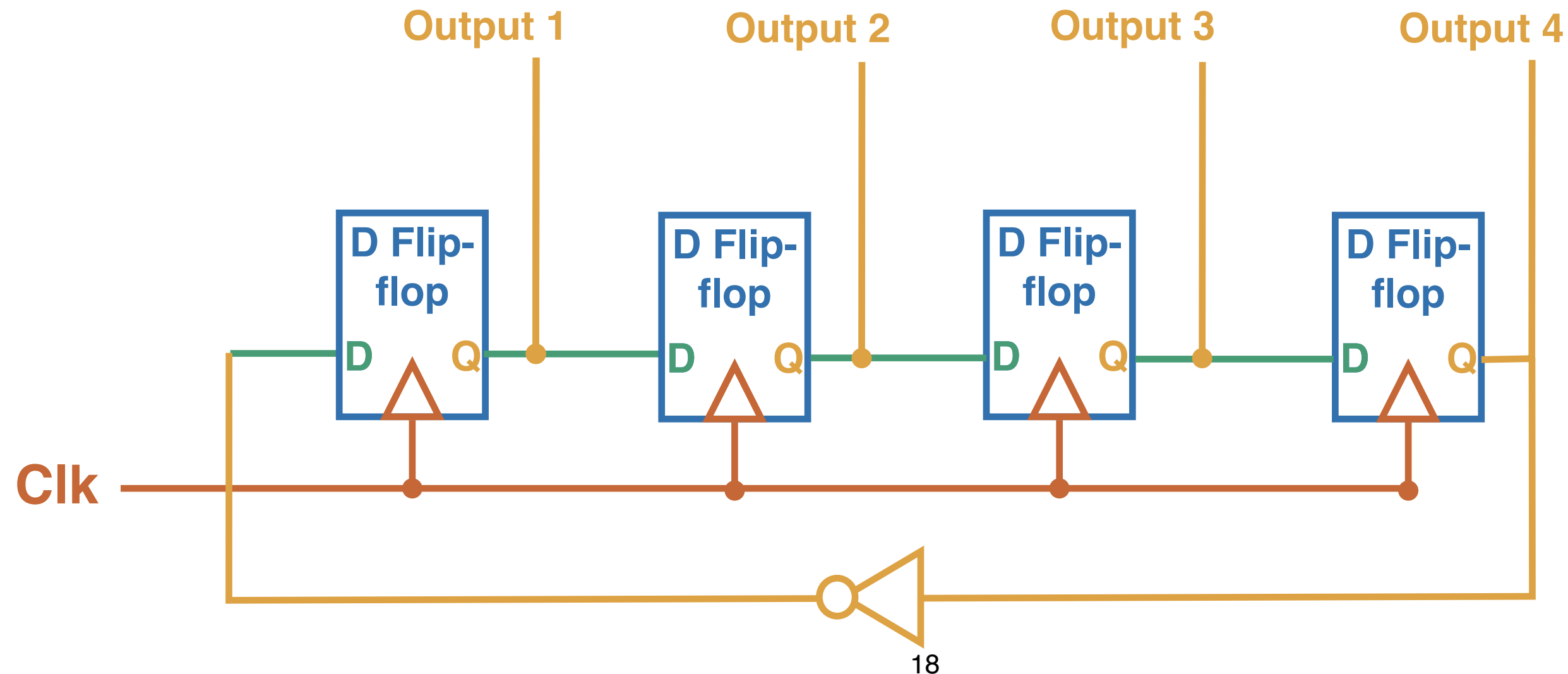
# Counters

- Sequences through a fixed set of patterns
- Note: definition is general
- For example, the one in the figure is a type of counter called Linear Feedback Shift Register (LFSR)



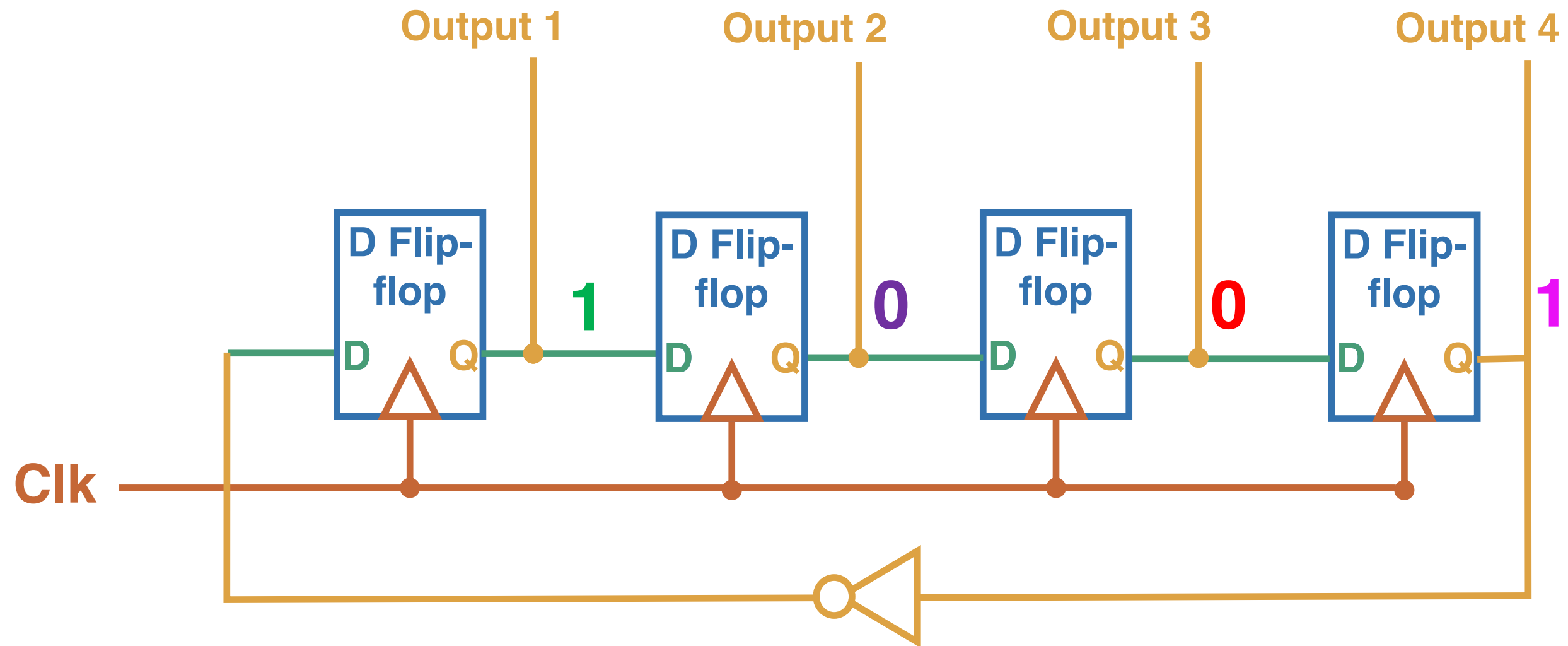
# Counters

- Assume that initially,  $O1 = 1$ ,  $O2 = 0$ ,  $O3 = 0$ ,  $O4 = 1$



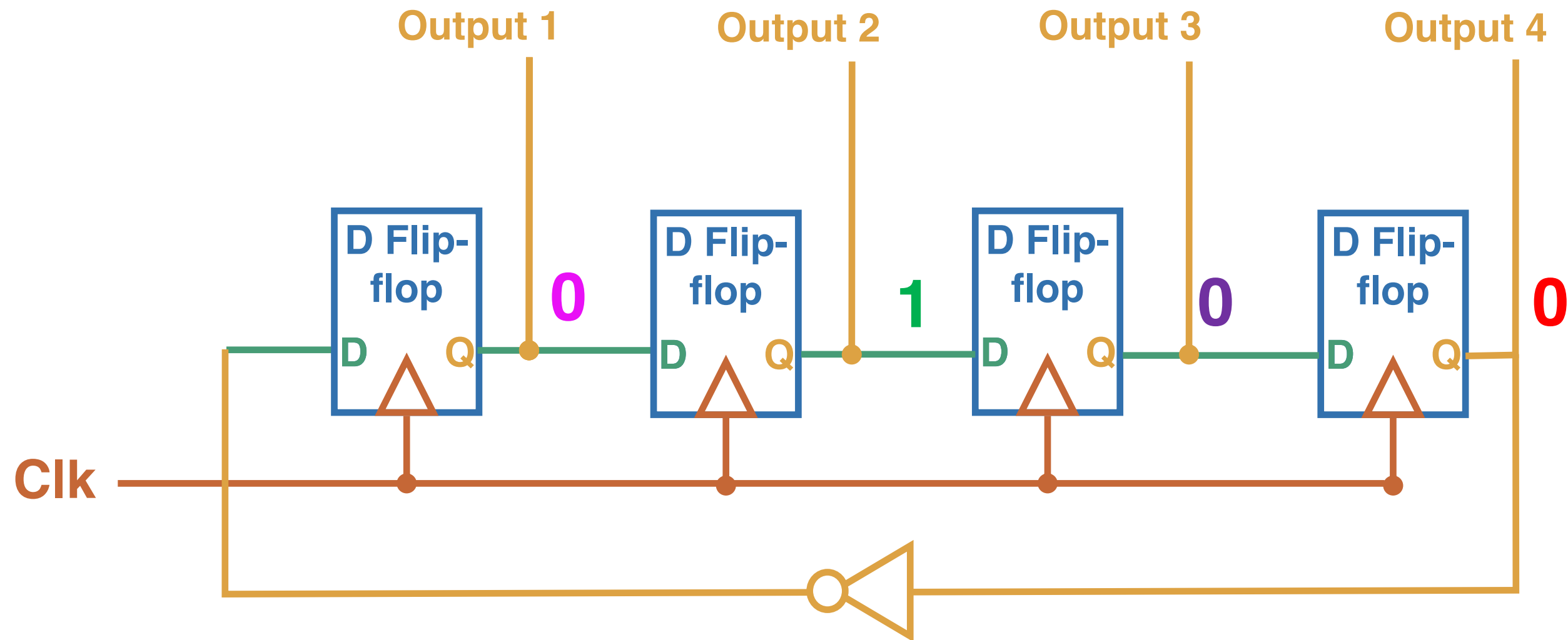
# After one clock cycle

- Assume that initially, O1 = 1, O2 = 0, O3 = 0, O4 = 1



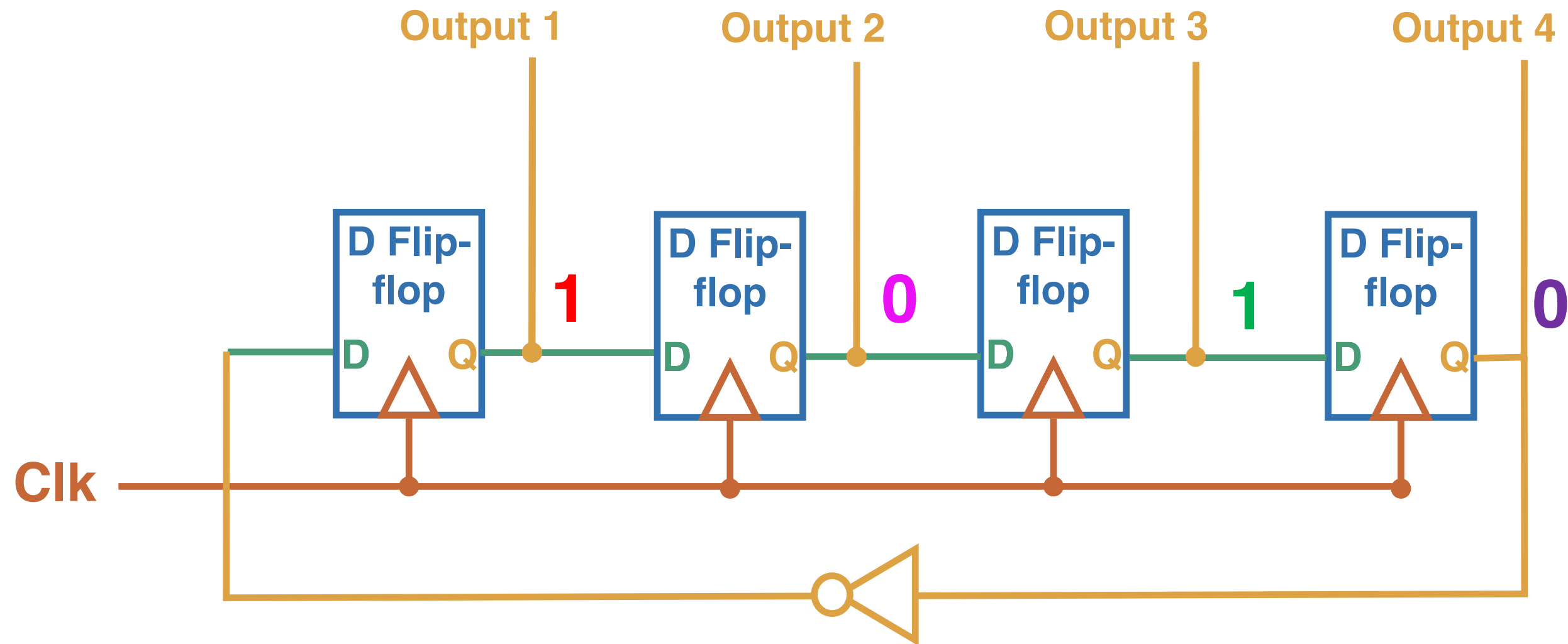
# After two clock cycles

- Assume that initially, O1 = 1, O2 = 0, O3 = 0, O4 = 1



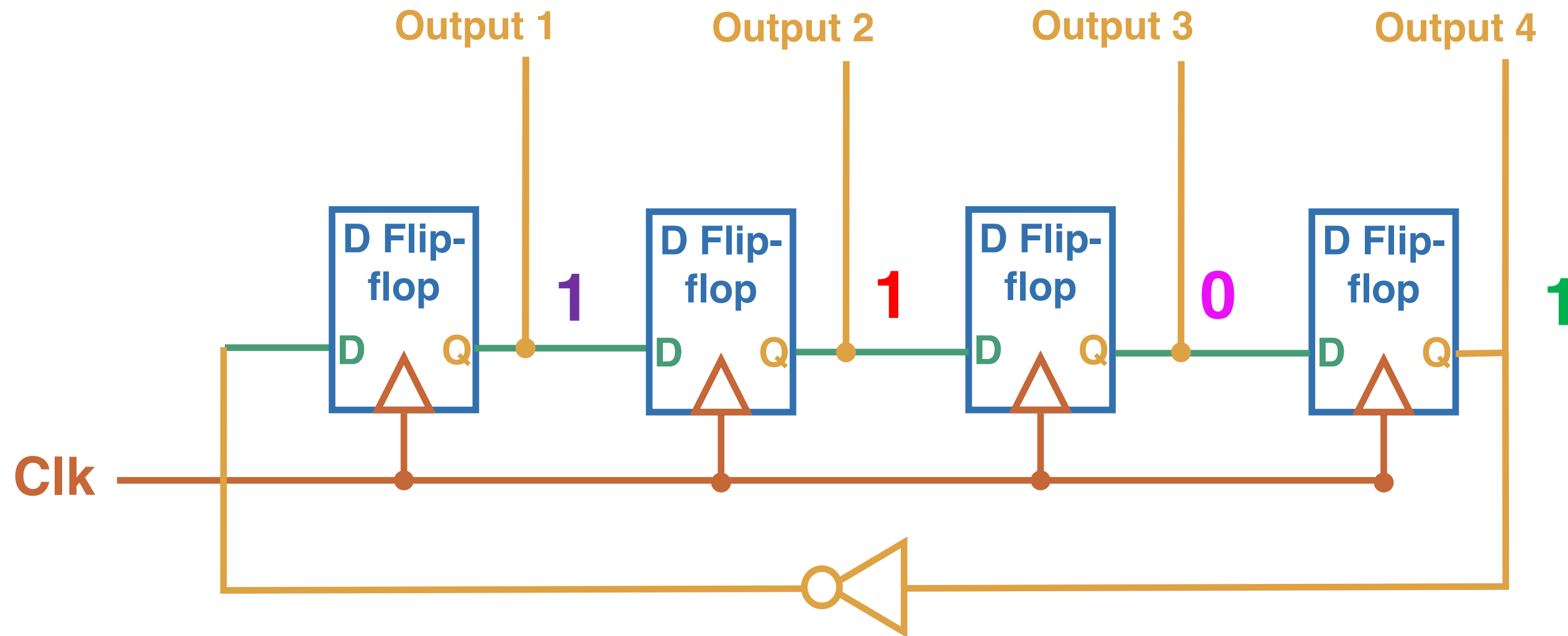
# After three clock cycles

- Assume that initially, O1 = 1, O2 = 0, O3 = 0, O4 = 1



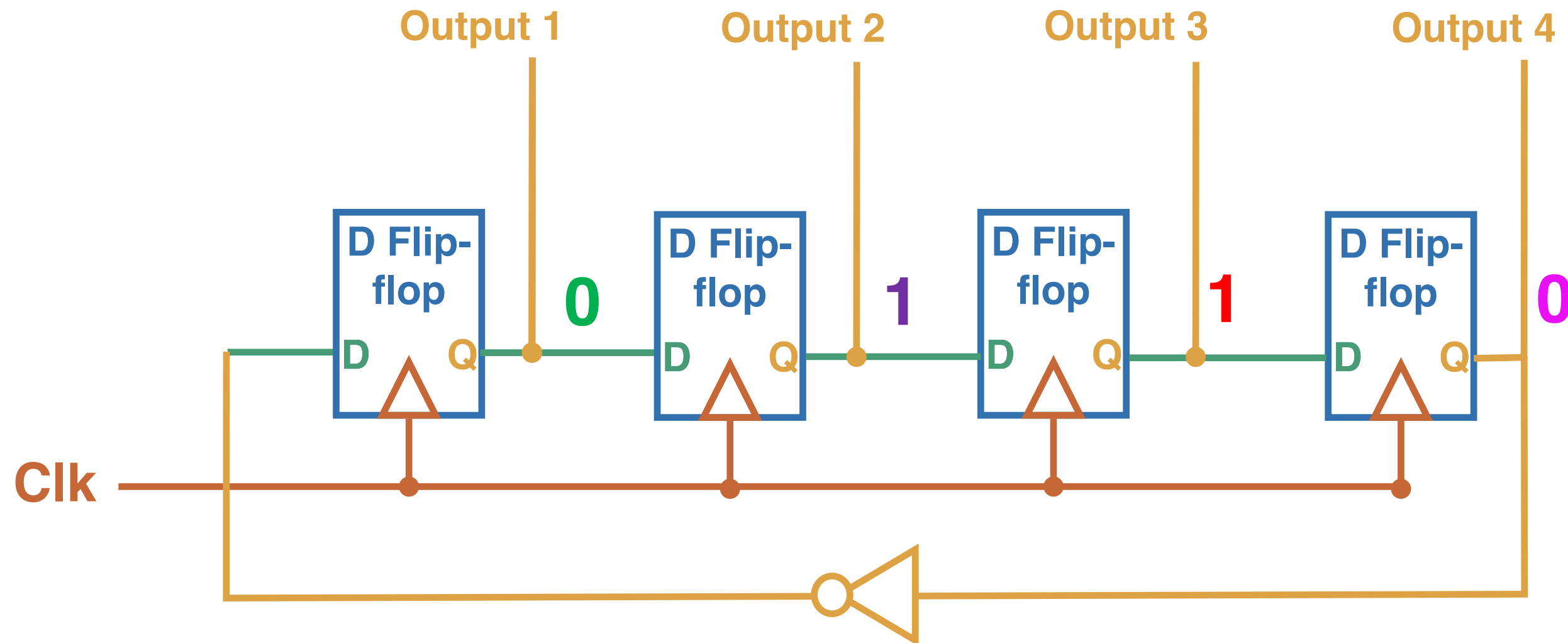
# After four clock cycles

- Assume that initially, O1 = 1, O2 = 0, O3 = 0, O4 = 1


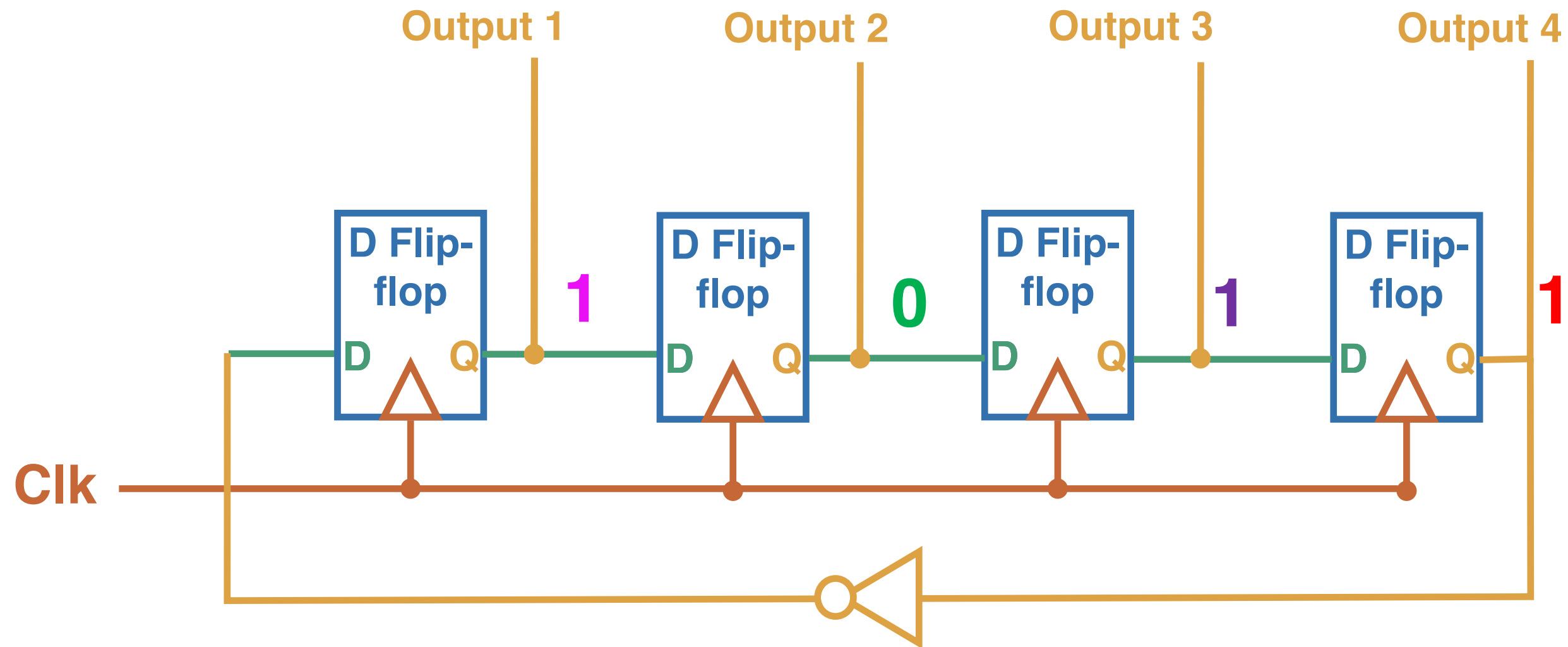
# After five clock cycles


- Assume that initially, O1 = 1, O2 = 0, O3 = 0, O4 = 1





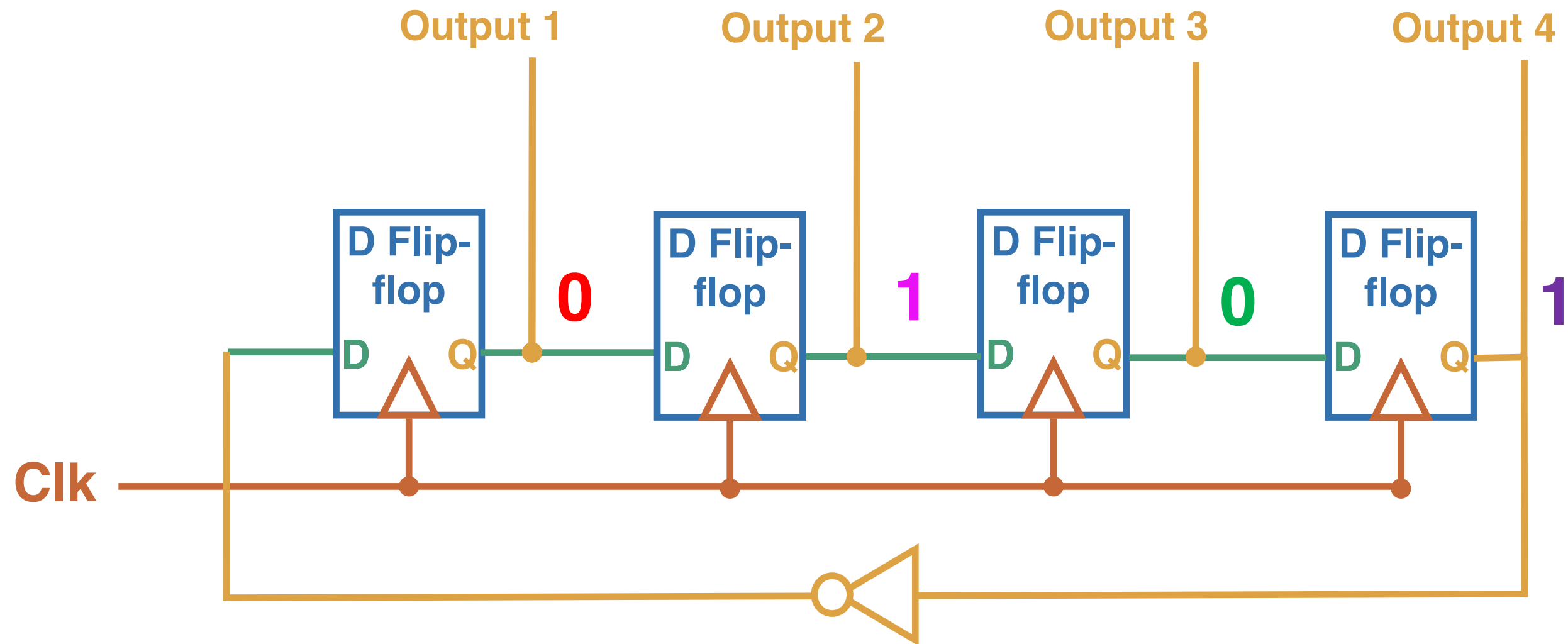
# After six clock cycles

- Assume that initially,  $O1 = 1$ ,  $O2 = 0$ ,  $O3 = 0$ ,  $O4 = 1$


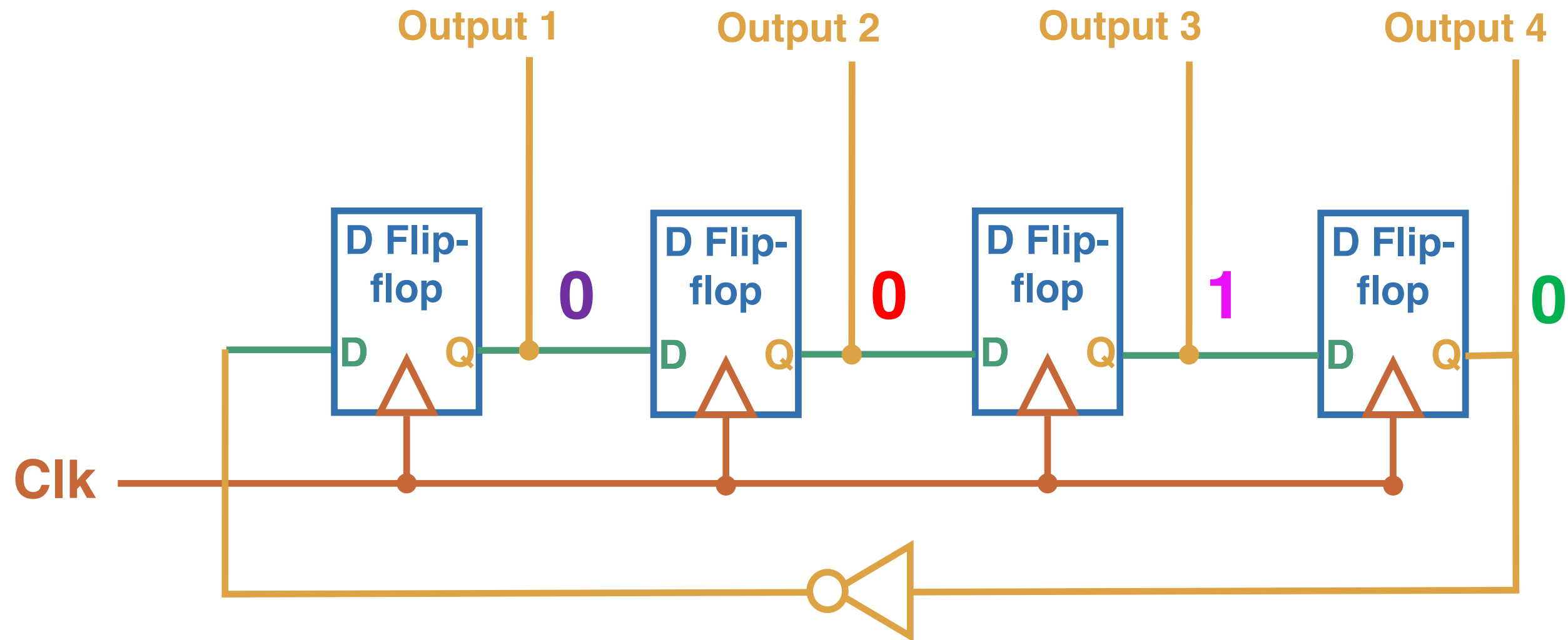
# After seven clock cycles


- Assume that initially, O1 = 1, O2 = 0, O3 = 0, O4 = 1



# After eight clock cycles

- Assume that initially,  $O1 = 1$ ,  $O2 = 0$ ,  $O3 = 0$ ,  $O4 = 1$

Back to the  
initial status!!

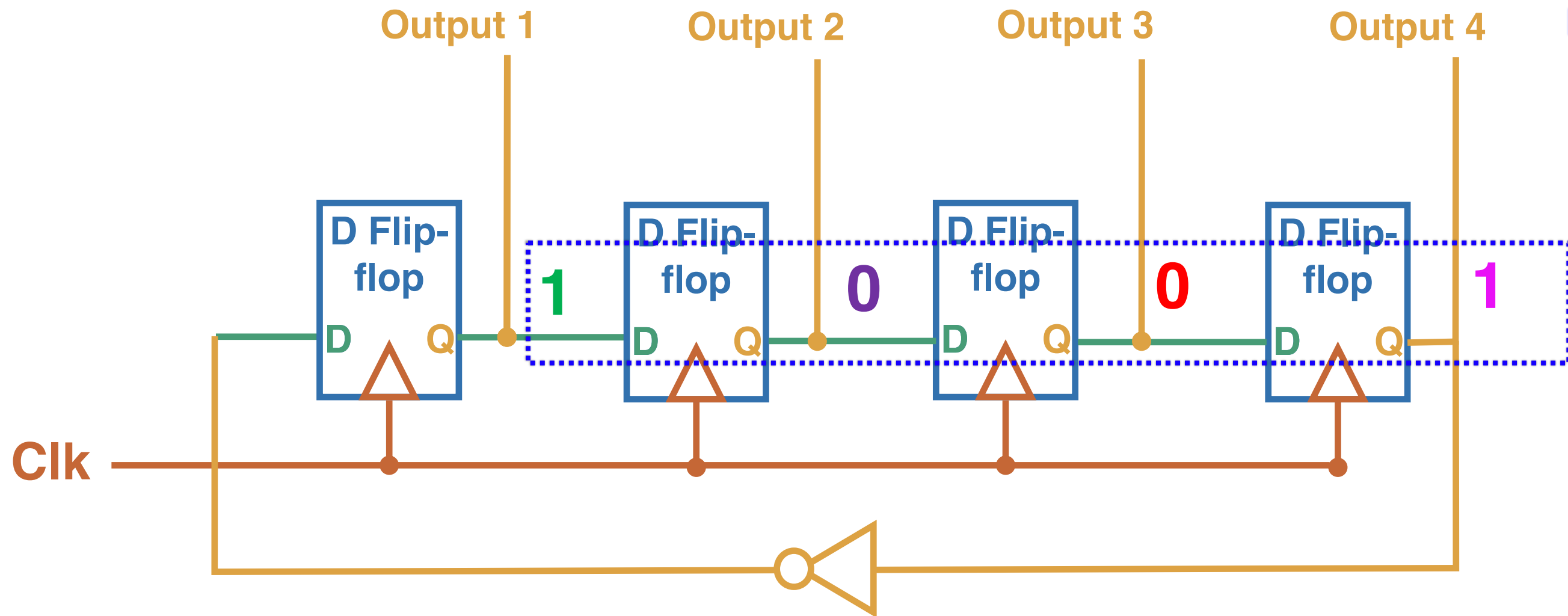


# Shifters

# Shifters

- **Logical shifter**: shifts value to left or right and fills empty spaces with 0's
  - $11001 \ggg 2 = 00110$  (right)
  - $11001 \lll 2 = 00100$  (left)
- **Arithmetic shifter**: same as logical shifter, but on right shift, fills empty spaces with the old most significant bit
  - Ex:  $11001 \ggg 2 = 11110$  (right)
  - Ex:  $11001 \lll 2 = 00100$  (left)
- **Rotator**: rotates bits in a circle, such that bits shifted off one end are shifted into the other end
  - Ex:  $11001 \text{ ROR } 2 = 01110$  (right)
  - Ex:  $11001 \text{ ROL } 2 = 00111$  (left)

# Shift “Right”

 

Based on the value of the selection input (shamt = shift amount)

If S=11, shift right by 3 bits


Example:  
if S = 11  
then  
Y<sub>3</sub> = 0  
Y<sub>2</sub> = 0  
Y<sub>1</sub> = 0  
Y<sub>0</sub> = A<sub>3</sub>

Example:  
if S = 10  
then  
Y<sub>3</sub> = 0  
Y<sub>2</sub> = 0  
Y<sub>1</sub> = A<sub>3</sub>  
Y<sub>0</sub> = A<sub>2</sub>

The “chain” of multiplexers determines how many bits to shift

A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
0	0	0	A <sub>3</sub>
↑	↑	↑	↑
Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>

# Shift "left"

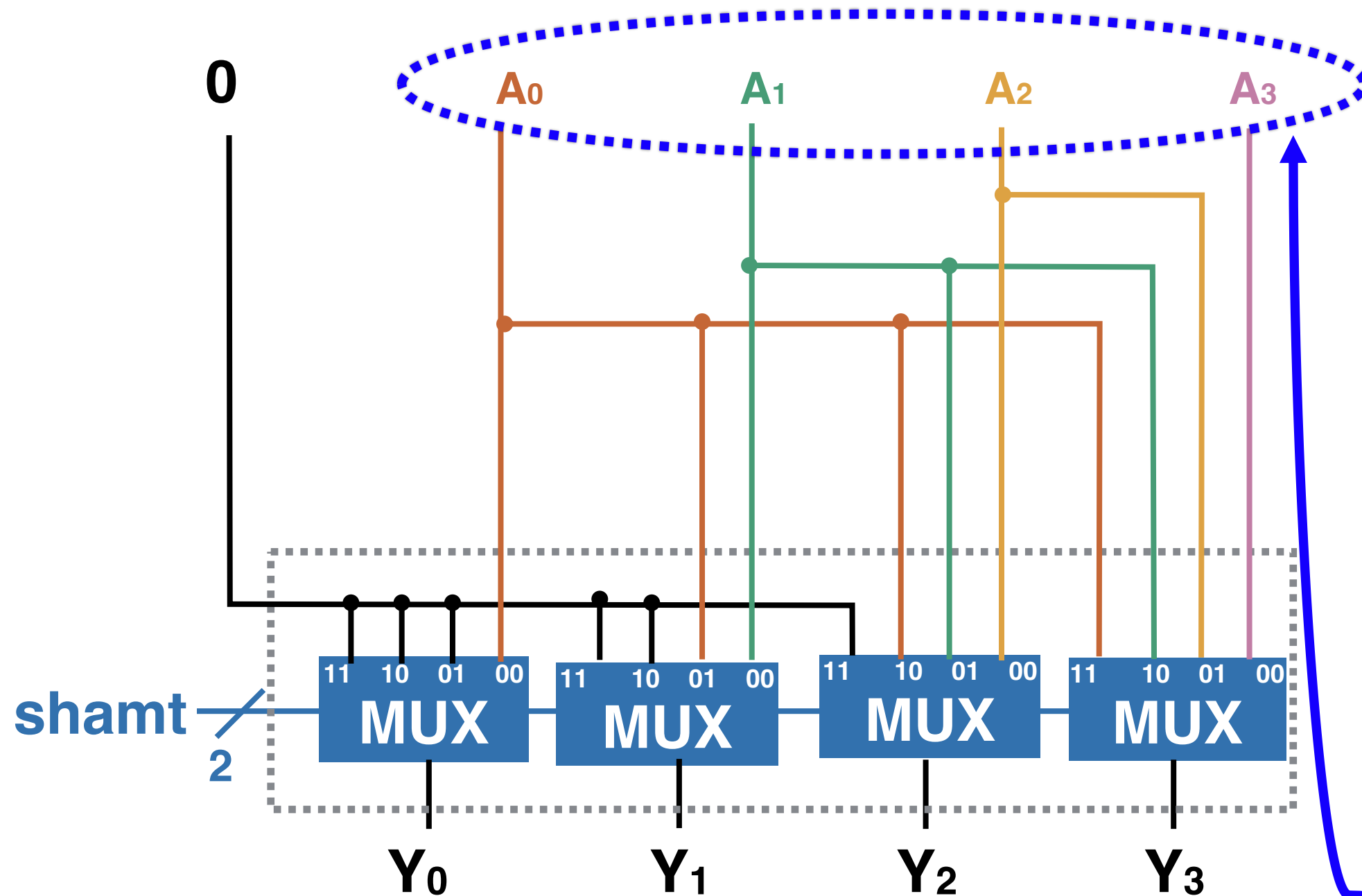


Based on the value of the selection input ( $shamt = \text{shift amount}$ )

Example: if $S = 01$ then $Y_3 = A_2$ $Y_2 = A_1$ $Y_1 = A_0$ $Y_0 = 0$	Example: if $S = 10$ then $Y_3 = A_1$ $Y_2 = A_0$ $Y_1 = 0$ $Y_0 = 0$	Example: if $S = 11$ then $Y_3 = A_0$ $Y_2 = 0$ $Y_1 = 0$ $Y_0 = 0$
---	---	---

The "chain" of multiplexers determines how many bits to shift


We don't need to modify the circuit, just change the order of inputs!

# Generic Shifter

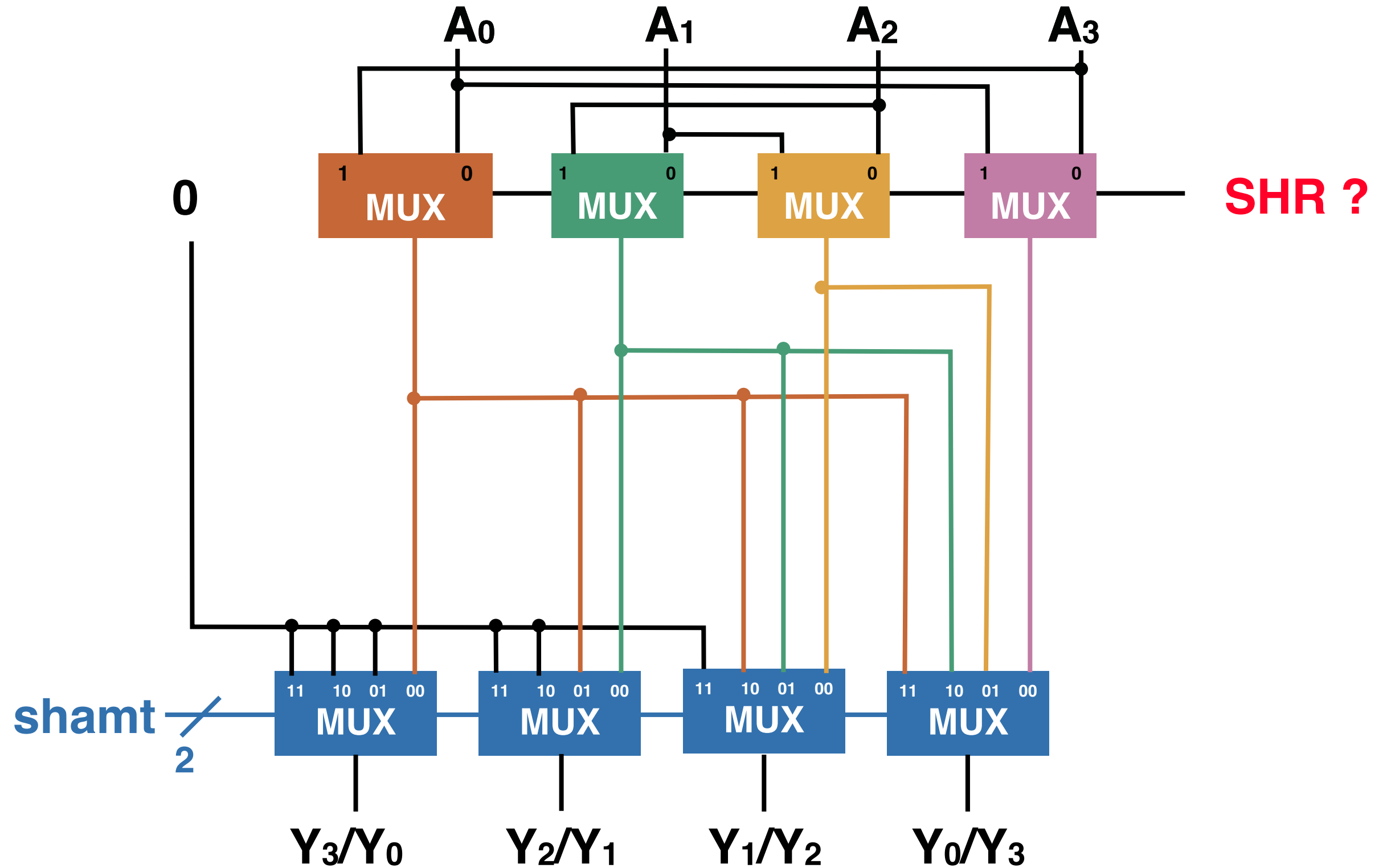





# Generic Shifter

 

# Generic Shifter

 


# Generic Shifter

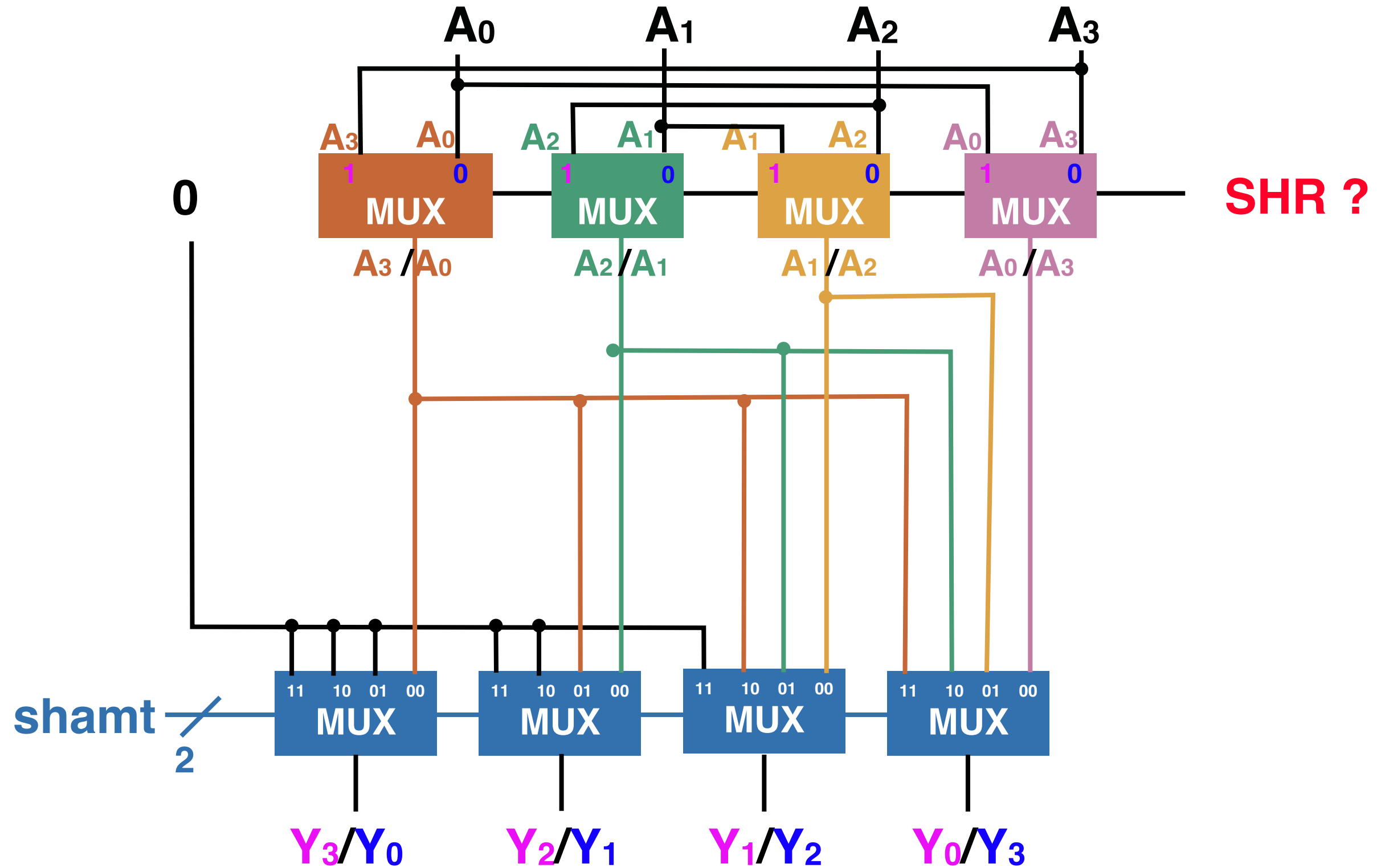

# Encoder

# Binary Encoders

 


A  $2^n$ -to- $n$  binary encoder.

Exactly one of input signals should have a value of 1 ( **one-hot coded**), and the outputs present the binary number that identifies which input is equal to 1.

# Binary Encoders

$w_3$	$w_2$	$w_1$	$w_0$	$y_1$	$y_0$
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

(a) Truth table (partial)

 

(b) Circuit

Incompletely specified function  
(12 don't care conditions)

K-maps for  $y_1$  and  $y_0$

4-to-2 binary encoder

Encoders can be used for efficient data communication and storage, since  $2^n$  bits are **compressed** to  $n$  bits in the process.

# Comparator

# Comparator

- A comparator compares the relative values of two binary numbers.
- If we design a comparator comparing two 4-bit unsigned numbers using a truth table, we need  $2^8 = 256$  rows.
- We actually can compare the two numbers bit by bit.

$A = a_3a_2a_1a_0$  unsigned

$B = b_3b_2b_1b_0$  unsigned

Define  $i_k = (b_k \oplus a_k)'$  -----  $i_k$  gives a 1 if  $b_k = a_k$

Then

$$A = B \quad AeqB = i_3i_2i_1i_0$$


$$A > B \quad AgtB = a_3b_3' + i_3a_2b_2' + i_3i_2a_1b_1' + i_3i_2i_1a_0b_0'$$

$$A < B \quad AltB = (AgtB + AeqB)'$$

Note that we can compare the bits of A and B at the same position from left to right. When we found a difference, the comparison is done.




# Comparator

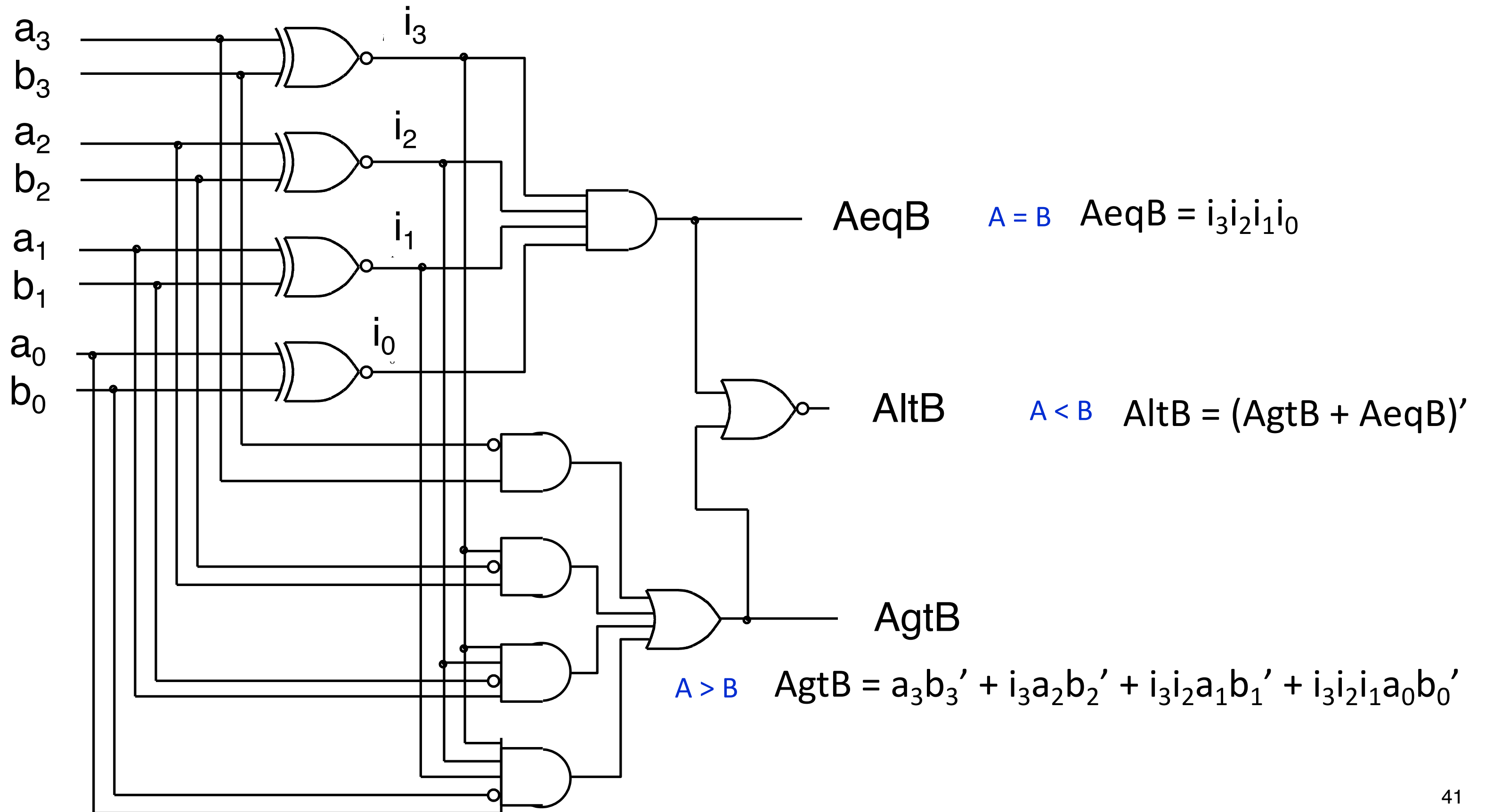

# Multiplier

Definition  $\mathbf{0} := [00000000]$

# Shift and add

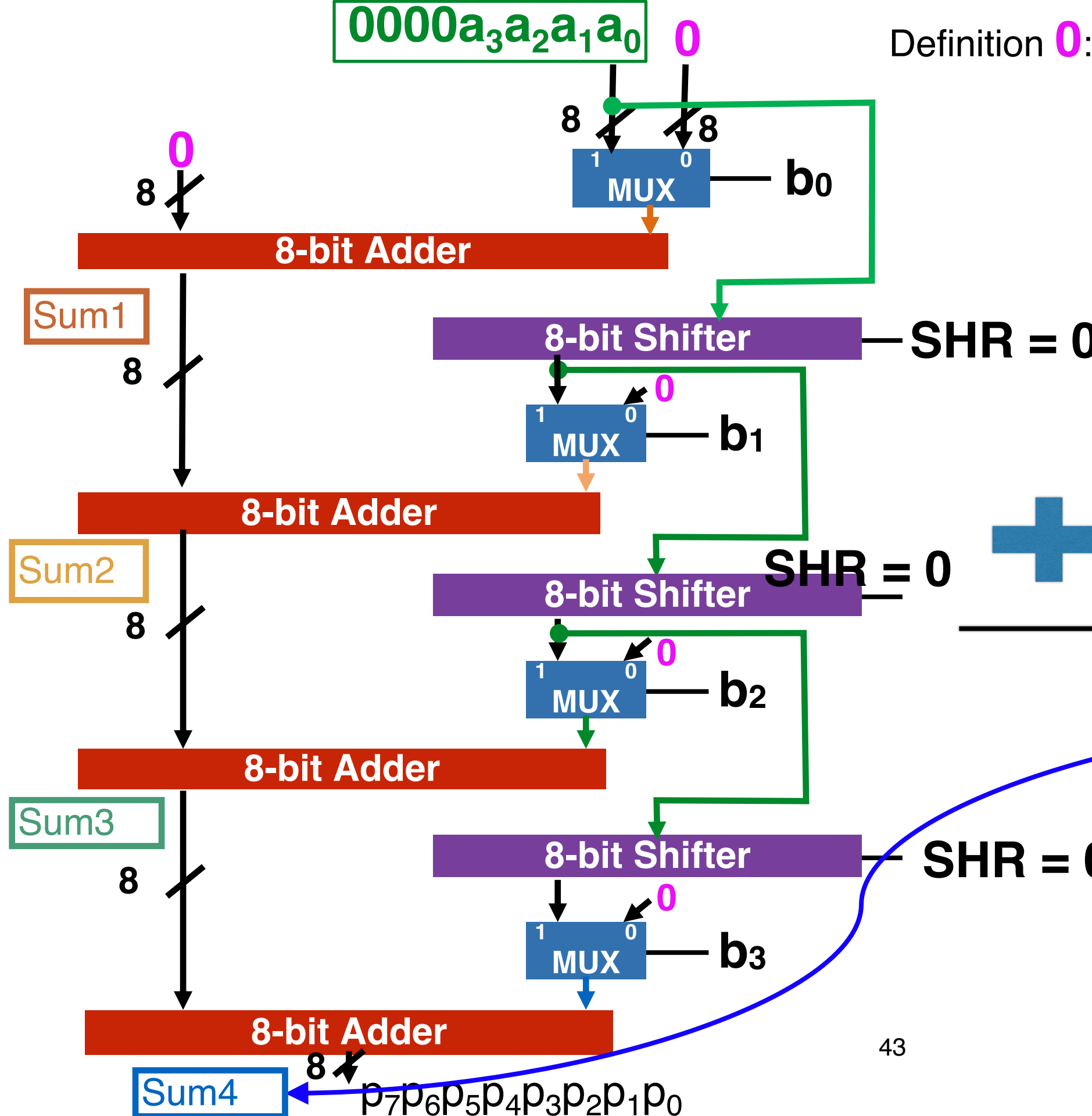

+

					$a_3$	$a_2$	$a_1$	$a_0$
				$\times$	$b_3$	$b_2$	$b_1$	$b_0$
0	0	0	0	$a_3b_0$	$a_2b_0$	$a_1b_0$	$a_0b_0$	
0	0	0	$a_3b_1$	$a_2b_1$	$a_1b_1$	$a_0b_1$	$\emptyset$	
0	0	$a_3b_2$	$a_2b_2$	$a_1b_2$	$a_0b_2$	$\emptyset$	$\emptyset$	
0	$a_3b_3$	$a_2b_3$	$a_1b_3$	$a_0b_3$	$\emptyset$	$\emptyset$	$\emptyset$	
$p_7$	$p_6$	$p_5$	$p_4$	$p_3$	$p_2$	$p_1$	$p_0$	

Sum4

# Divider

# Division of positive binary numbers

- Repeated subtraction
  - Set quotient to 0
  - Repeat while (dividend  $\geq$  divisor)
    - Subtract divisor from dividend
    - Add 1 to quotient
  - When dividend  $<$  divisor:
    - Remainder = dividend
    - Quotient is correct