


Multiplexer and Decoder

Jia Chen
jiac@ucr.edu

Multiplexer

Let's start with a 2-to-1 Multiplexer (MUX)

 
- The MUX has two input ports — numbered as 0 and 1
- To select from two inputs, you need a 1-bit control/select signal to indicate the desired input port




Input			Output
A	B	Sel	
0	0	0	0
0	1	0	0
1	0	0	1
1	1	0	1
0	0	1	0
0	1	1	1
1	0	1	0
1	1	1	1

2-to-1 MUX
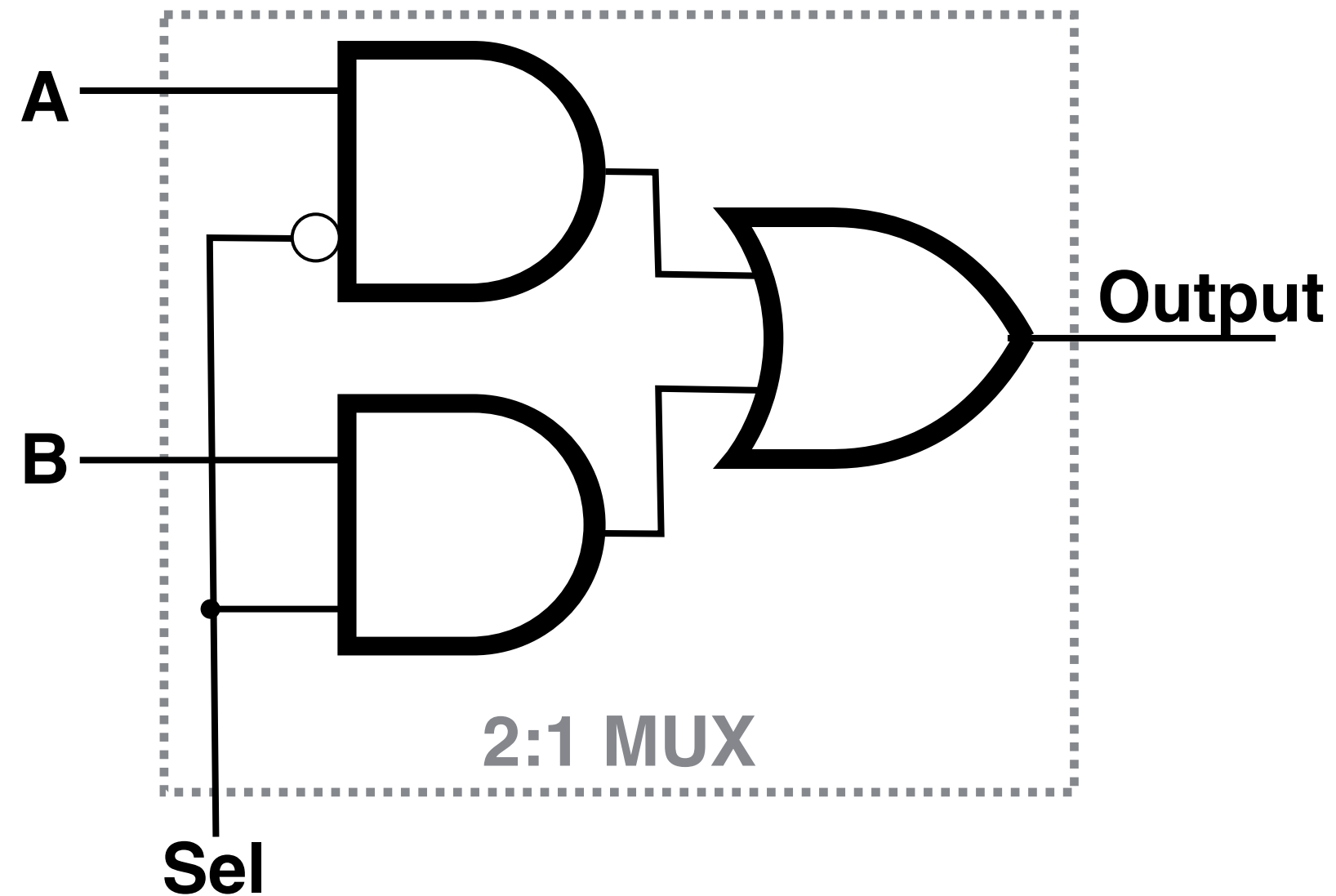
$$\text{Output} = A\text{Sel}' + B\text{Sel}$$



4-to-1 MUX

 


$S1==0 \ \&\& \ S0==0$ output A
 $S1==0 \ \&\& \ S0==1$ output B
 $S1==1 \ \&\& \ S0==0$ output C
 $S1==1 \ \&\& \ S0==1$ output D

$$\text{Output} = AS0'S1' + BS0S1' + CS0'S1 + DS0S1$$




2
S

Graphical symbols

 


16-to-1 MUX

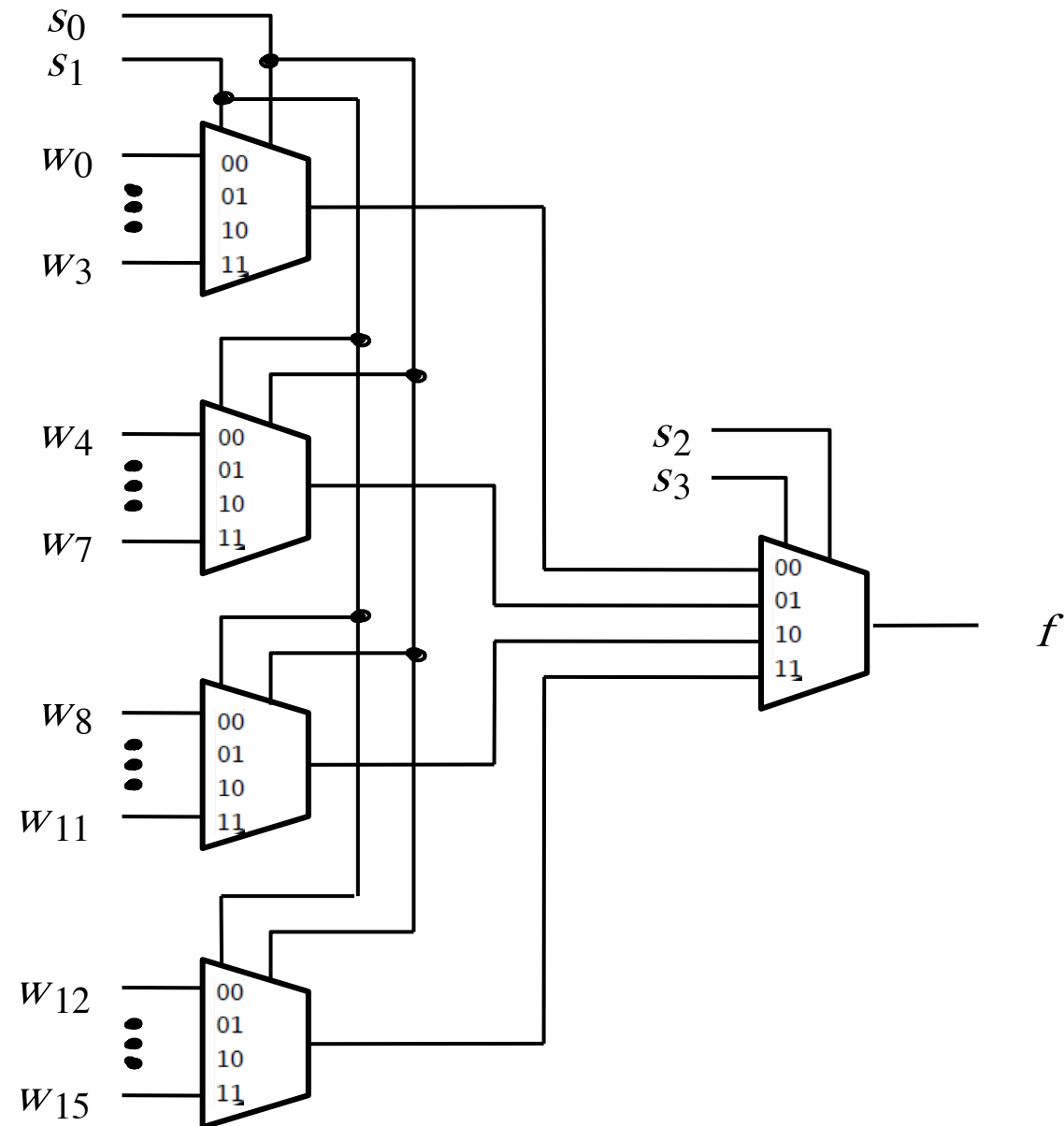

A 16-to-1 multiplexer.

N-bit MUX

 
- What if we need to output an N-bit (say 4-bit) number from the input set?



Decoder

Decoders

 Only one of the outputs is asserted at a time (i.e., which is different from all the others), and each output corresponds to one valuation of the inputs.




An n -to- 2^n binary decoder.


Decoders

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

 


(b) Graphical symbol

 

(c) Logic circuit

Decoders

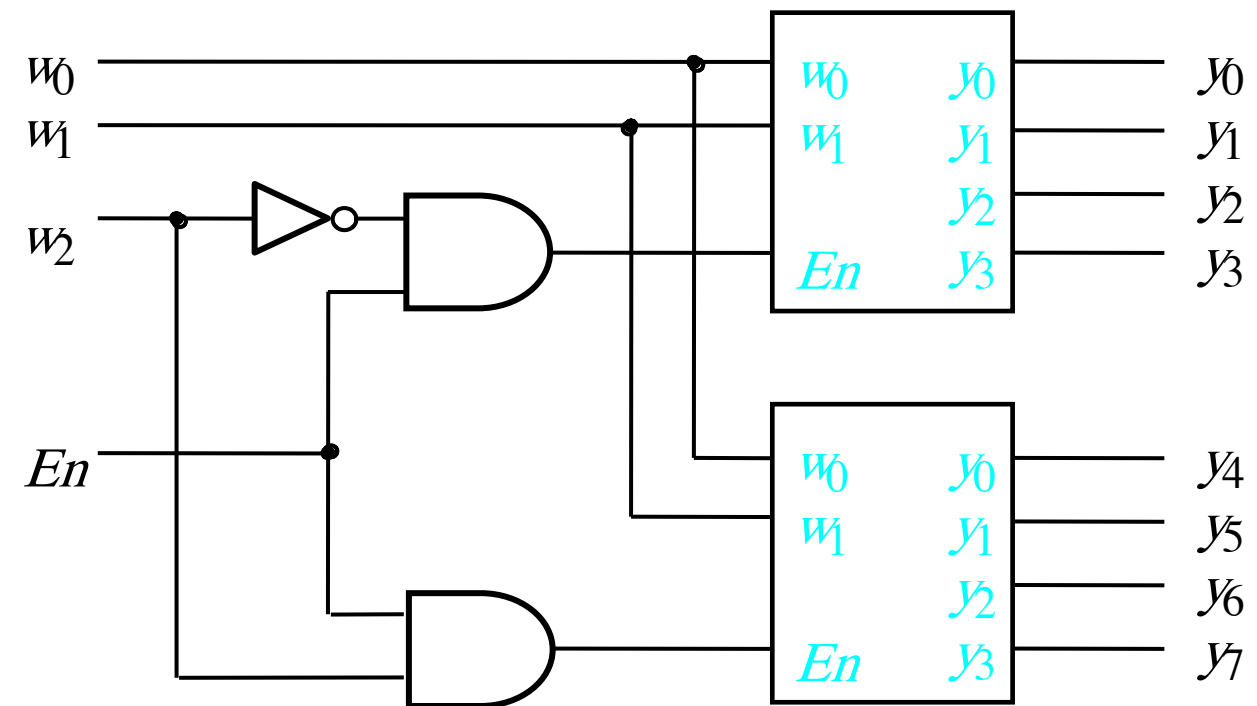


A 3-to-8 decoder using two 2-to-4 decoders.

Incompletely Specified Functions

- Certain input conditions can never occur
E. g. $(x_1, x_2) = 11$ is a **don't-care condition**: a circuit can be designed by ignoring this condition
- A function that has **don't-care condition(s)** is said to be **incompletely specified**.
- Assume that the function value for these valuations is **either 1 or 0**, whichever is more useful

Truth table with Don't Cares

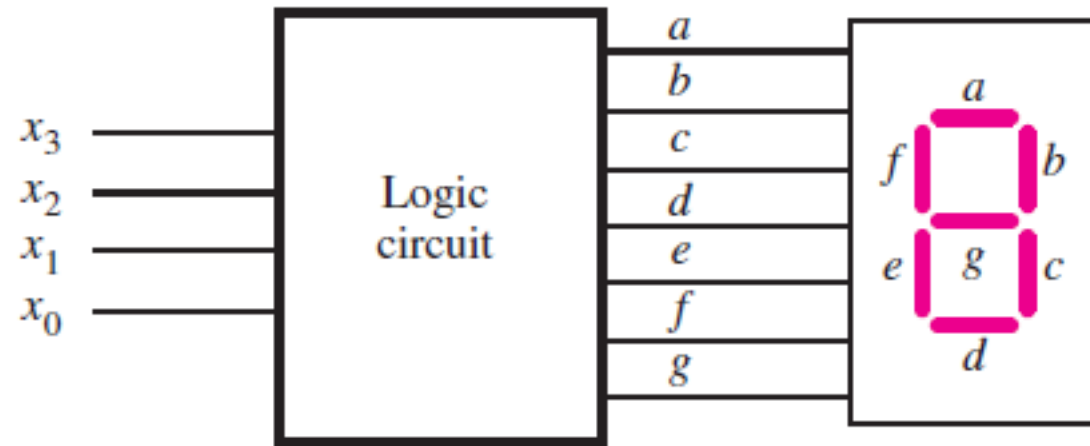

(a) Logic circuit and 7-segment display

Don't-care
conditions

	x_3	x_2	x_1	x_0	a	b	c	d	e	f	g
0-1000	0	0	0	0	1	1	1	1	1	1	0
	0	0	0	1	0	1	1	0	0	0	0
	0	0	1	0	1	1	0	1	1	0	1
	0	0	1	1	1	1	1	1	0	0	1
	0	1	0	0	0	1	1	0	0	1	1
	0	1	0	1	1	0	1	1	0	1	1
	0	1	1	0	1	0	1	1	1	1	1
	0	1	1	1	1	1	1	0	0	0	0
	1	0	0	0	1	1	1	1	1	1	1
	1	0	0	1	1	1	1	1	0	1	1
1000-1111	1	0	1	0	x	x	x	x	x	x	x
	1	0	1	1	x	x	x	x	x	x	x
	1	1	0	0	x	x	x	x	x	x	x
	1	1	0	1	x	x	x	x	x	x	x
	1	1	1	0	x	x	x	x	x	x	x
	1	1	1	1	x	x	x	x	x	x	x