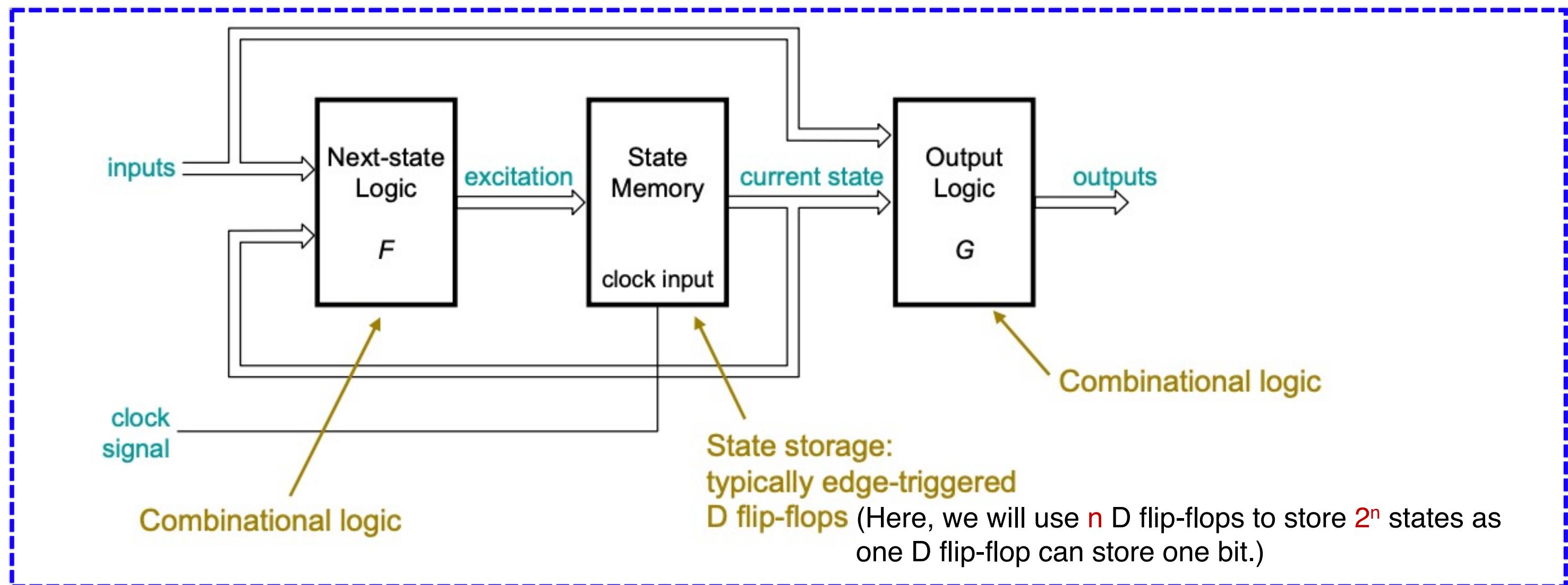


# **Canonical Form: Mealy and Moore Machines**


# Mealy FSM

**Mealy machine:** output depends on state and current input

Next state =  $F$  (current state, input); Output =  $G$  (current state, input)



**State transition on Mealy machine:**

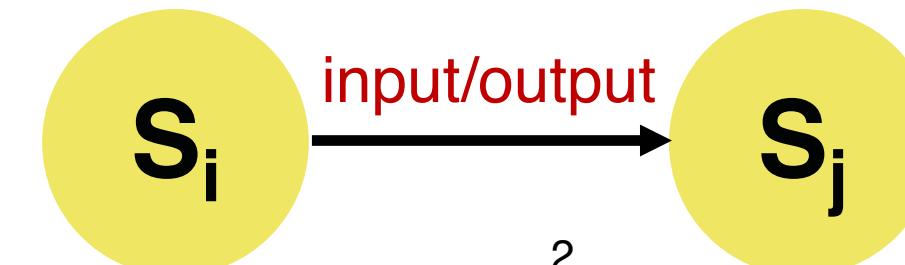


$S_i$  and  $S_j$  are two states


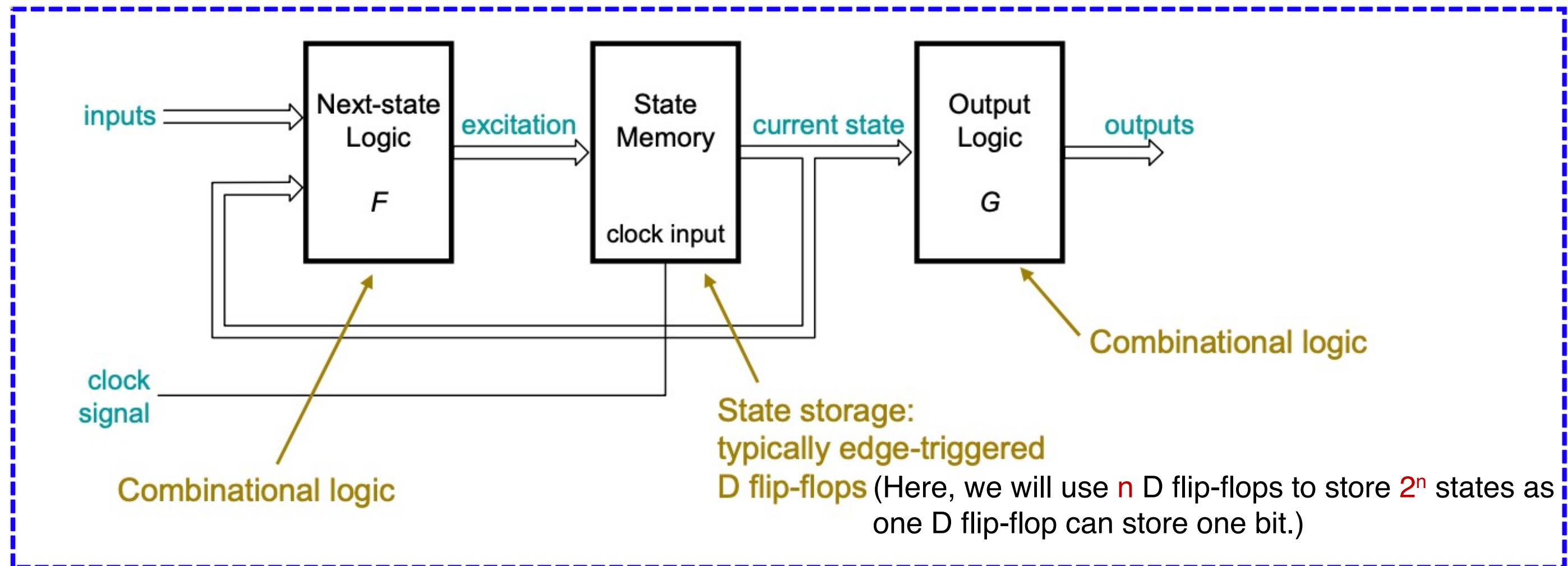
# Moore FSM

**Moore machine:** output depends only on current state

Next state =  $F$  (current state, input); Output =  $G$  (**current state**)




**State transition on Moore machine:**

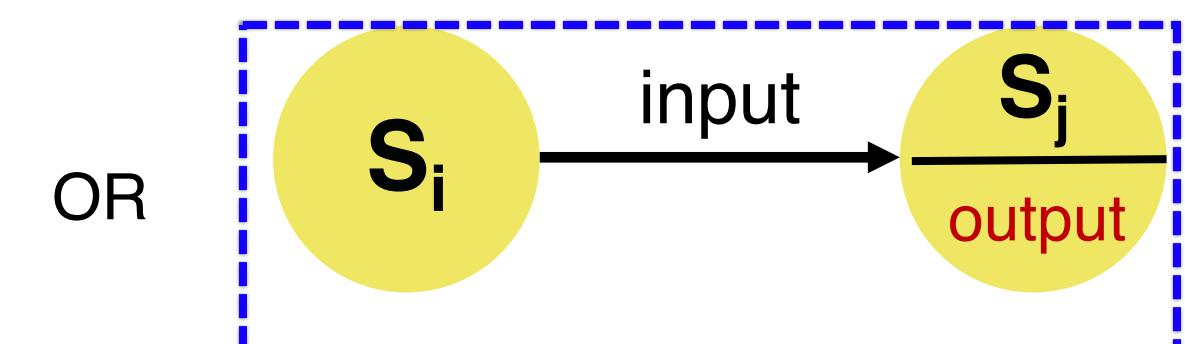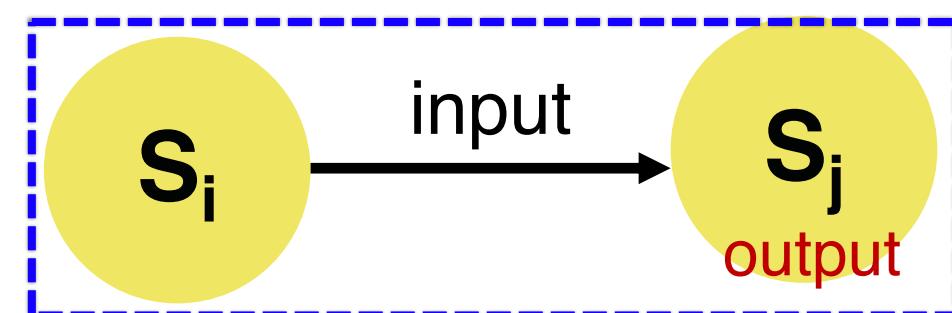


# Mealy machine vs Moore machine


Mealy

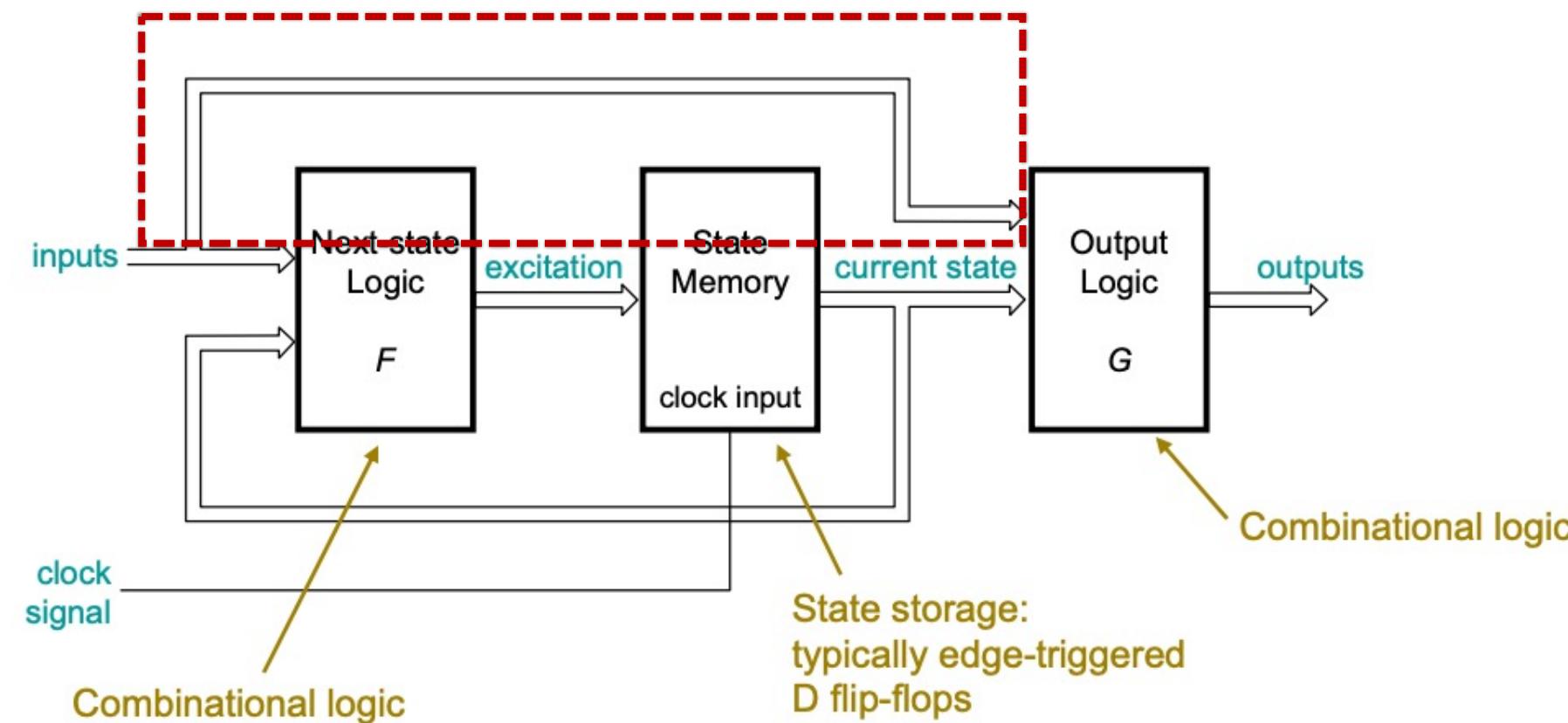

Moore

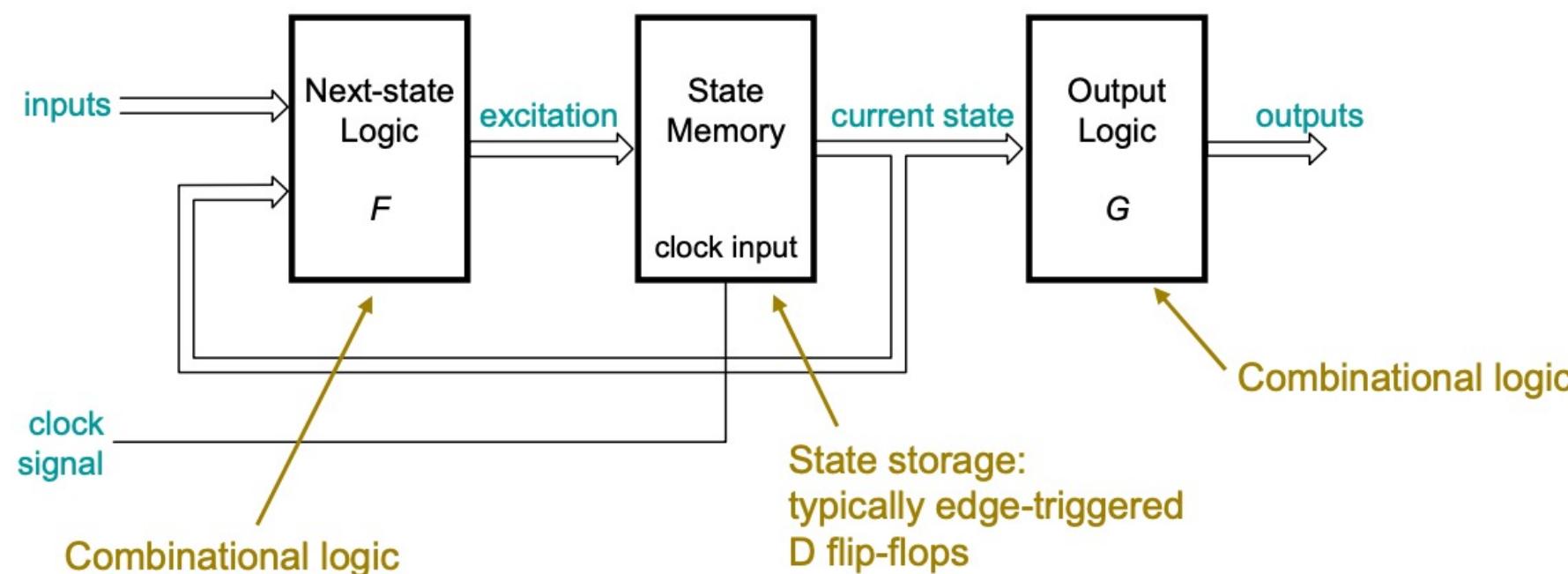


# Initial state of a FSM

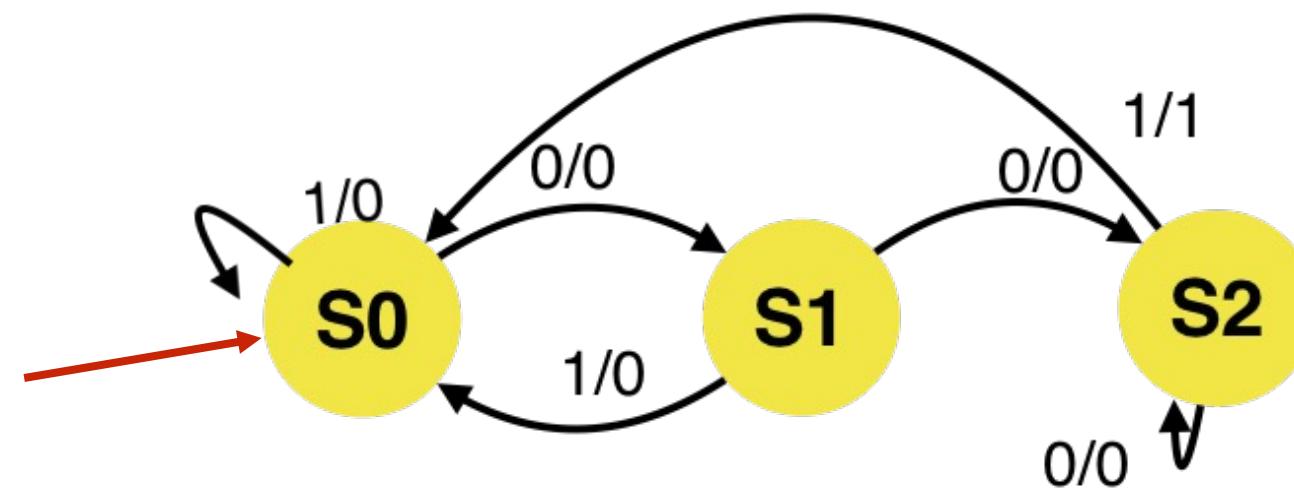

- An arrow points to the initial state, i.e.,  $S_0$  is the initial state
- Not every FSM diagram specifies the initial state.
- Not every initial state is called  $S_0$ .

# **How to make FSM true?**

# Revisit the FSM for a timer

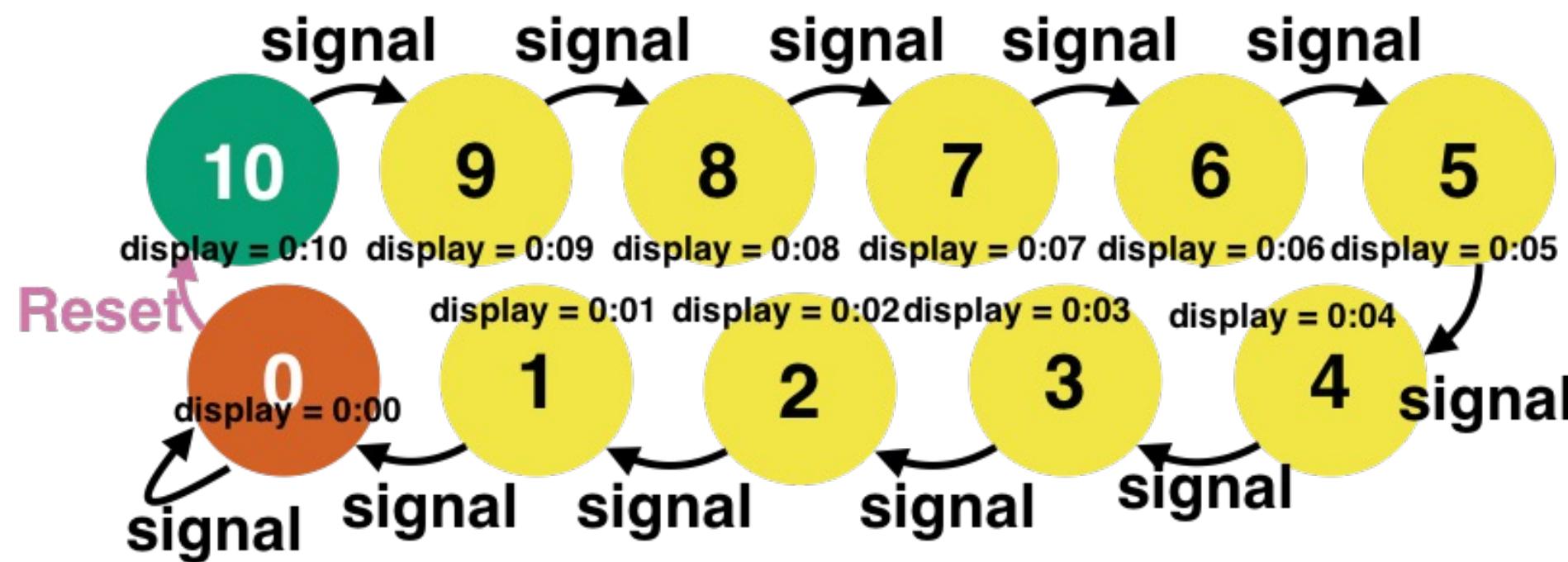

# What do we need to physically implement the timer?



- 1) Logic to display the remaining time
  - use **combinational logic**, e.g., 7-segment display
- 2) Logic that uses the “*current state*” and “*new input(s)*” to transit to a “*new state*” and generate the “*output(s)*”
  - use **combinational logic**
- 3) Logic to keep track of the “*current state*”
  - **need memory**
- 4) A control signal that helps us to transit from current state to next state at the right time
  - **need clock**

# **The basic form of memory**


# SR-Latch: the very basic “memory”

NOR gate


Input		Output
A	B	
0	0	1
0	1	0
1	0	0
1	1	0

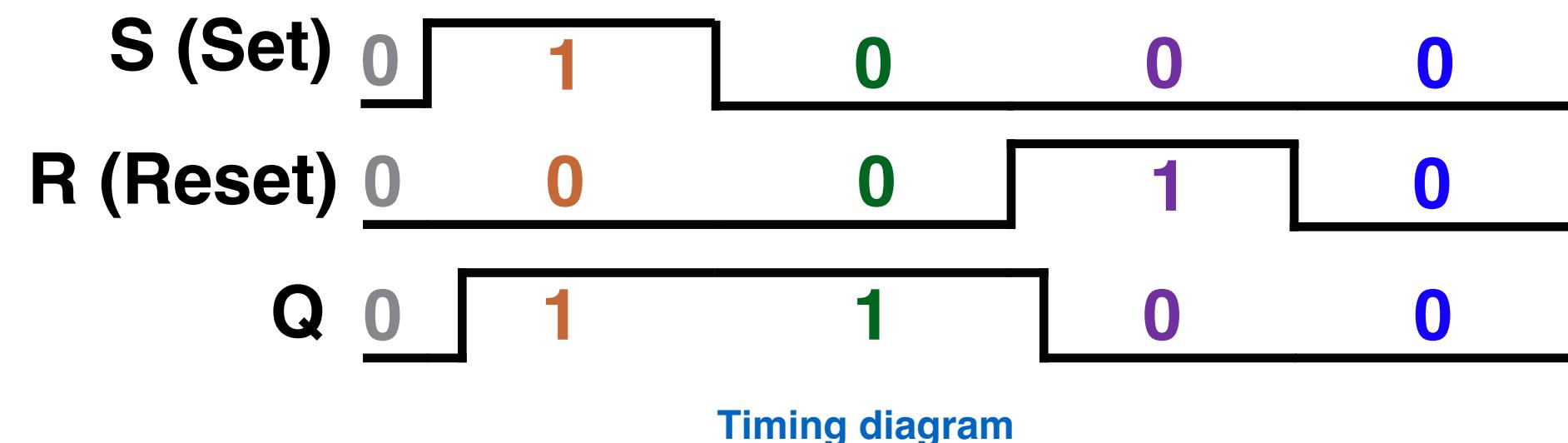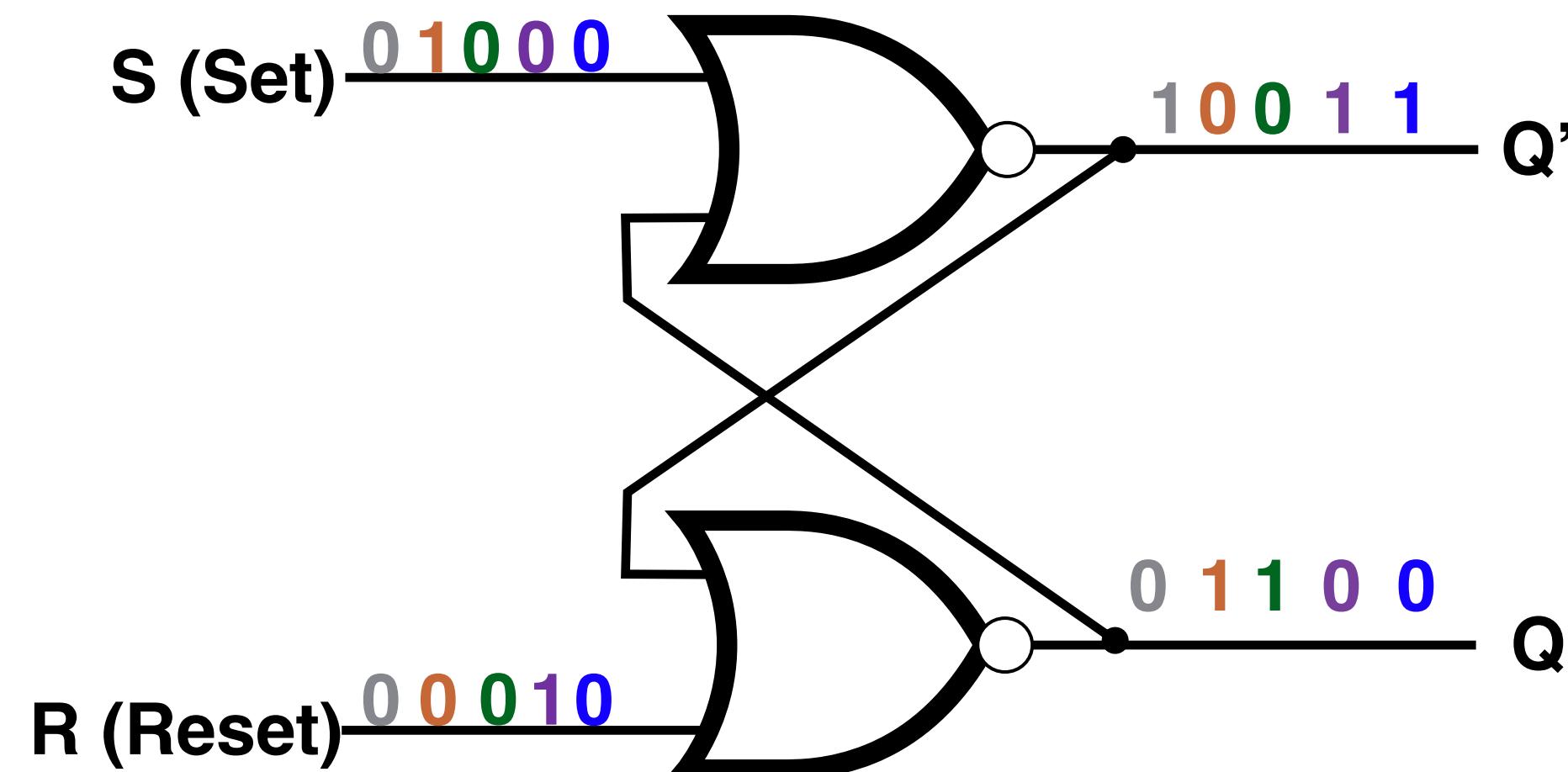

# SR-Latch: the very basic “memory”

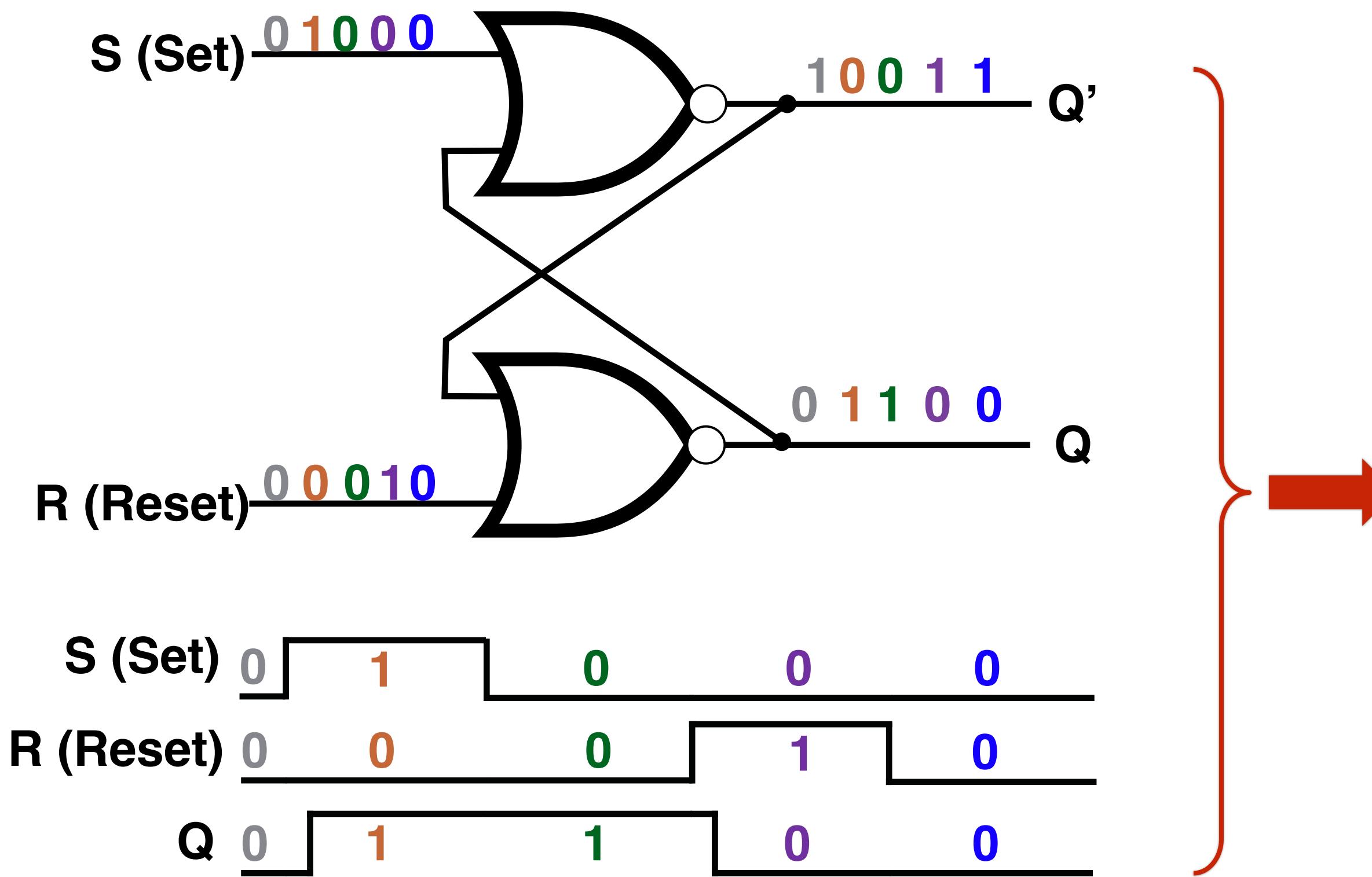


# SR-Latch: the very basic “memory”

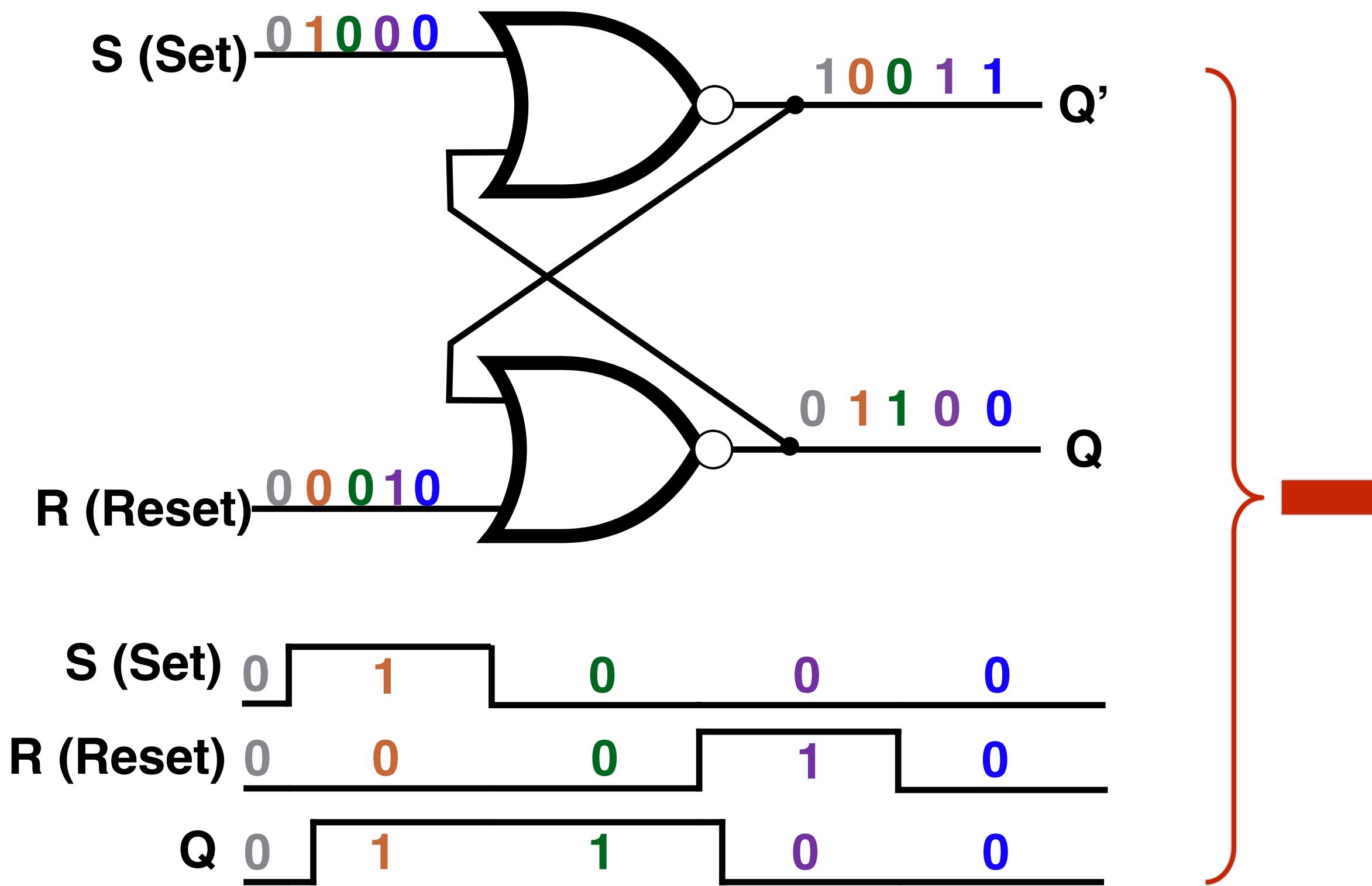

$Q(t+1) = 1$  when  $S=1$ ,  $R=0$ ,  
regardless of  $Q(t)$

**Set — Make the “stored bit 1”**

# SR-Latch: the very basic “memory”

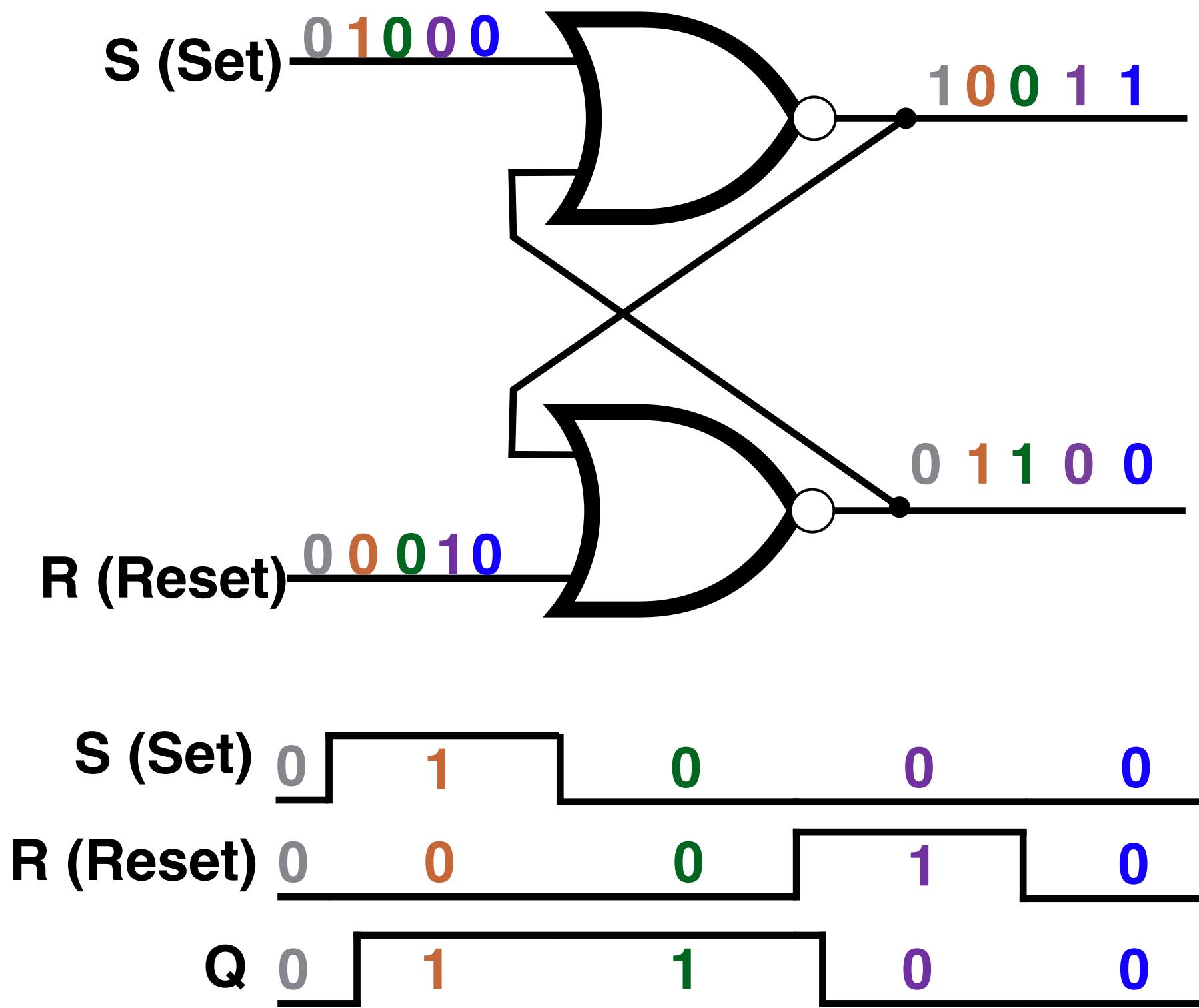


S	R	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

$Q(t+1) = 0$  when  $R=1$ ,  $S=0$ ,  
regardless of  $Q(t)$

Reset – Make the “stored bit 0”

# SR-Latch: the very basic “memory”

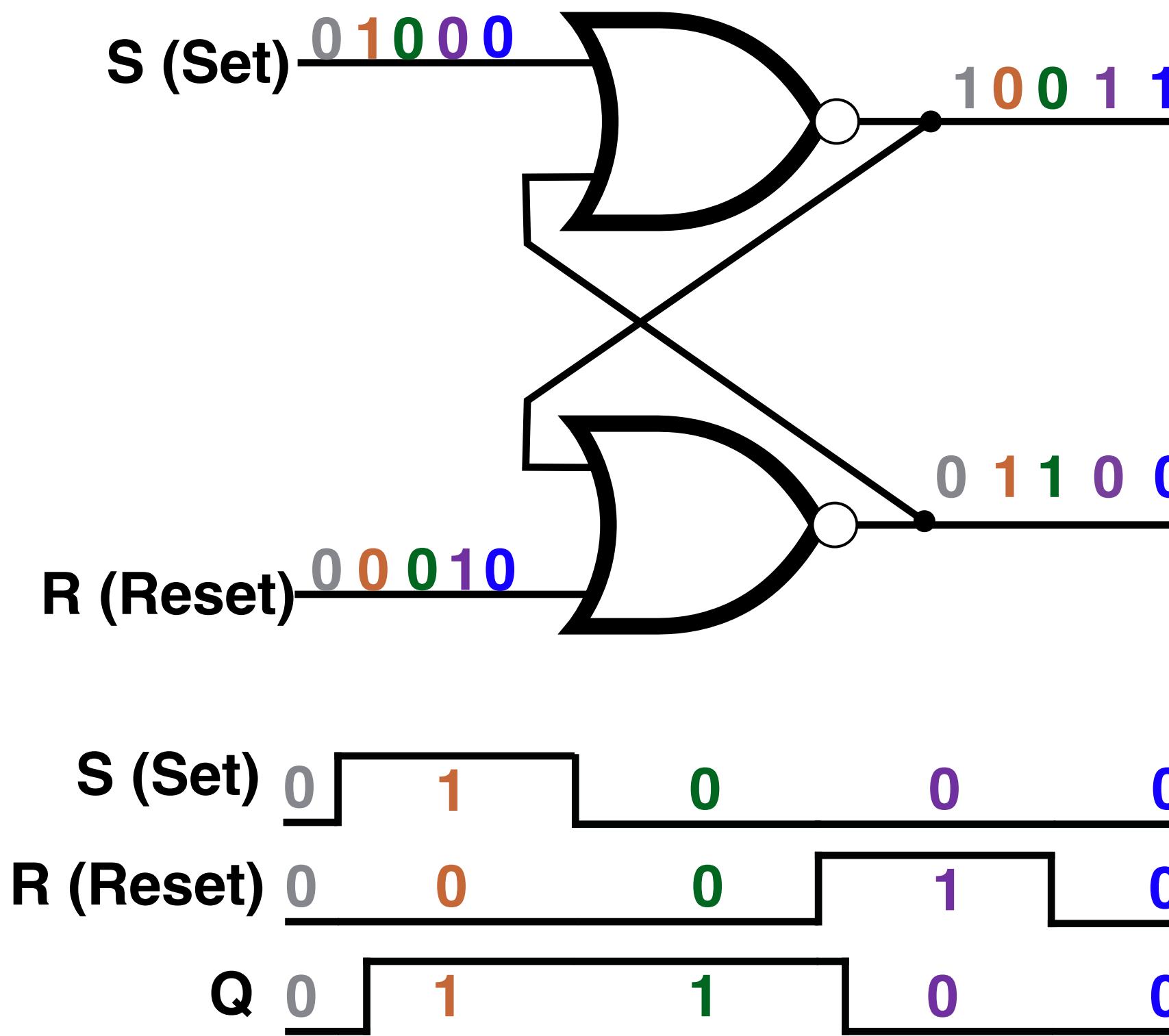


Hold – Store the previous value

S	R	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1


$Q(t+1) = Q(t)$  when  $R=0, S=0$

# SR-Latch: the very basic “memory”

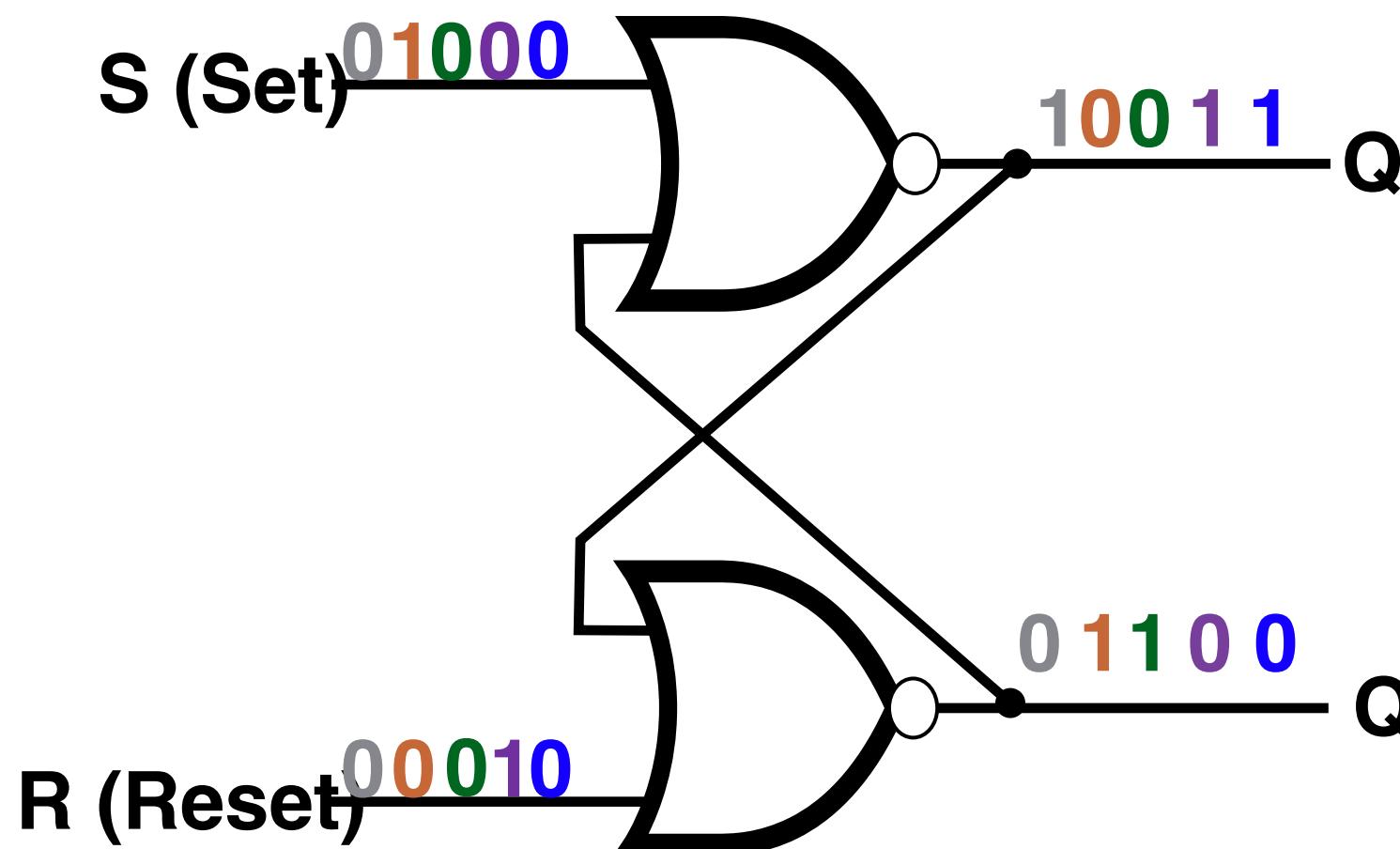

S	R	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	
1	1	1	

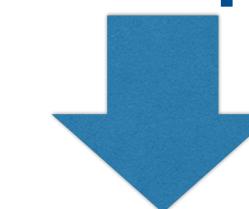**Set** – Make the “stored bit 1”  
**Reset** – Make the “stored bit 0”  
**Hold** – Store the previous value




**The circuit has memory!**


# What if both S & R are “1”?

NOR gate

Input		Output
A	B	
0	0	1
0	1	0
1	0	0
1	1	0

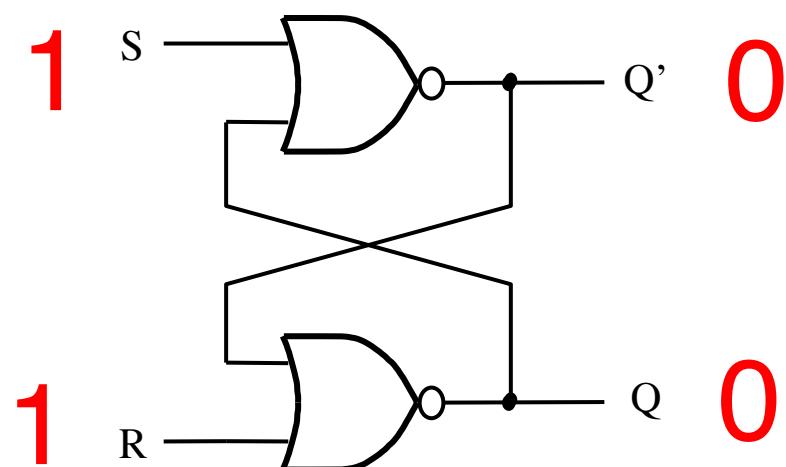


Doesn't function if both are "1"!

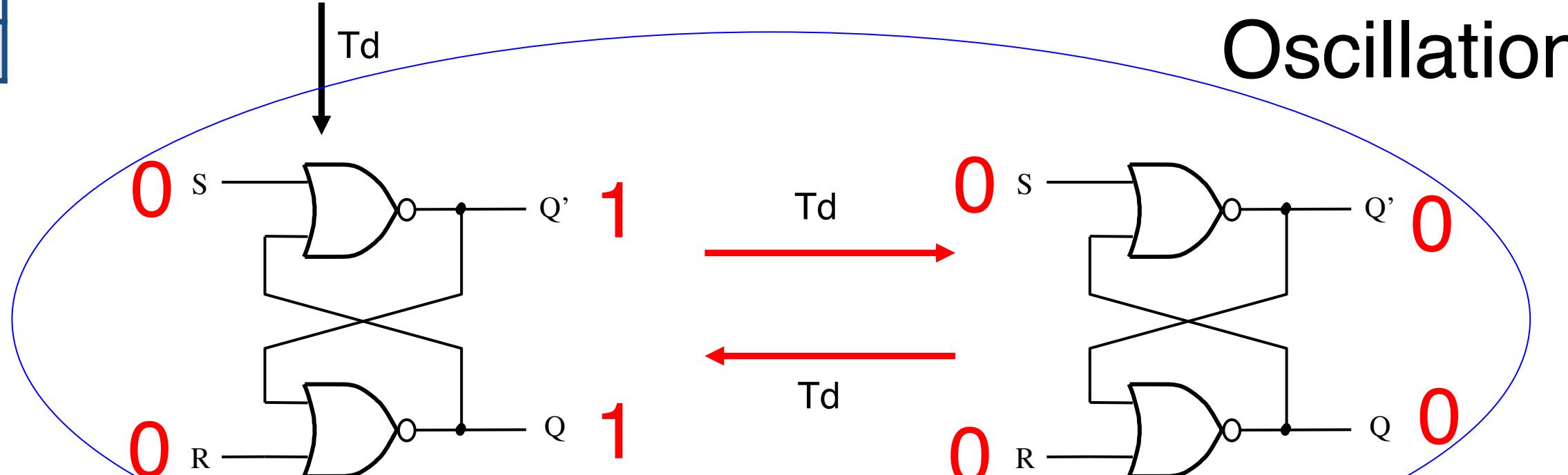


Oscillation
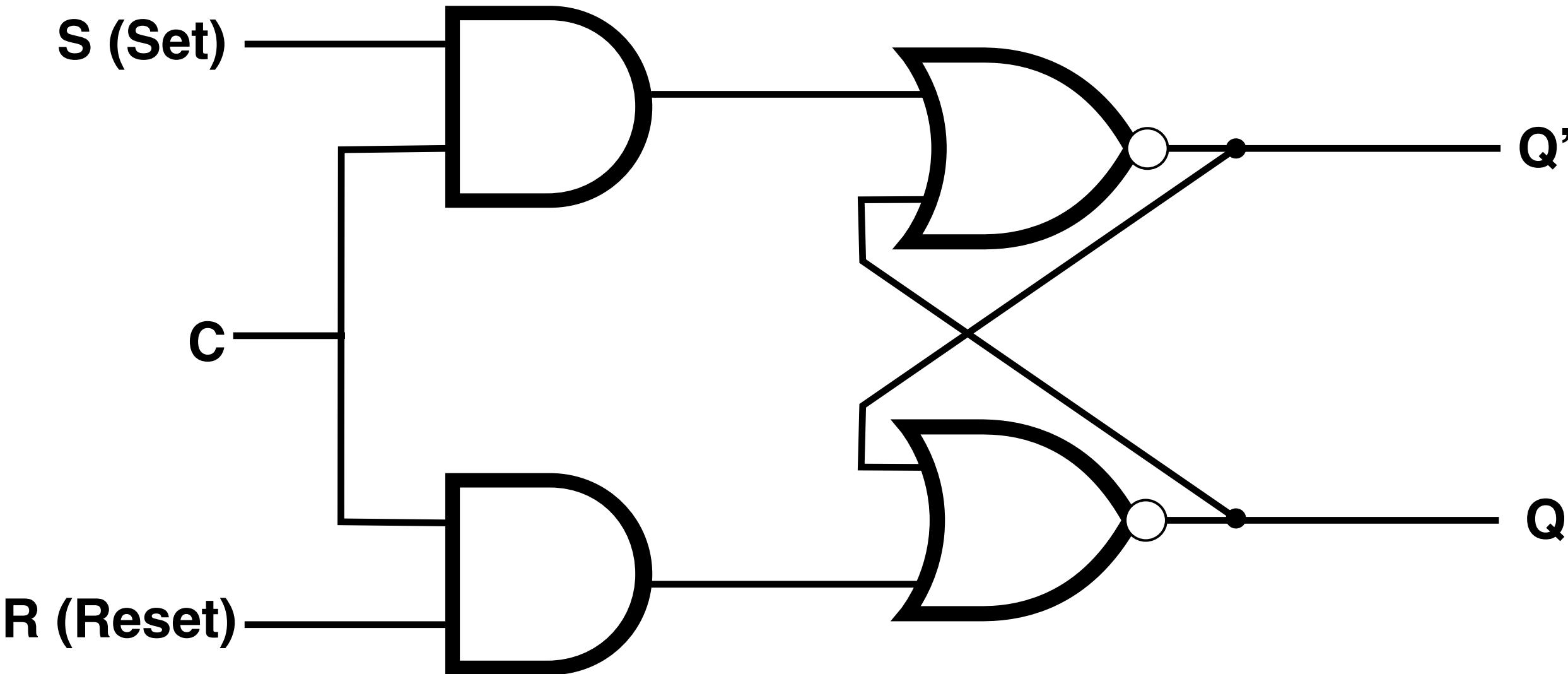
# Add an input! – Level-Sensitive SR Latch



- C is a signal aware of the **timing** of gates – **clock**



# Gated SR Latches

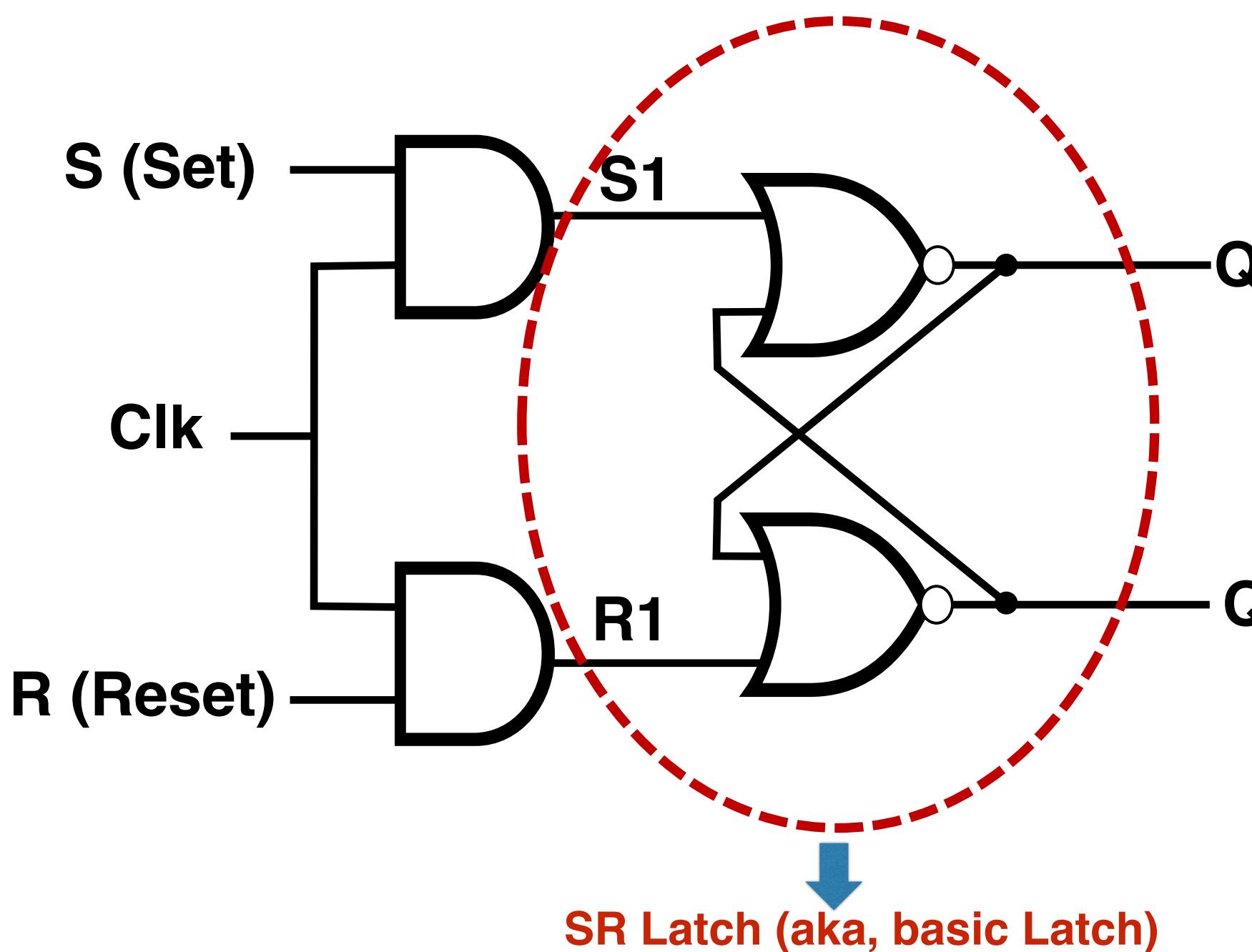

Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$
1	0	0	$Q(t)$
1	0	1	0
1	1	0	1
1	1	1	x




Characteristic table

# Gated SR Latches

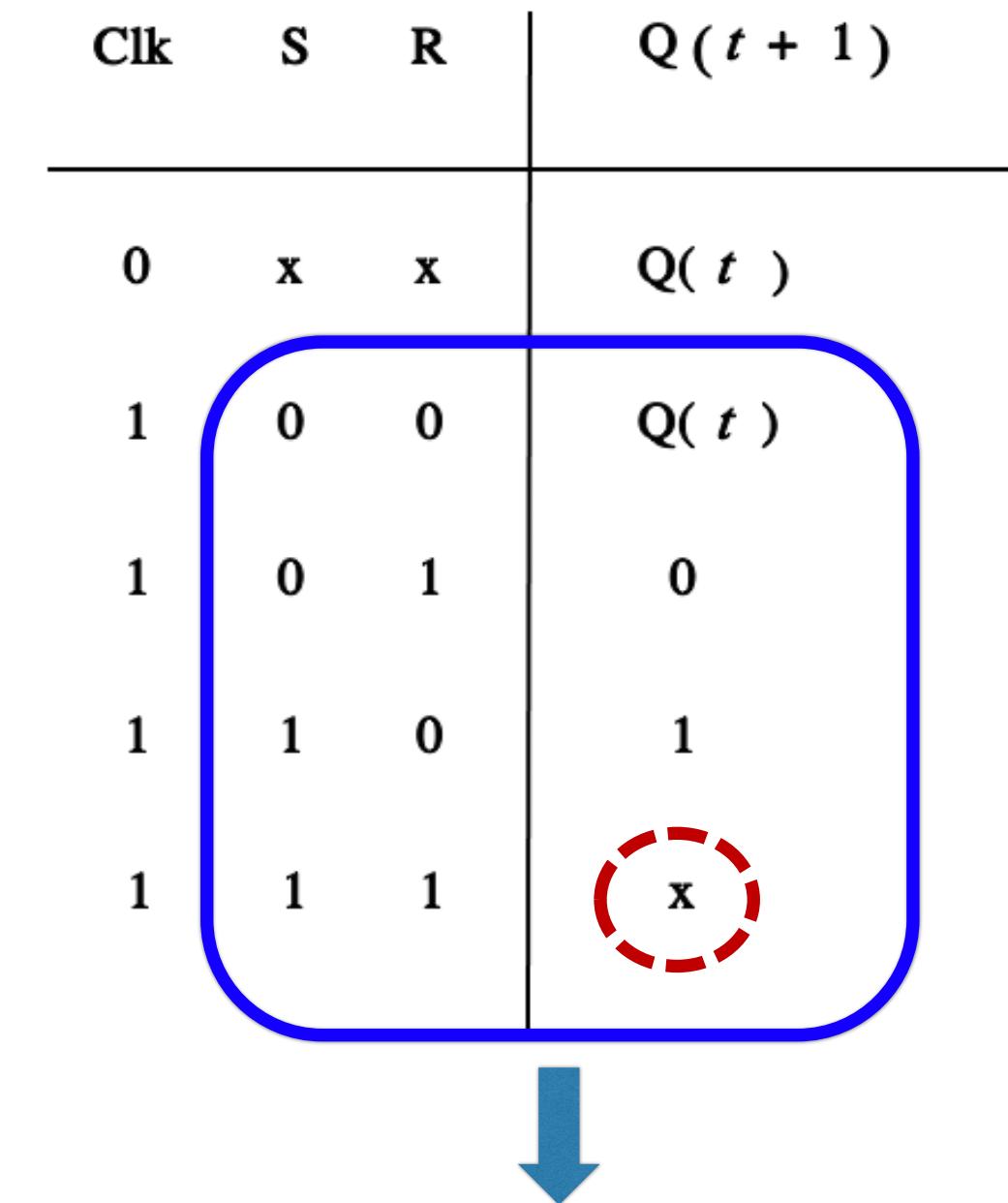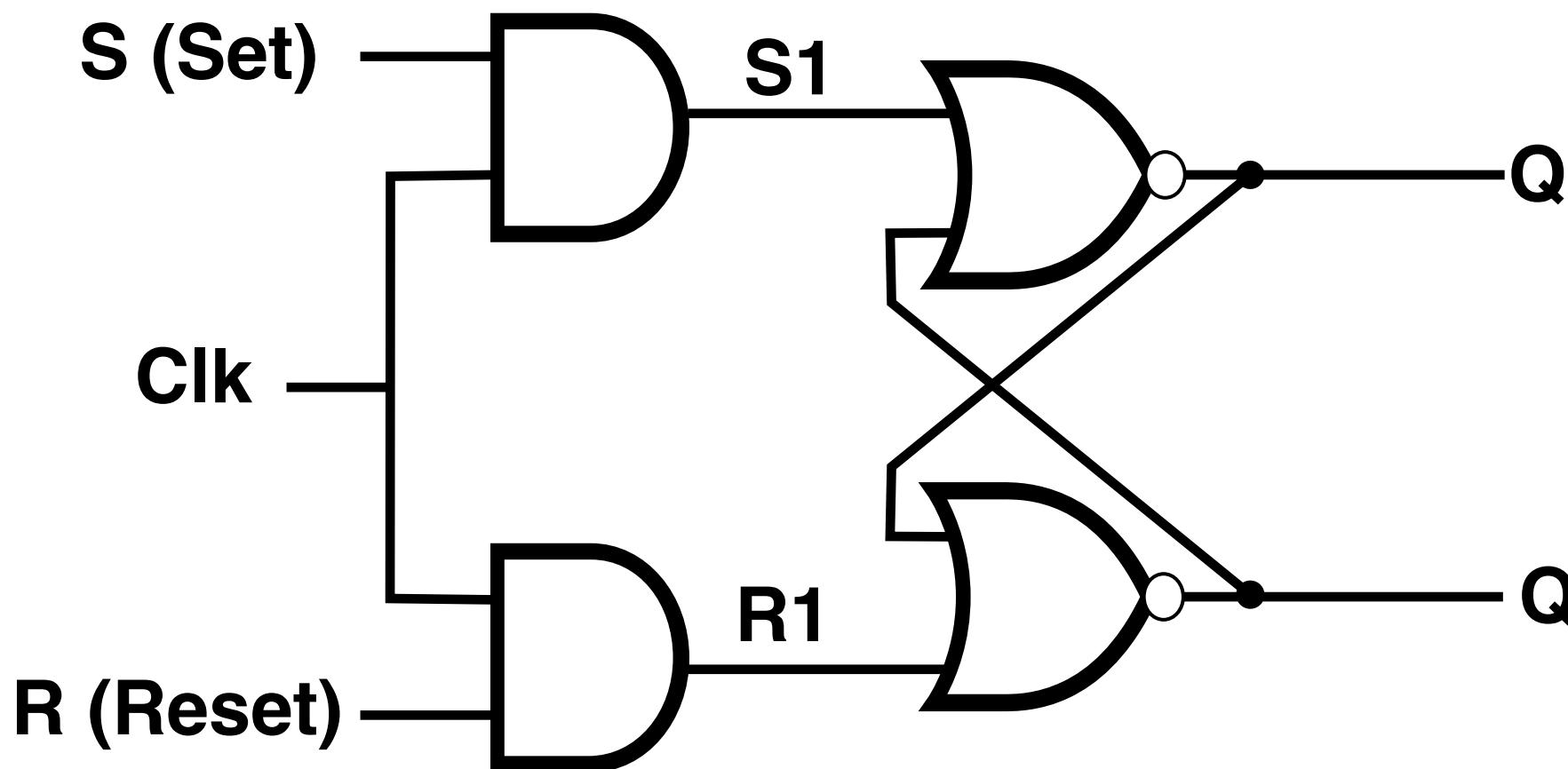

When  $\text{Clk} = 1$ , Gated SR Latch = SR Latch


# Two designs of the Gated SR Latches

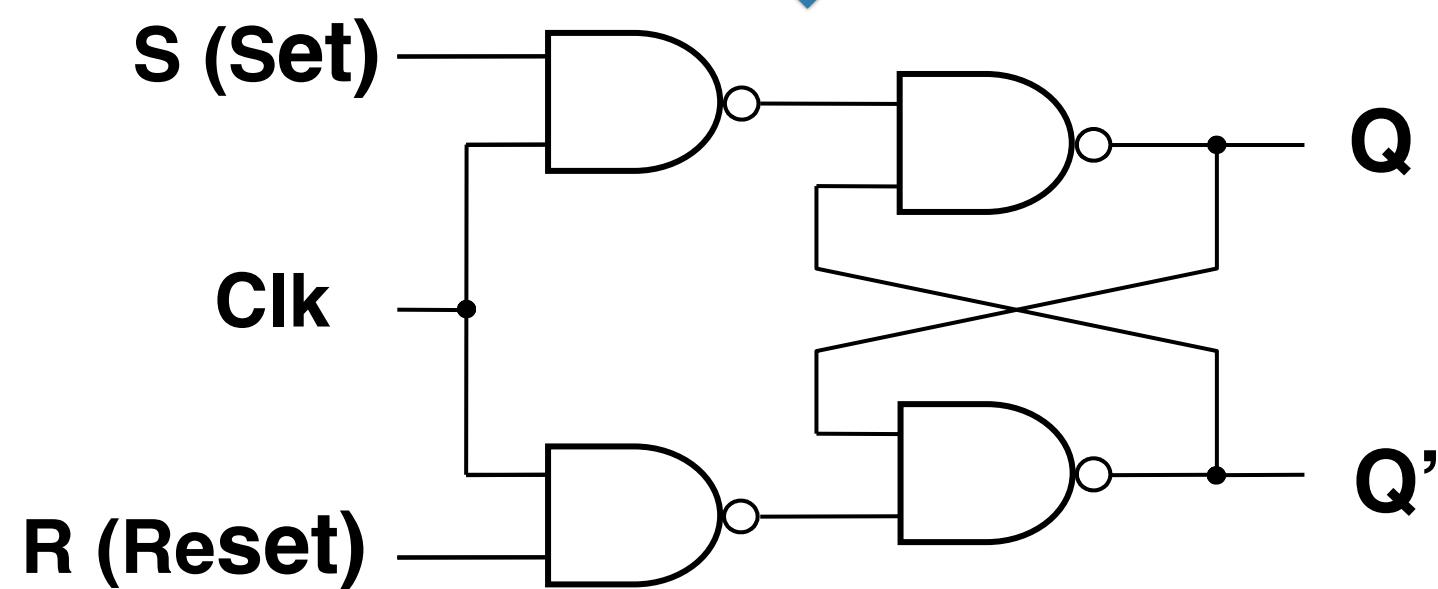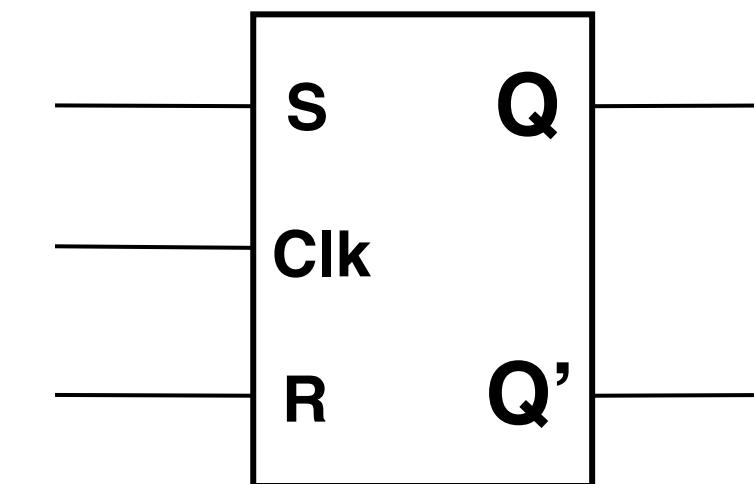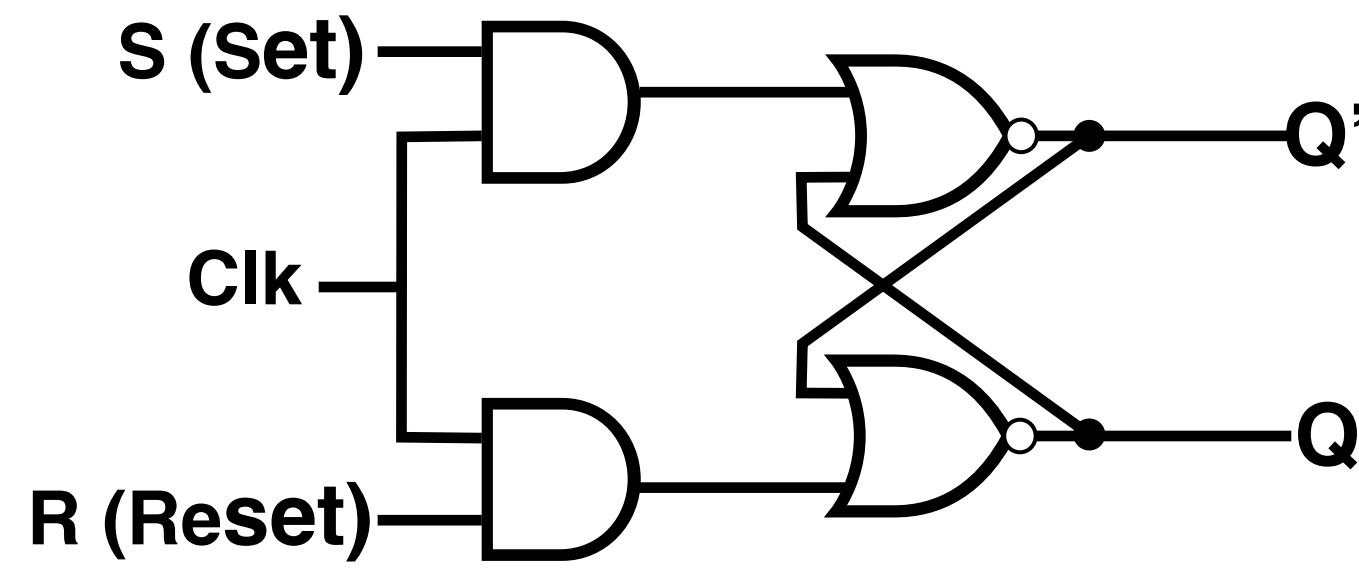

Graphical symbol

# D-Latch

We will never  
get 1, 1 in this  
way

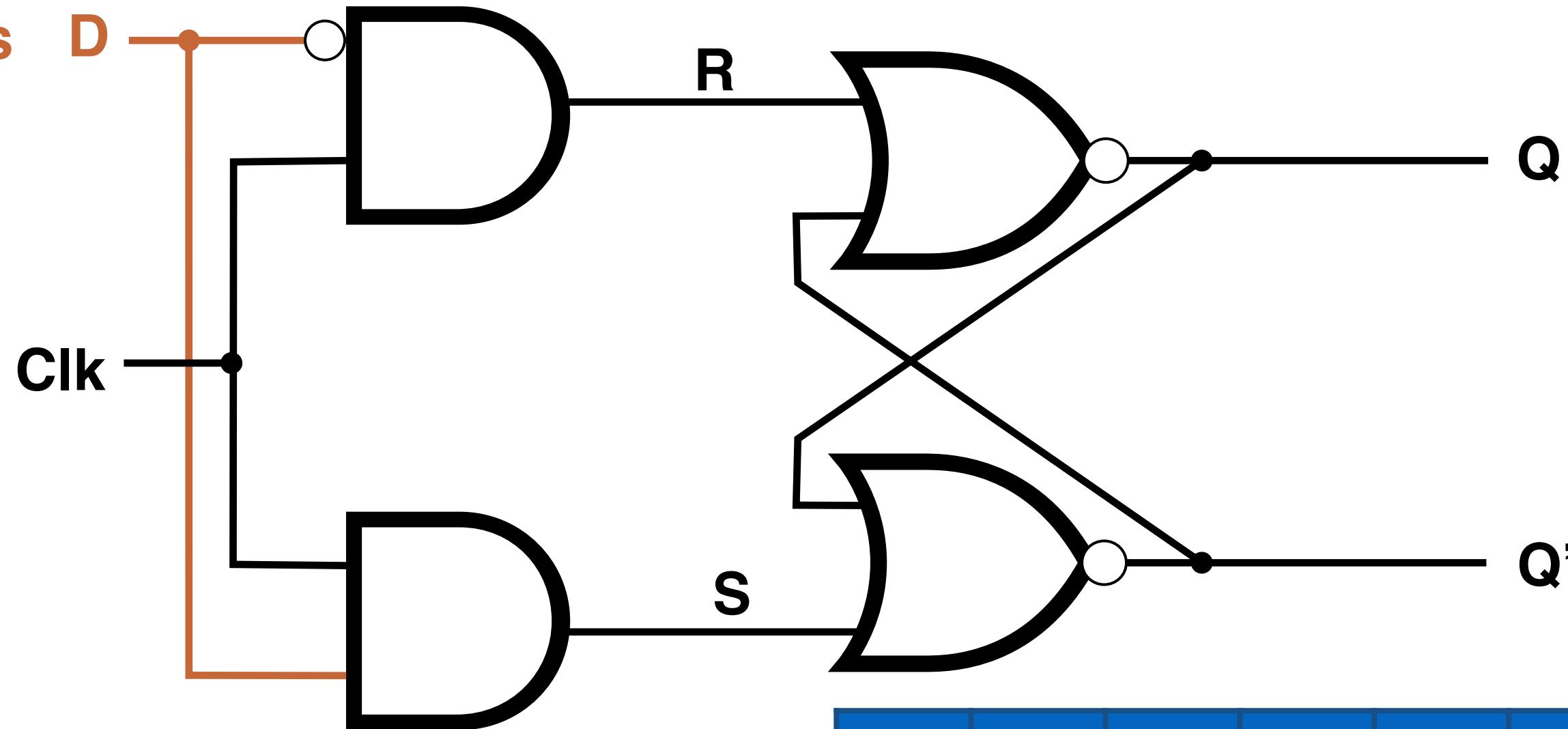

Clk	D	D'	S	R	Q(t+1)	Q(t+1)'
0	X	X'	0	0	Q(t)	Q(t)'
1	0	1	0	1	0	1
1	1	0	1	0	1	0

# D-Latch

C <sub>lk</sub>	D	D'	S	R	Q(t+1)	Q(t+1)'
0	X	X'	0	0	Q(t)	Q(t)'
1	0	1	0	1	0	1
1	1	0	1	0	1	0

Note:


$Q(t+1) = Q(t)$  when  $C_{lk}=0$

$Q(t+1) = D$  when  $C_{lk}=1$



C <sub>lk</sub>	D	Q(t + 1)
0	x	Q(t)
1	0	0
1	1	1

Characteristic table

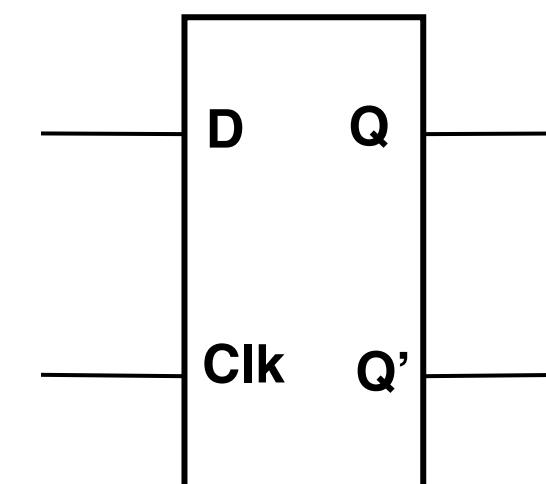


OR




Graphical symbol


# D-Latch

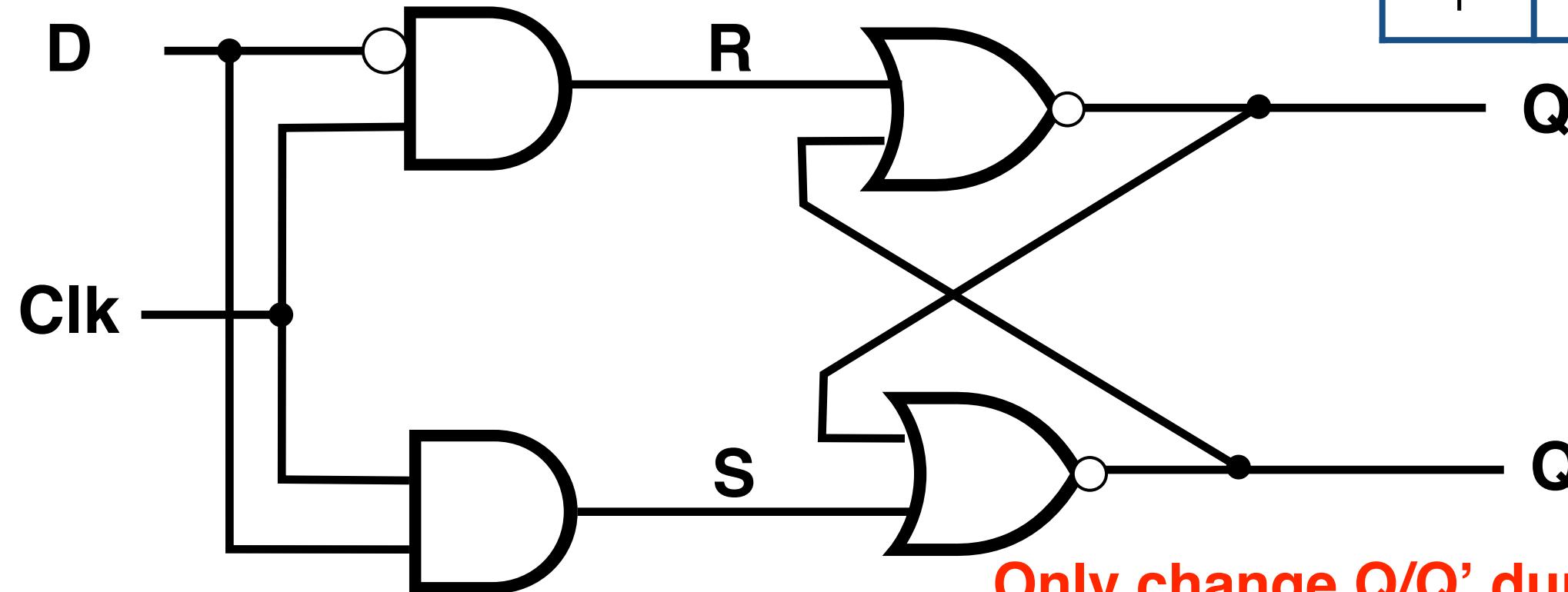


Clk	D	D'	S	R	Q(t+1)	Q(t+1)'
0	X	X'	0	0	Q(t)	Q(t)'
1	0	1	0	1	0	1
1	1	0	1	0	1	0

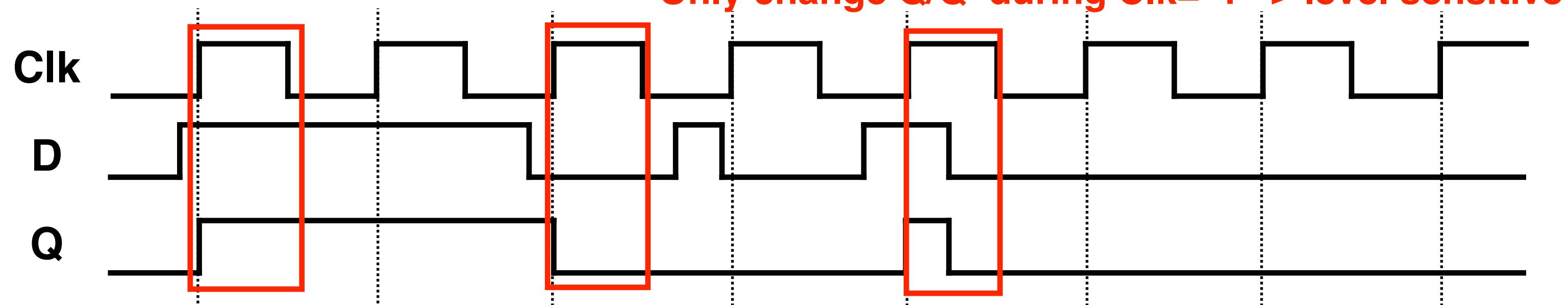

# D-Latch

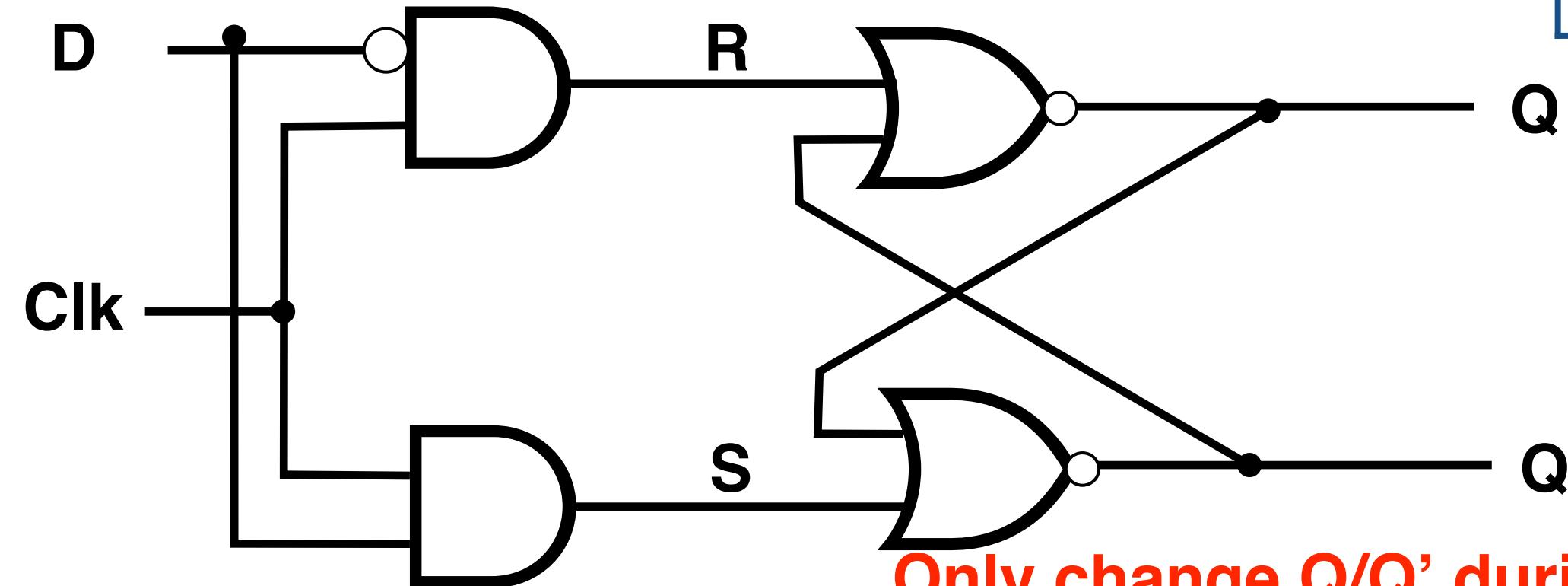

CLK	D	D'	S	R	Q	Q'
0	X	X'	0	0	Qprev	Qprev'
1	0	1	0	1	0	1
1	1	0	1	0	1	0

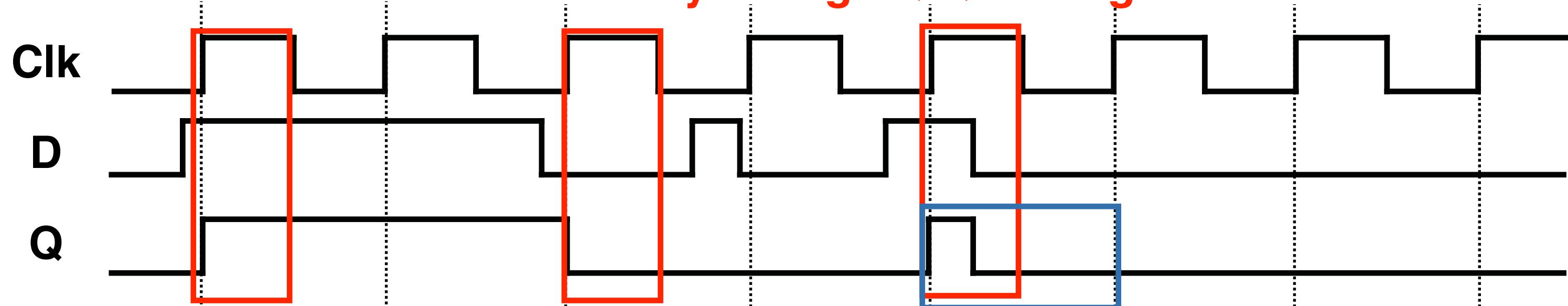


Timing diagram

Output doesn't hold for the whole cycle

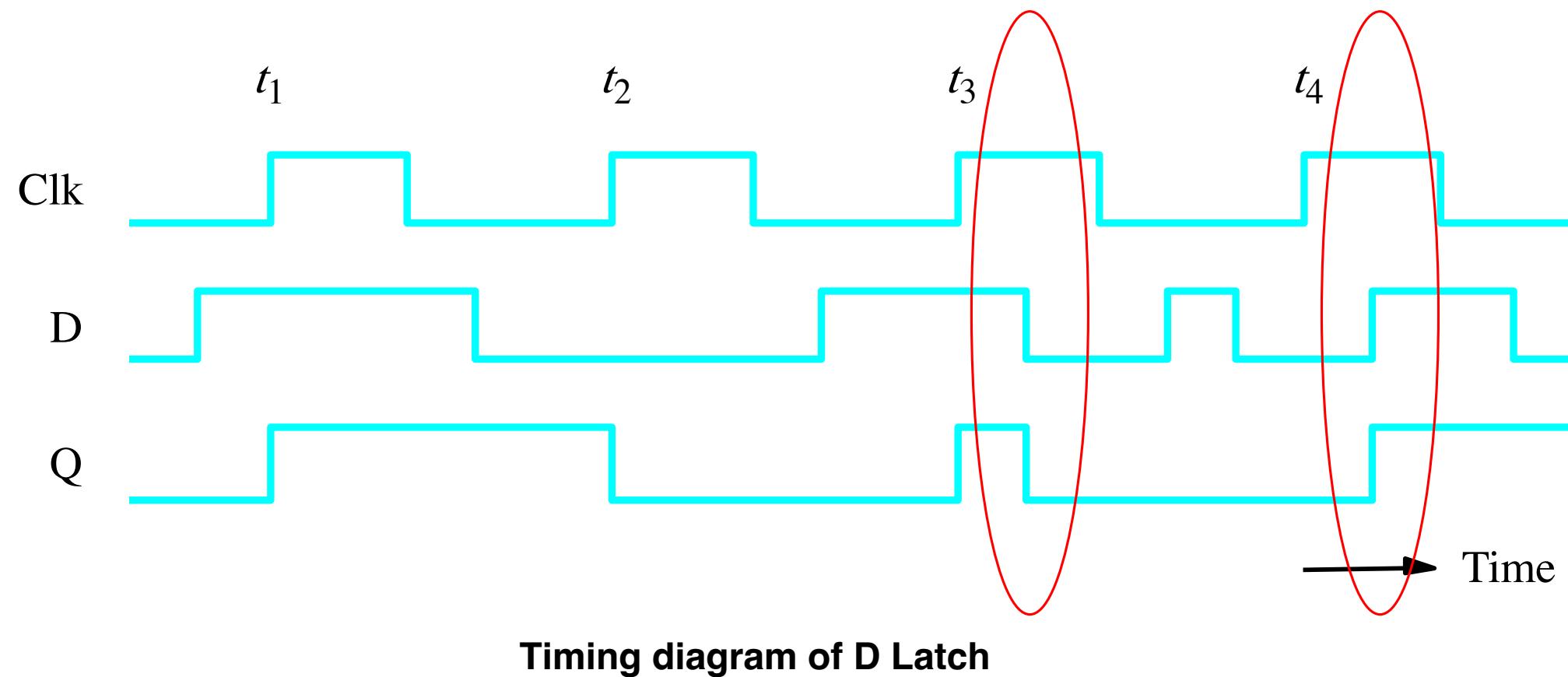
# Latches vs Flip-flops


- When the Clk control signal is 1, the output of a latch may respond to all the changes of the inputs. So latches are level sensitive.




- With flip-flops, the output state can only be changed at the active edges of the Clk control signal. So flip-flops are edge triggered.

# D flip-flop


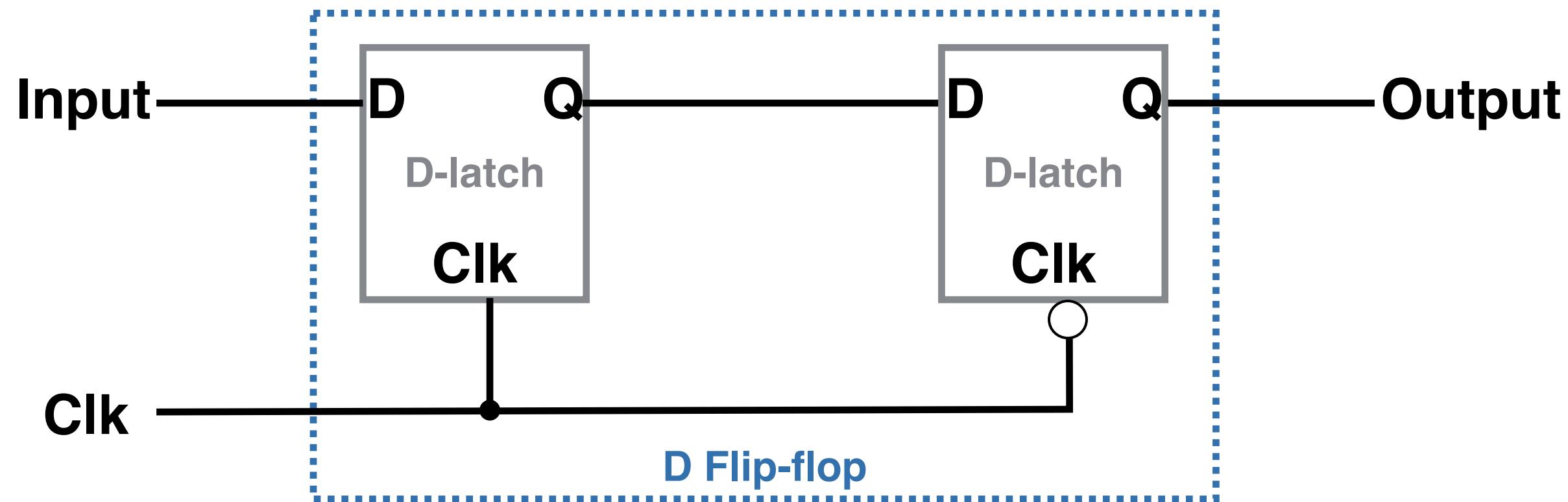


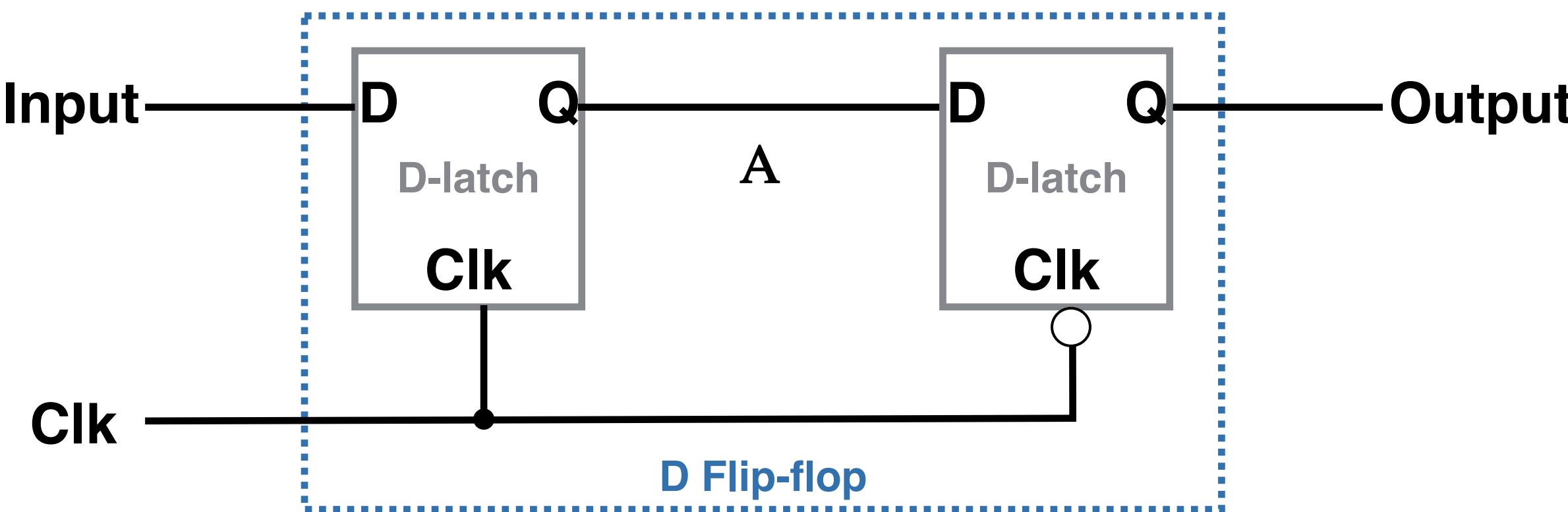


The first D-Latch

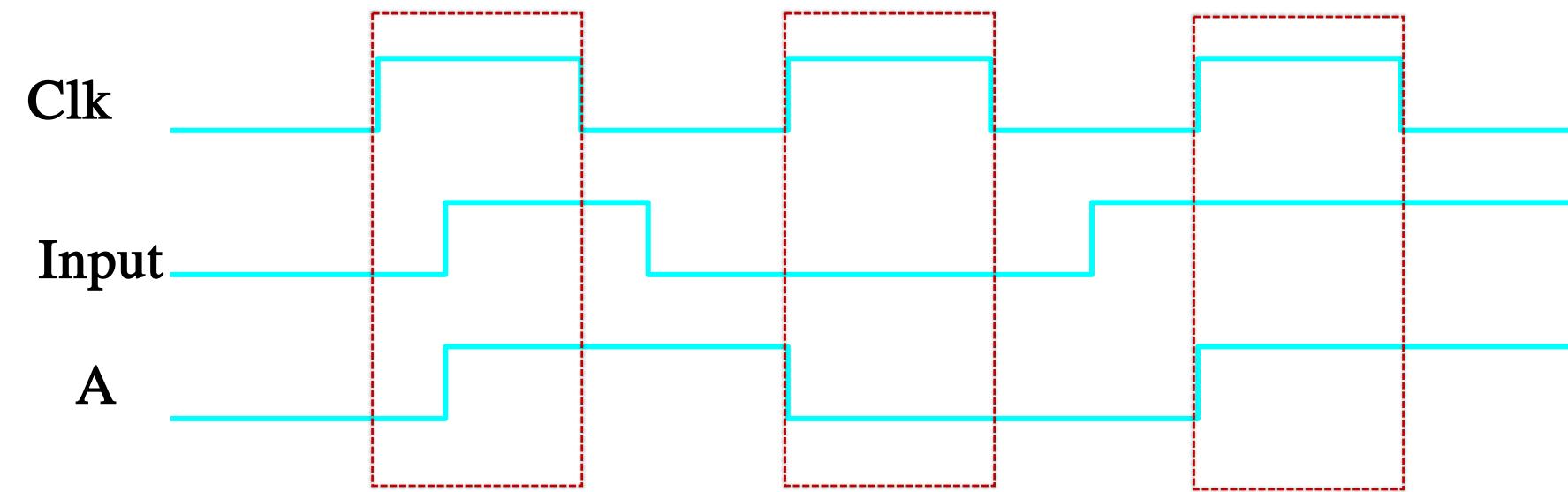

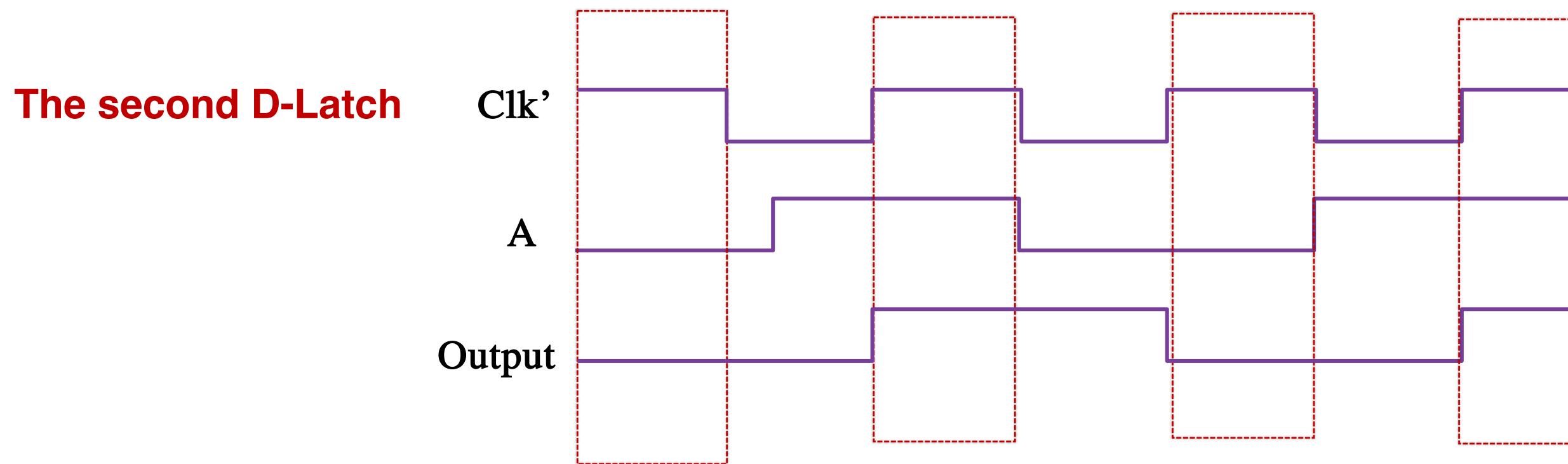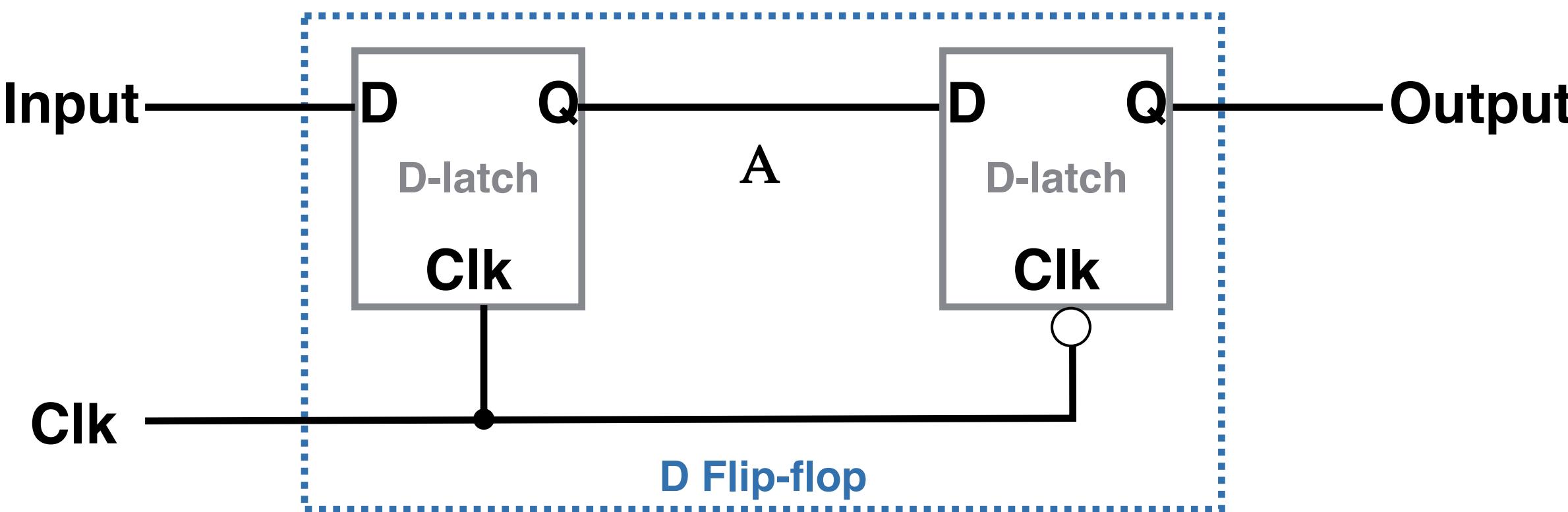
A = Input when Clk = 1  
A = Previous A when Clk = 0



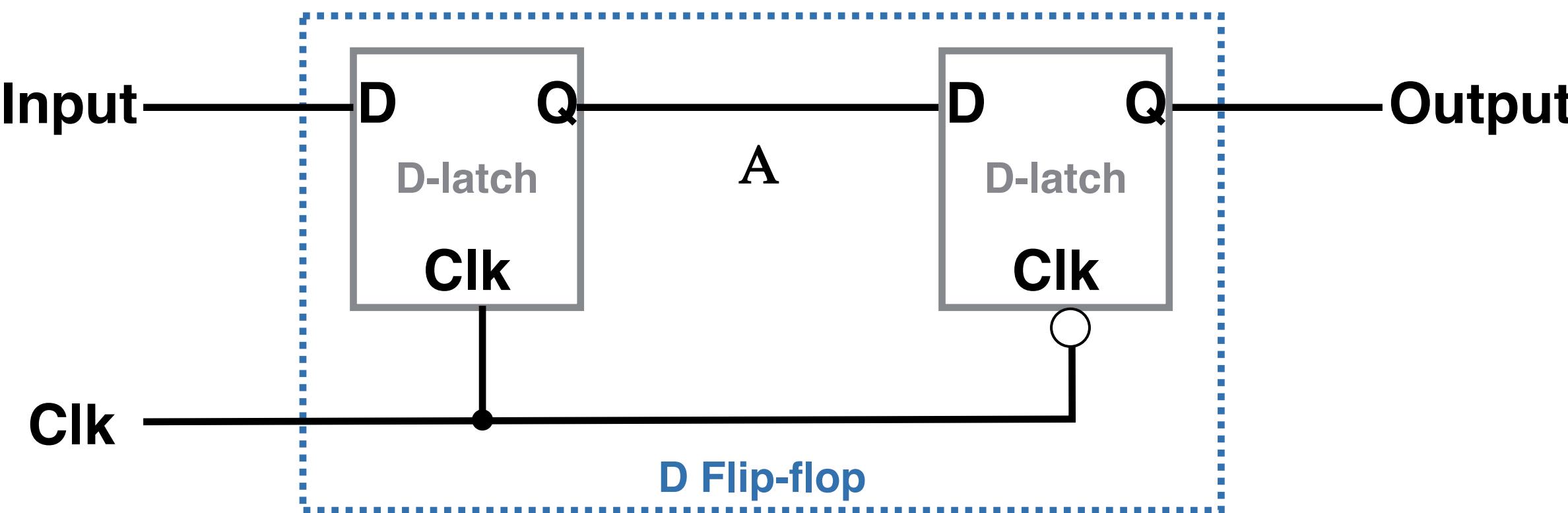Output = A when  $\text{Clk}' = 1$   
 Output = Previous Output when  $\text{Clk}' = 0$



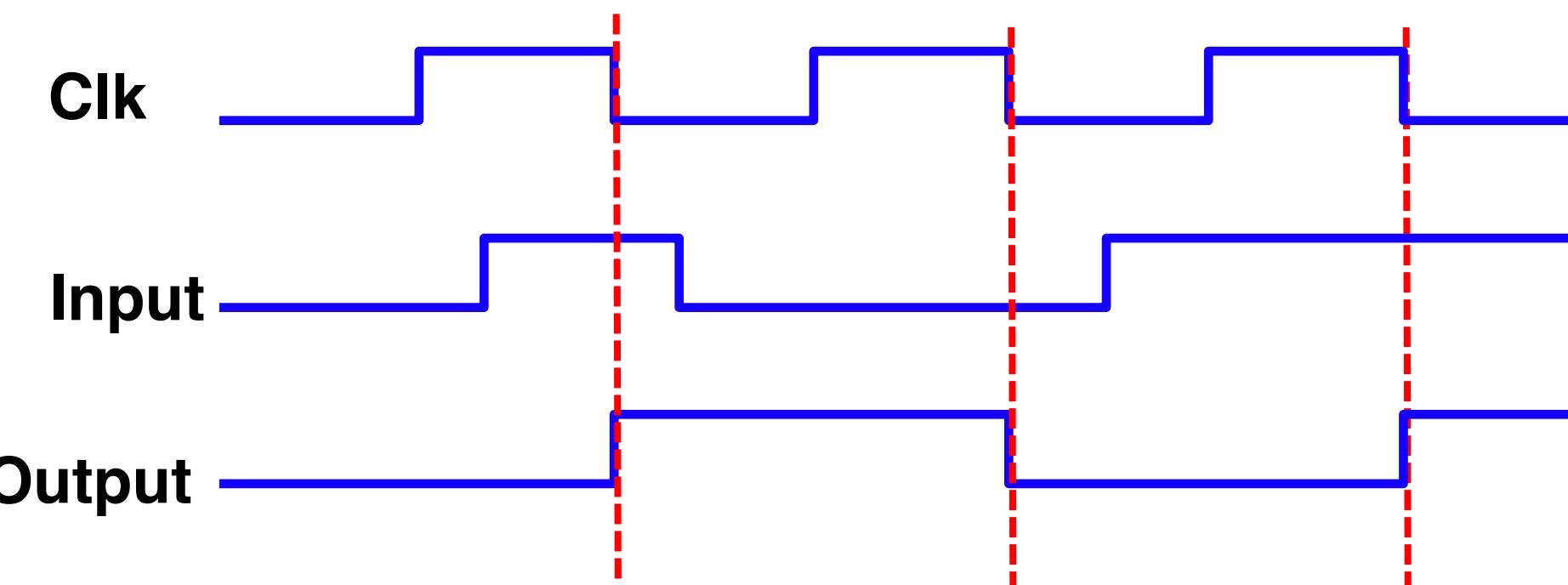**Putting the analysis of two D-Latches together**




Timing diagram


Output follows Input when Clock drops (Clk is changing from “1” to “0”).

# D Flip-Flops



Graphical symbol

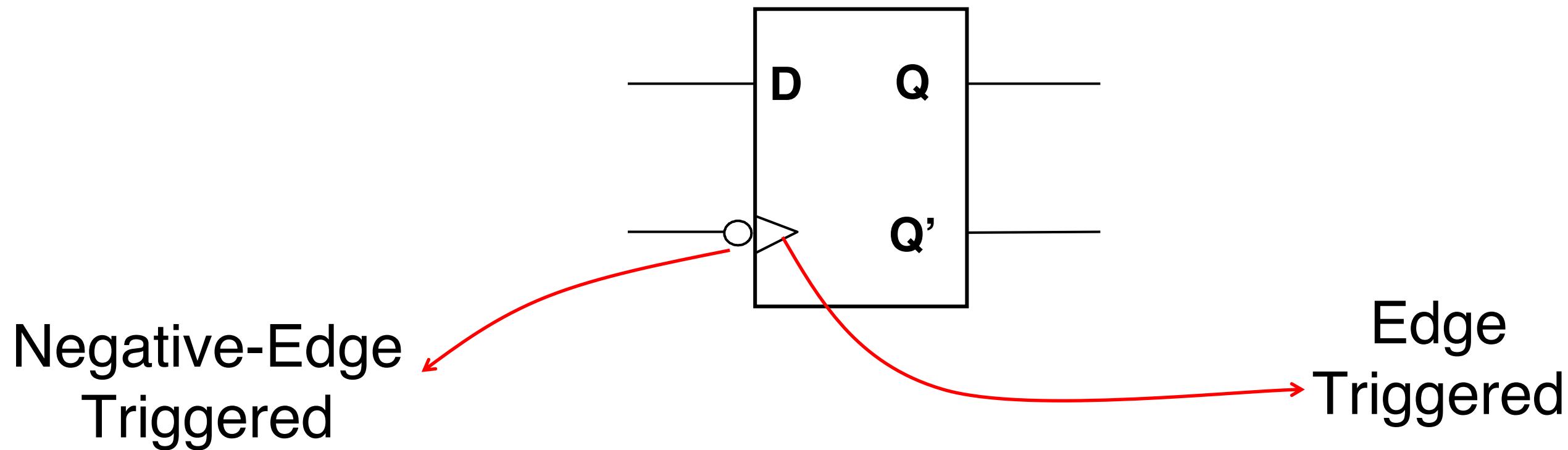

Clock signal's negative edges

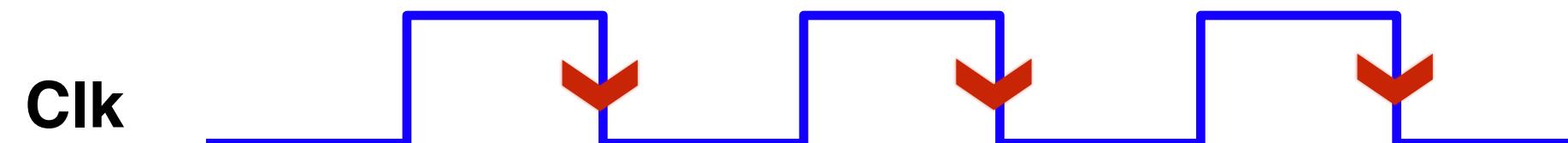


# Positive-edge-triggered D flip-flop

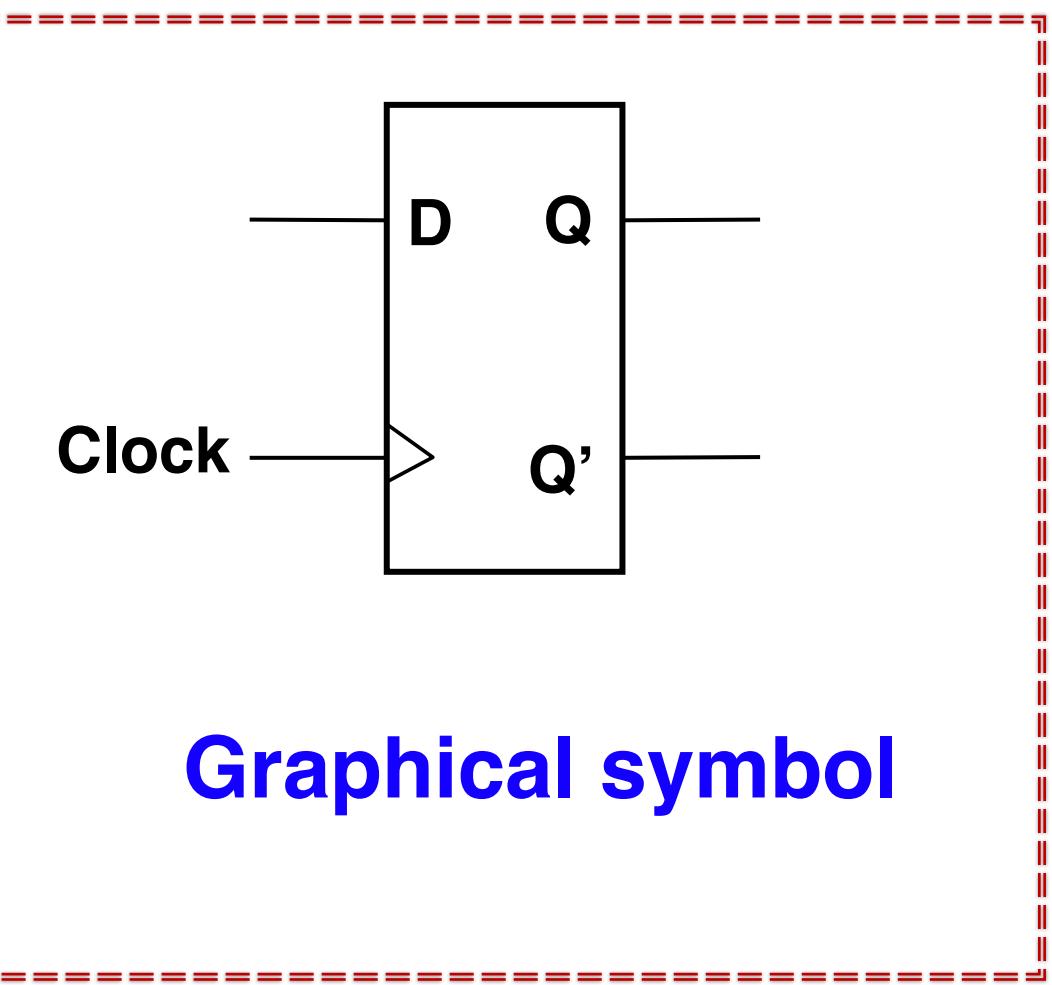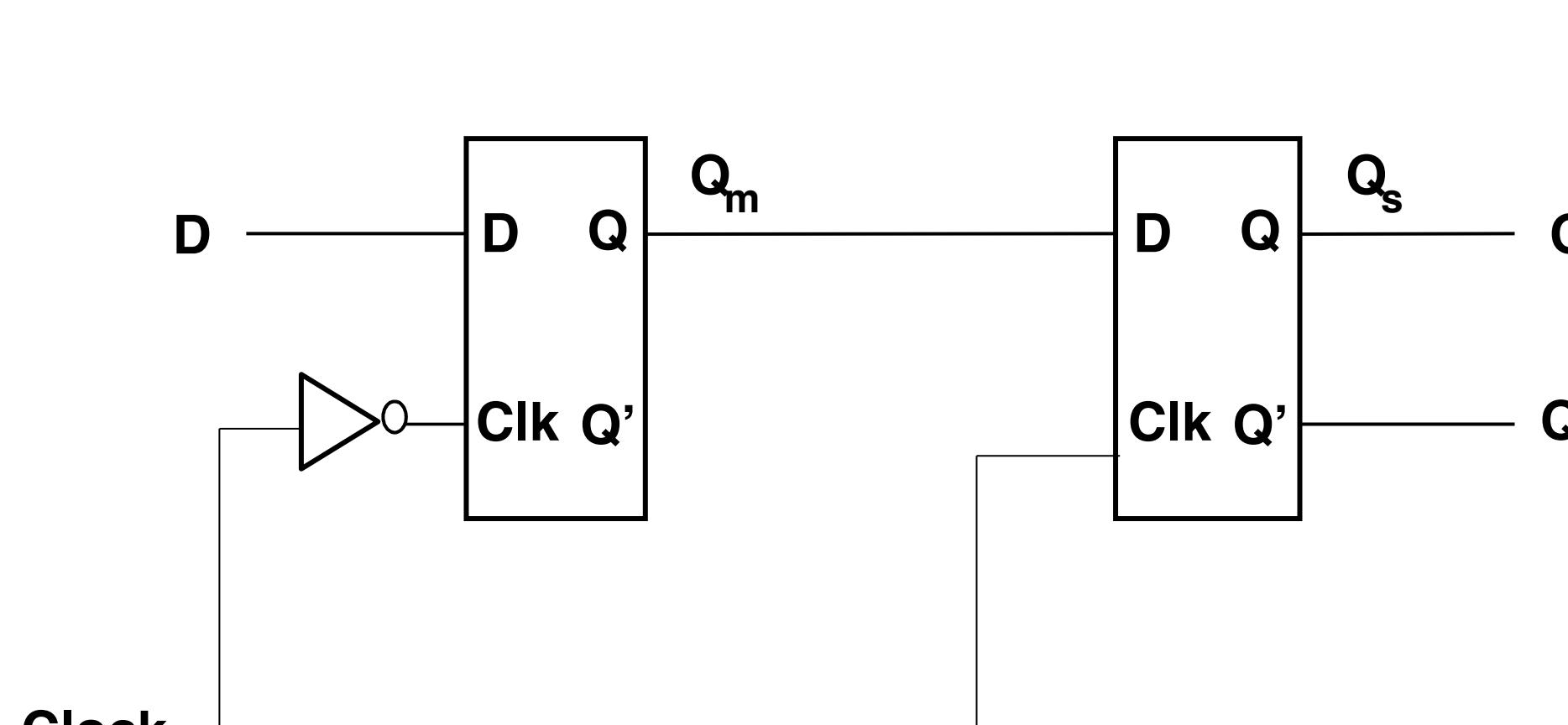

Graphical symbol

Clock signal's positive edges

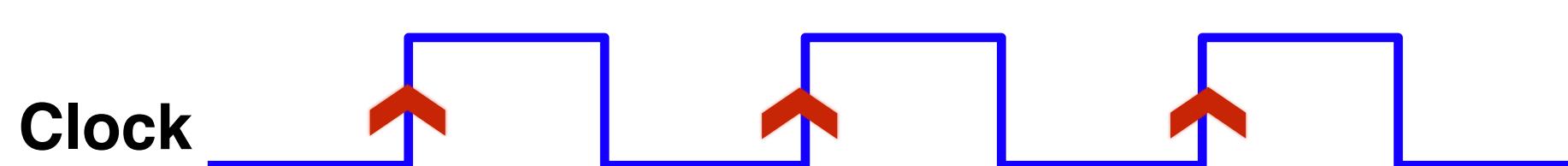


Output follows Input when Clock rises  
(Clock is changing from “0” to “1”).

# What do we need to physically implement the timer?

- 1) Logic to display the remaining time
  - use combinational logic, e.g., 7-segment display
- 2) Logic that uses the “*current state*” and “*new input(s)*” to transit to a “*new state*” and generate the “*output(s)*”
  - use combinational logic
- 3) Logic to keep track of the “*current state*”
  - need **memory**
- 4) A control signal that helps us to transit from current state to next state at the right time
  - need **clock**

# **The basic concept of “clock”**

# Clock signal

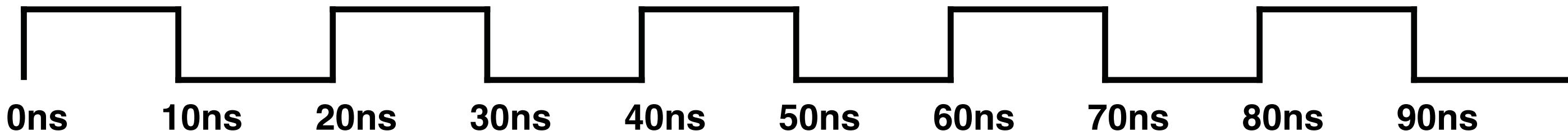

- Clock -- Pulsing signal for enabling latches; ticks like a clock
- The clock's period must be longer than the critical path which is the longest path in the circuit
- Synchronous circuit: sequential circuit with a clock
- Clock period: time between pulse starts
  - Above signal: period = 20 ns
- Clock cycle: one such time interval
  - Above signal shows 5 clock cycles
- Clock duty cycle: time clock is high
  - 50% in this case
- Clock frequency: 1/period
  - Above : freq = 1 / 20ns = 50MHz;

# Clock signal



- Regarding the above clock signal, please identify how many of the following statements are correct?
    - ① Clock period of 4ns with 250MHz frequency
    - ② Clock duty cycle 75%
    - ③ Clock period of 1ns with 1GHz frequency
    - ④ The above contains two complete clock cycles.
- A. 0  
B. 1  
C. 2  
D. 3  
E. 4


# Clock signal








- Regarding the above clock signal, please identify how many of the following statements are correct?
    - ① Clock period of 4ns with 250MHz frequency
    - ② Clock duty cycle 75%
    - ③ Clock period of 1ns with 1GHz frequency
    - ④ The above contains two complete clock cycles.
- A. 0
- B. 1
- C. 2
- D. 3
- E. 4

**Let's learn how to design  
sequential circuits!**
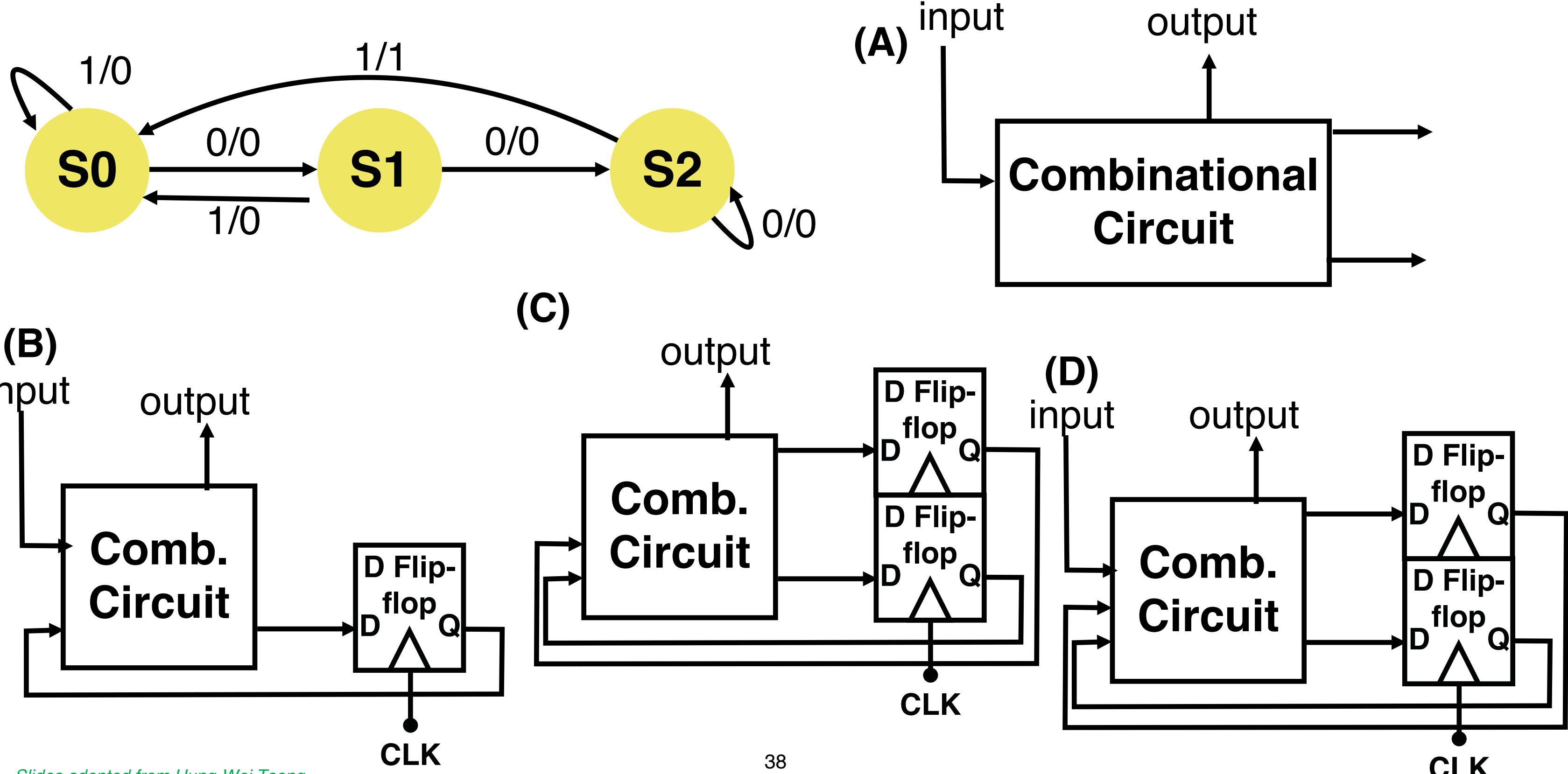
# Which is the most likely circuit realization of Life on Mars


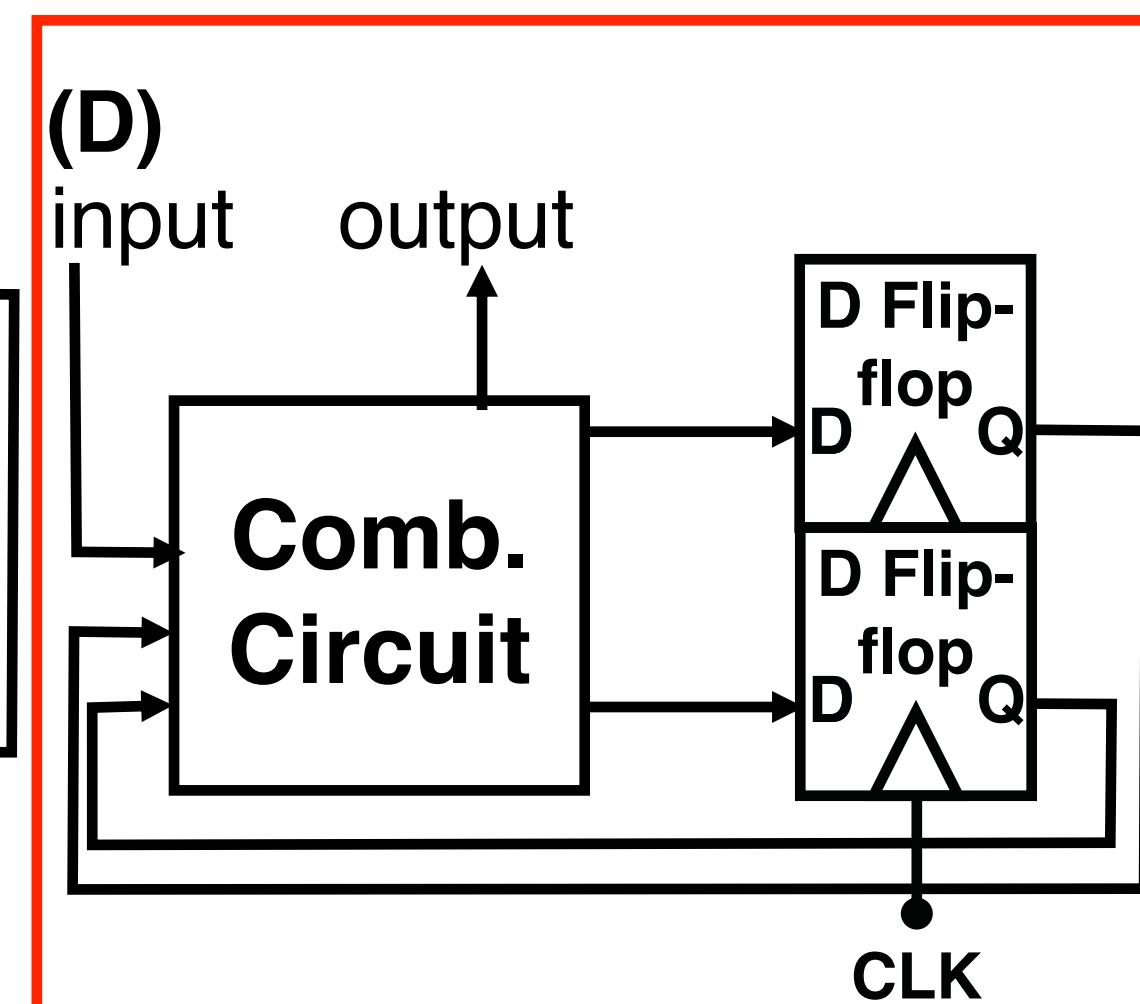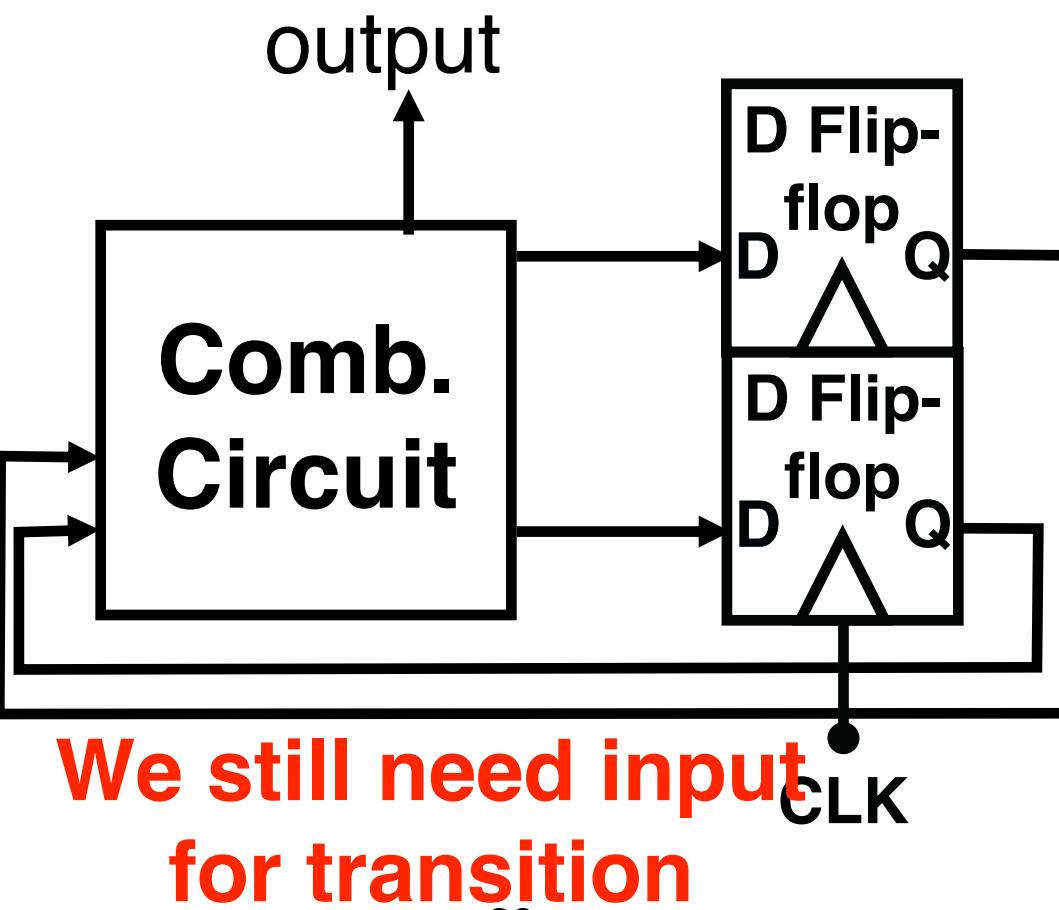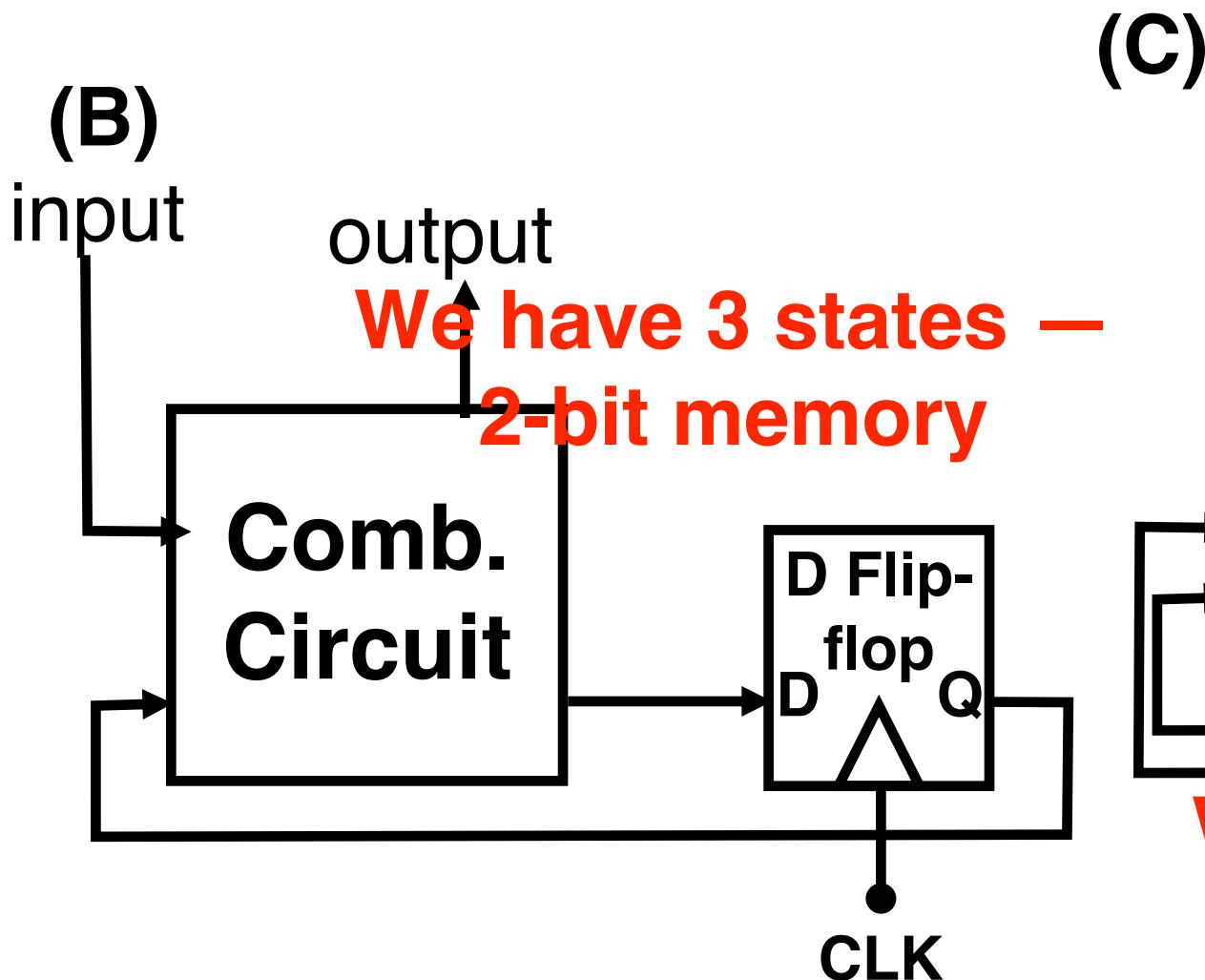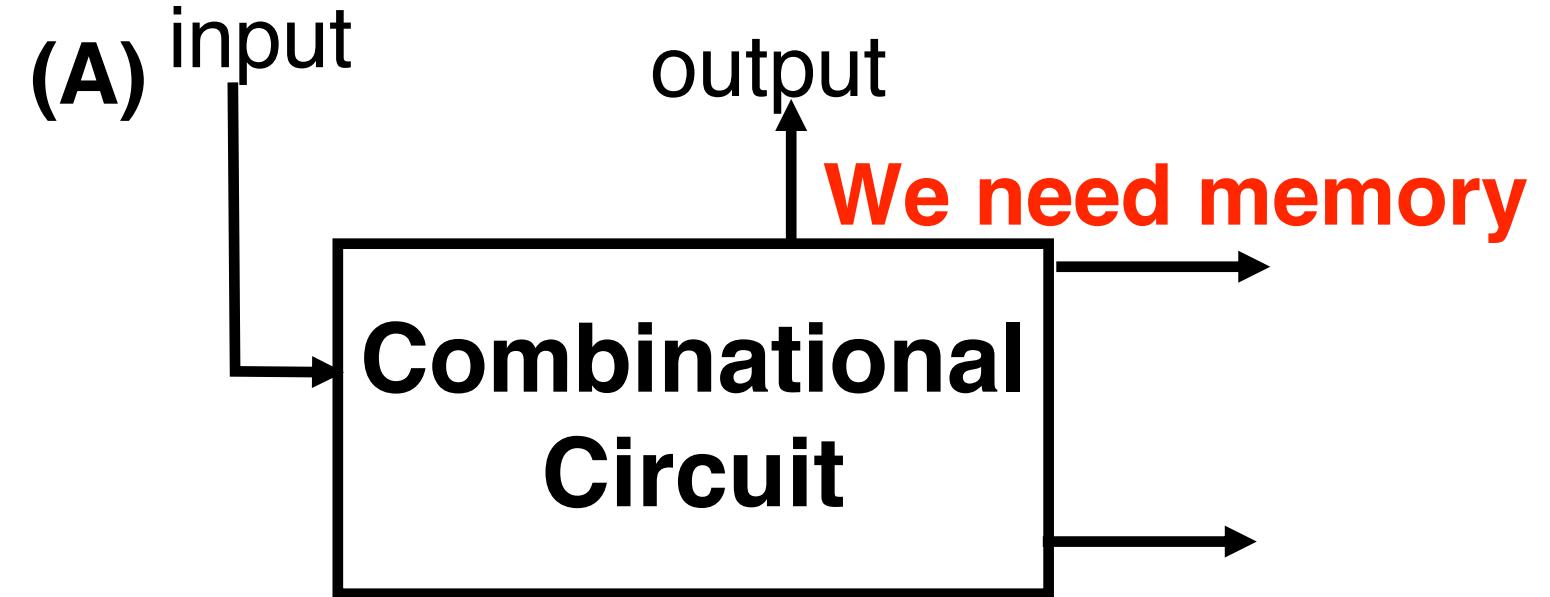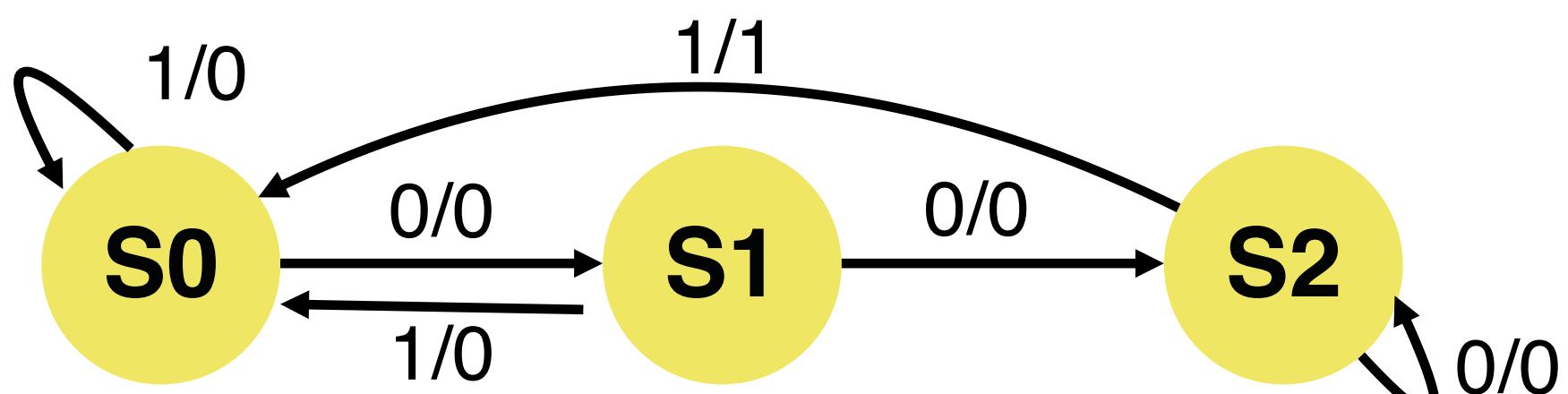
# Which is the most likely circuit realization of Life on Mars



# Sequential Circuit Design Flow

**Step 1: Create FSM (state diagram or state table)**



**Step 2: Reduce states if necessary (merging equivalent states)**



**Step 3: State assignment (use binary number to represent each state)**



**Step 4: Excitation table or Transition table (truth table for outputs and next state)**



**Step 5: Excitation equation and output equation  
(K-Map or Boolean algebra for equation simplification)**




**Step 6: Design the circuit using Flip-flops (based on Step 3)  
and combinational logic (based on Step 5)**

# Life on Mars

Step 1: Create FSM (state diagram or state table)


State Diagram

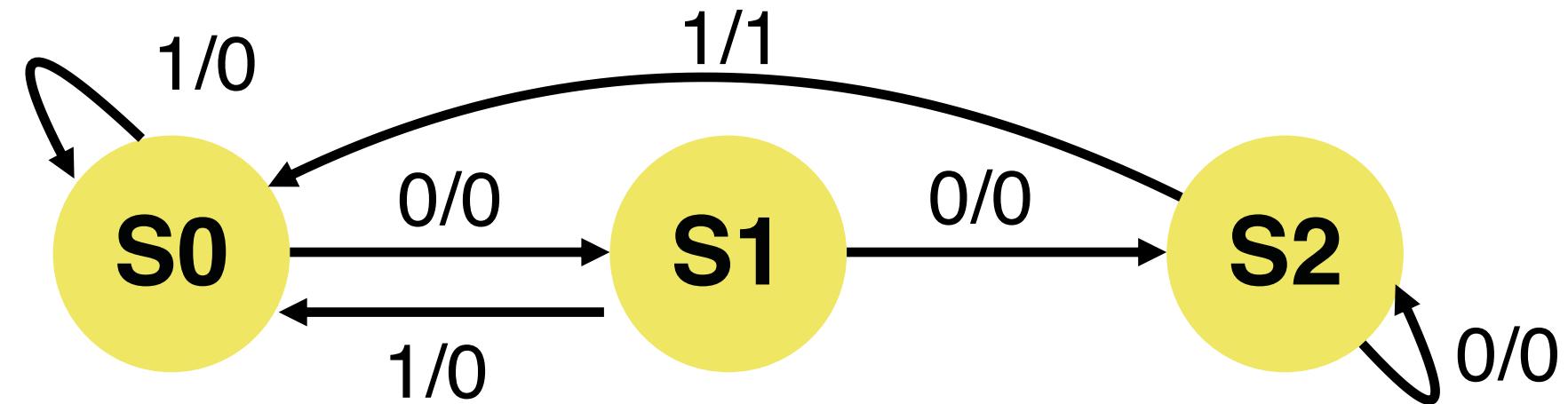

Current State	Next State, Output	
	Input	
S0	0	1
S0	S1, 0	S0, 0
S1	S2, 0	S0, 0
S2	S2, 0	S0, 1



State Table

Overview of the circuit

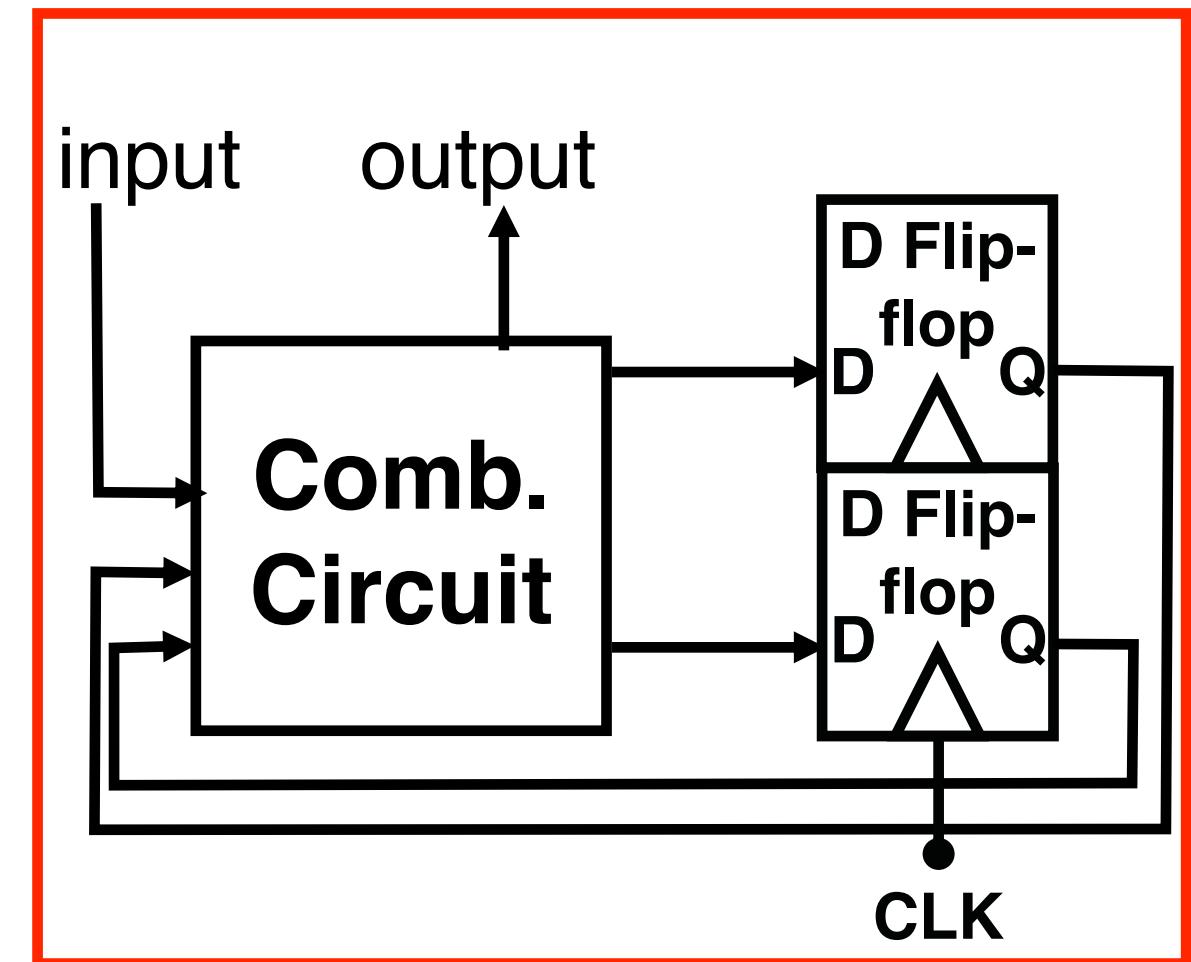

# Life on Mars

## State Diagram

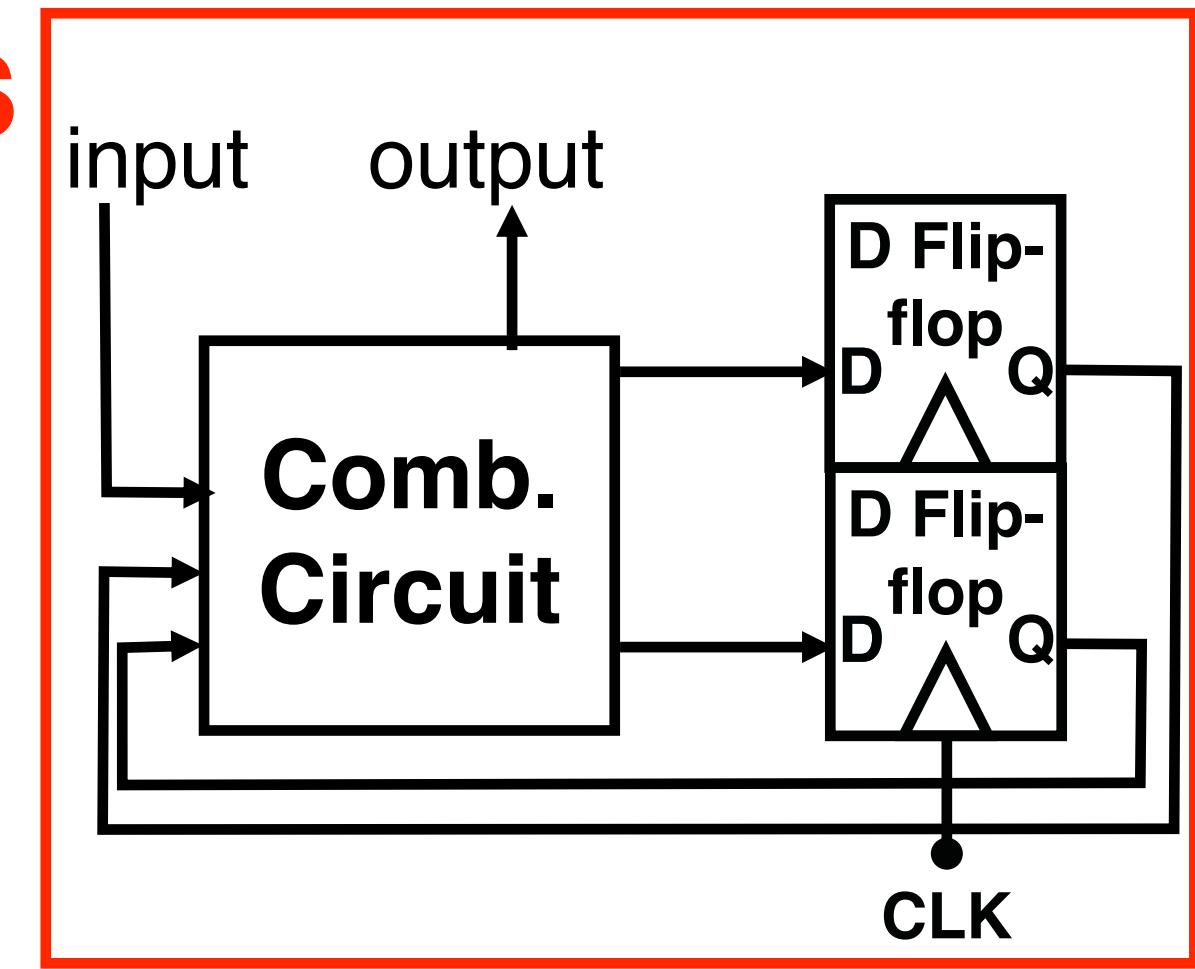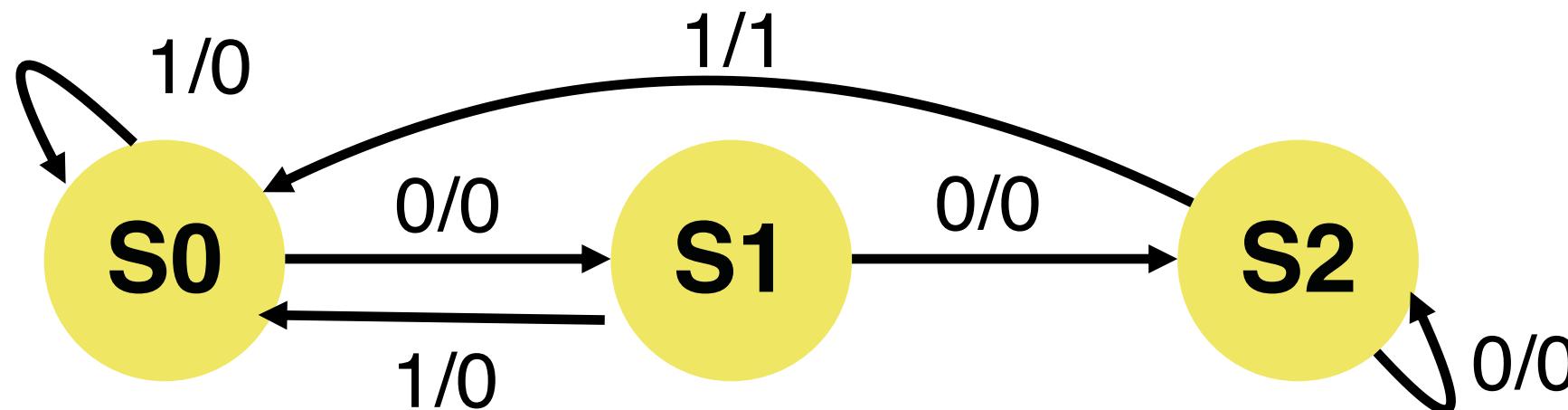

Current State	Next State, Output	
	Input	
	0	1
S0	S1, 0	S0, 0
S1	S2, 0	S0, 0
S2	S2, 0	S0, 1

State Table



Step 3: State assignment (use binary number to represent each state)

## State Assignment

S0	00
S1	01
S2	10

# Life on Mars

**State Diagram**

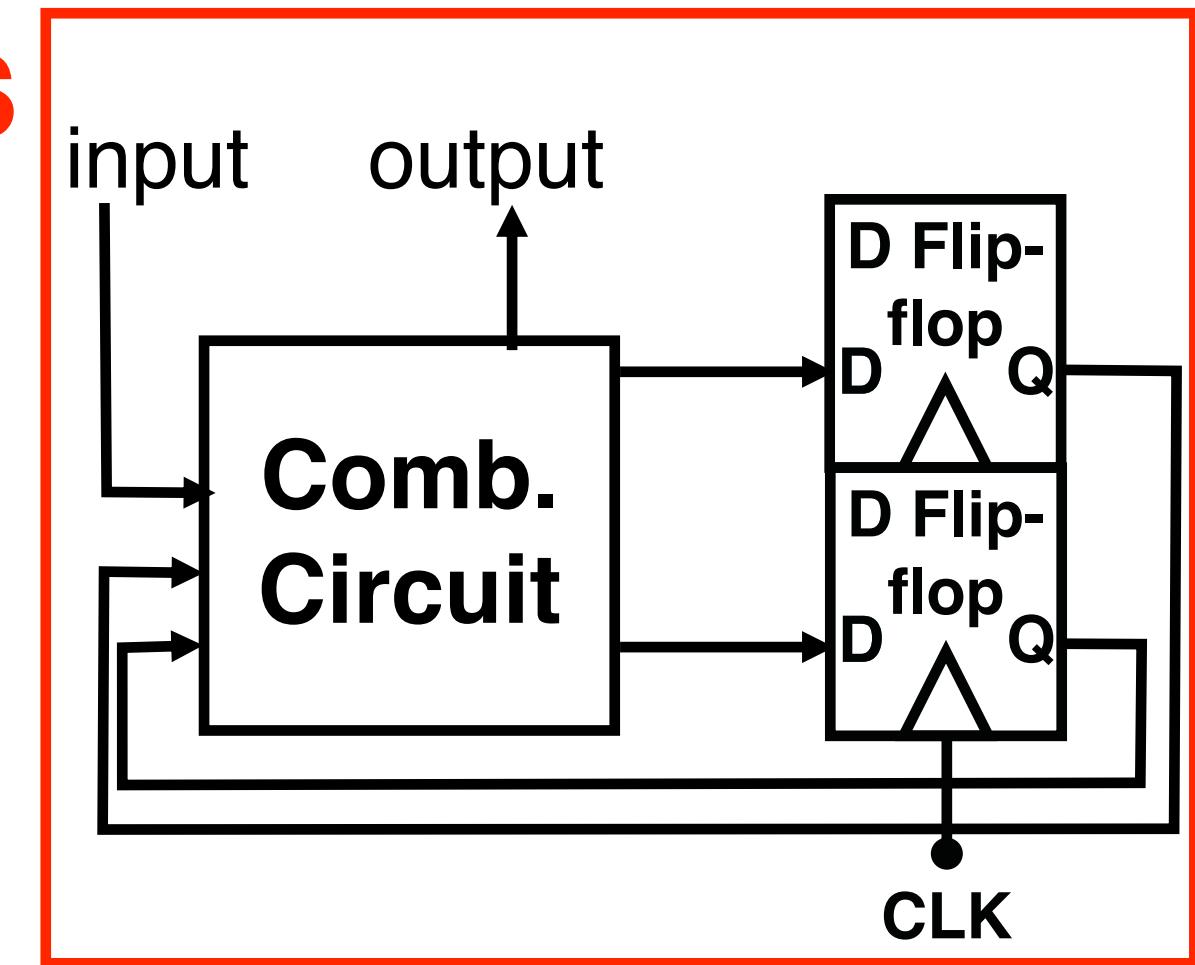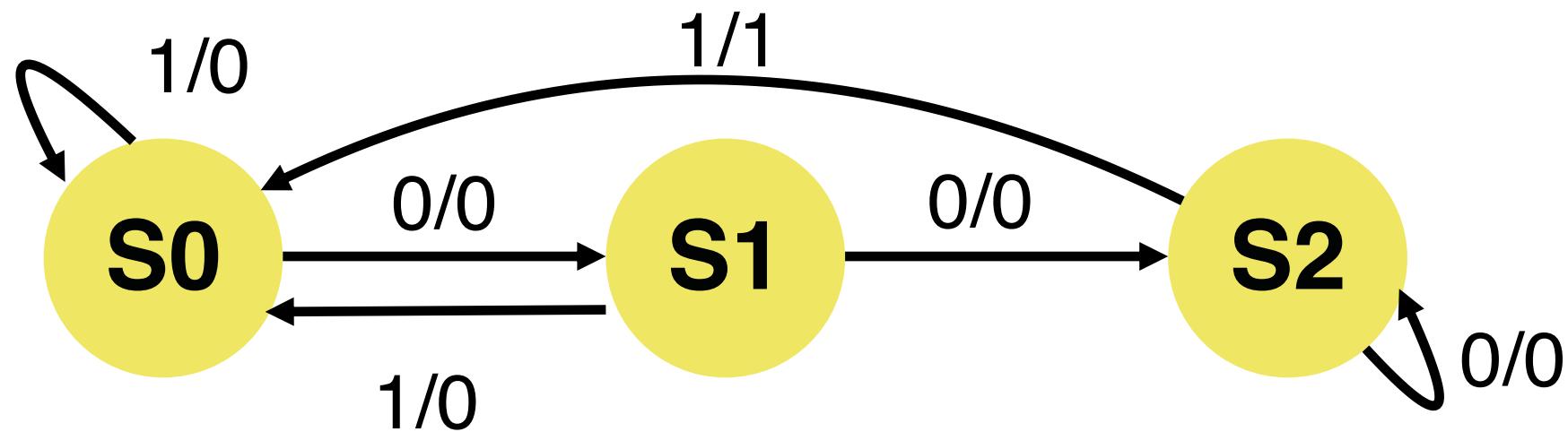

Current State	Next State, Output	
	Input	
	0	1
S0	S1, 0	S0, 0
S1	S2, 0	S0, 0
S2	S2, 0	S0, 1

**State Table**

**State Assignment**

S0	00
S1	01
S2	10


**State Truth Table**

State\Input	0	1
00	01, 0	00, 0
01	10, 0	00, 0
10	10, 0	00, 1

# Excitation Table

- Excitation table is basically the truth table describing the combinational circuit that provides inputs for the flip-flops in the sequential circuit. How many rows are there in the excitation table of Life on Mars?

- A. 2
- B. 3
- C. 4
- D. 8
- E. 32

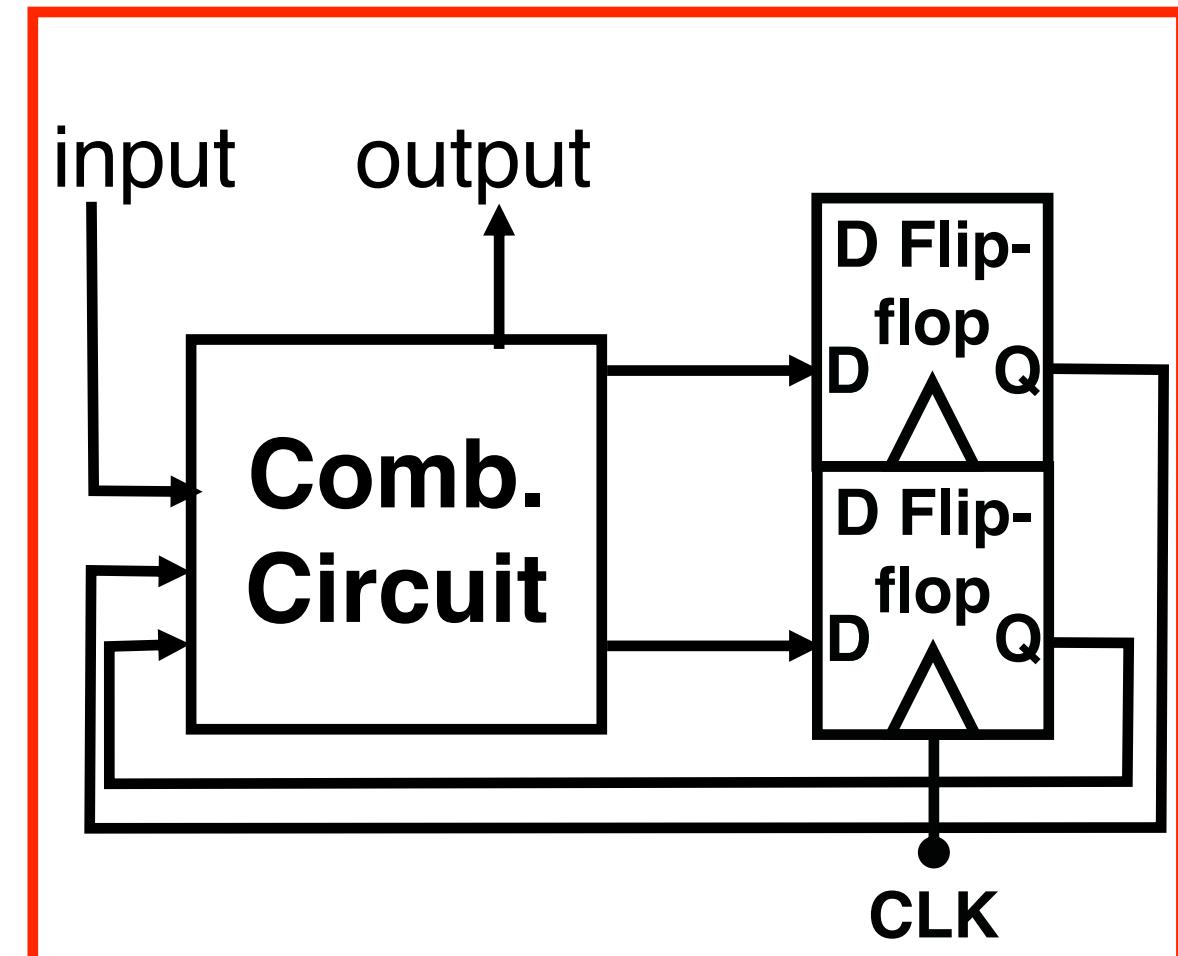

# Excitation Table

- Excitation table is basically the truth table describing the combinational circuit that provides inputs for the flip-flops in the sequential circuit. How many rows are there in the excitation table of Life on Mars?


A. 2

B. 3

C. 4

D. 8

E. 32

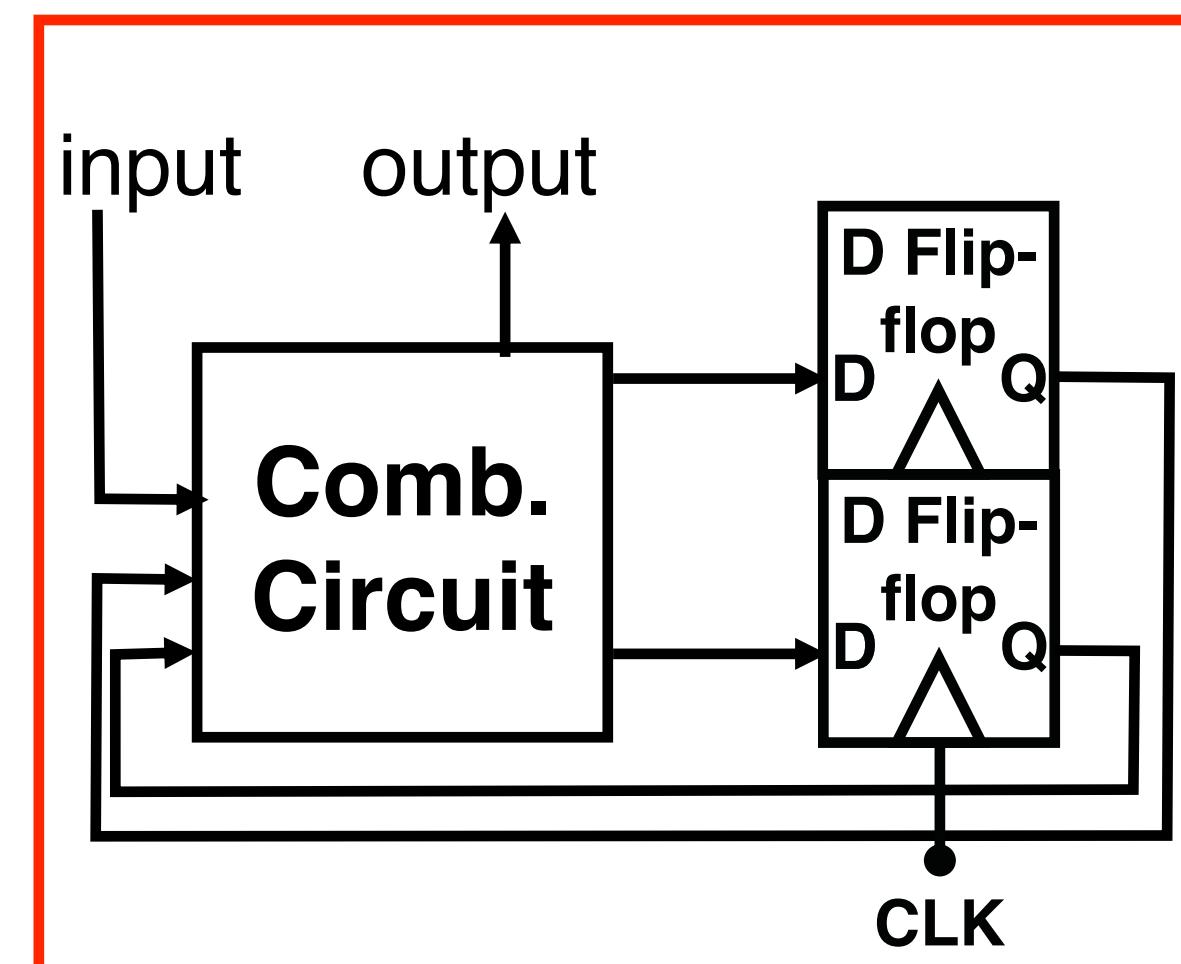

## State Truth Table



State\Input	0	1
00	01, 0	00, 0
01	10, 0	00, 0
10	10, 0	00, 1

## Excitation Table

NextStateOutput StateInput	D <sub>1</sub>	D <sub>0</sub>	y
000	0	1	0
001	0	0	0
010	1	0	0
011	0	0	0
100	1	0	0
101	0	0	1
110	X	X	X
111	X	X	X
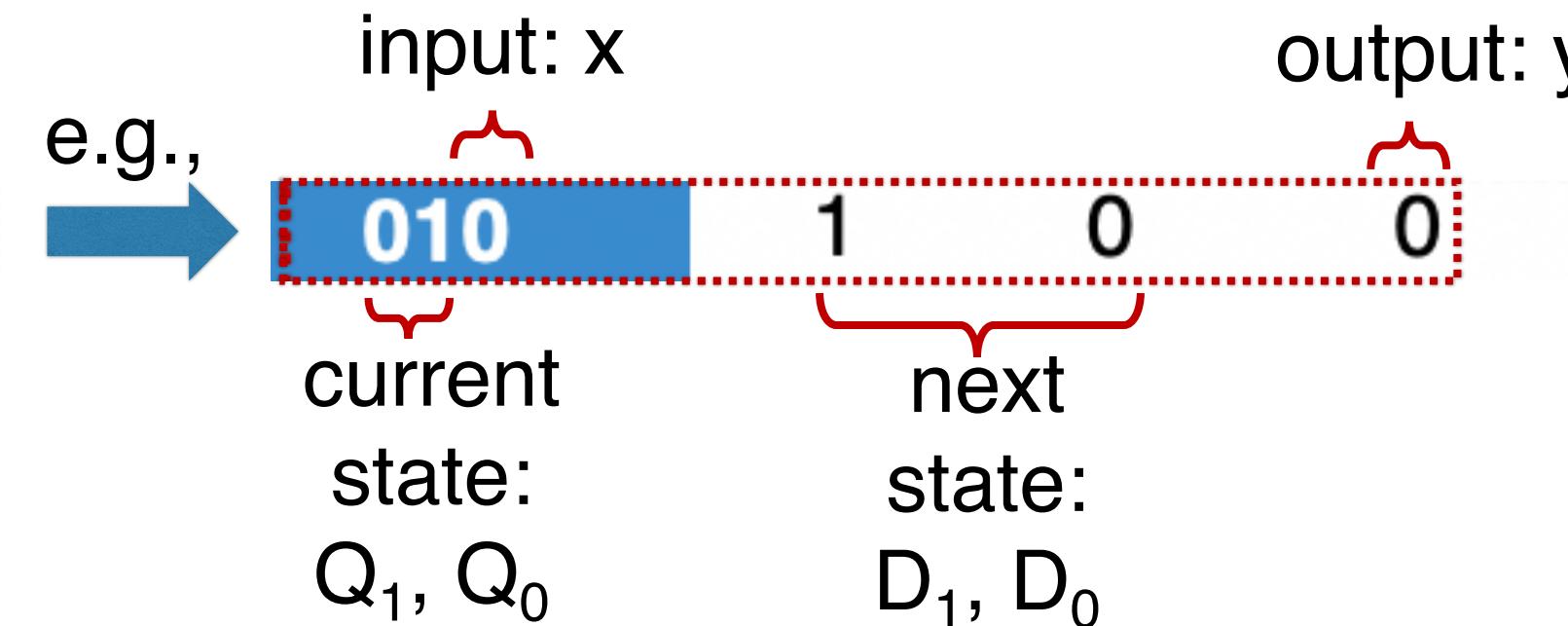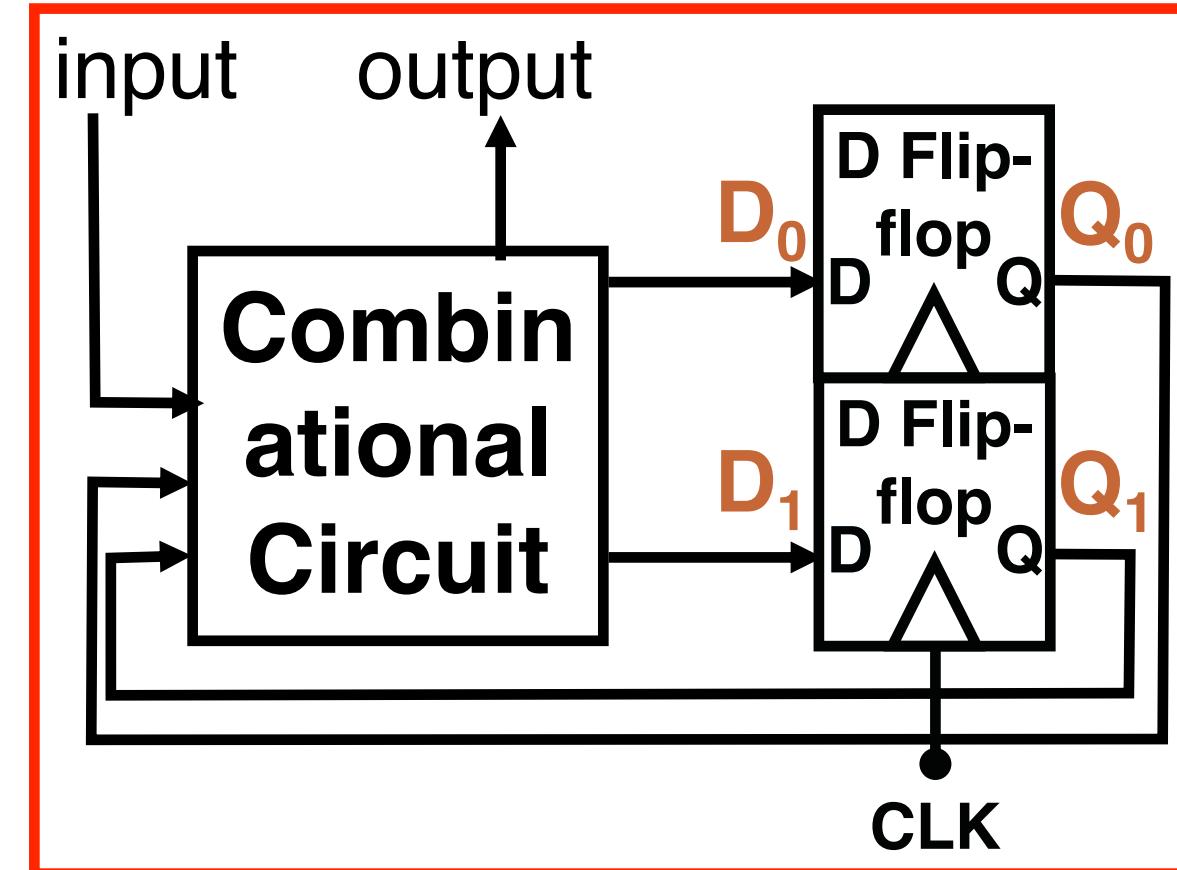
# Life on Mars

Step 4: Excitation table or Transition table (truth table for outputs and next state)



## State Truth Table


State\Input	0	1
00	01, 0	00, 0
01	10, 0	00, 0
10	10, 0	00, 1

## Excitation Table

NextState\Output	D <sub>1</sub>	D <sub>0</sub>	y
State\Input			
000	0	1	0
001	0	0	0
010	1	0	0
011	0	0	0
100	1	0	0
101	0	0	1
110	X	X	X
111	X	X	X
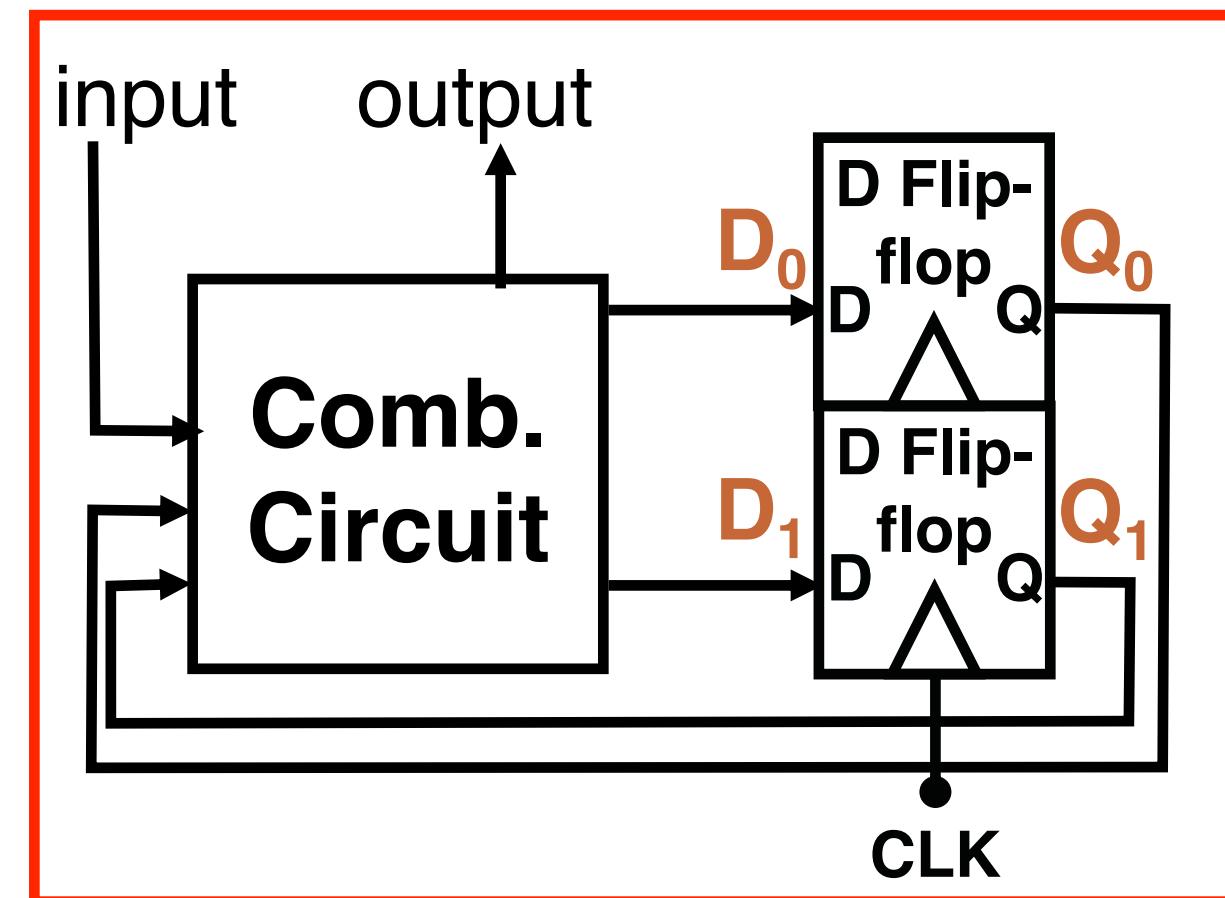
# Life on Mars

Step 5: Excitation equation  
and output equation  
(K-Map or Boolean algebra  
for equation simplification)



K-Map – D<sub>1</sub>

	0,0	0,1	1,1	1,0
0	0	1	X	1
1	0	0	X	0

K-Map – D<sub>0</sub>

	0,0	0,1	1,1	1,0
0	1	0	X	0
1	0	0	X	0

K-Map – y


	0,0	0,1	1,1	1,0
0	0	0	X	0
1	0	0	X	1

**Step 5: Excitation equation and output equation (K-Map or Boolean algebra for equation simplification)**

**Excitation Table**

NextStateOut StateInput	D <sub>1</sub>	D <sub>0</sub>	y
000	0	1	0
001	0	0	0
010	1	0	0
011	0	0	0
100	1	0	0
101	0	0	1
110	X	X	X
111	X	X	X

# K-Map for D<sub>1</sub>

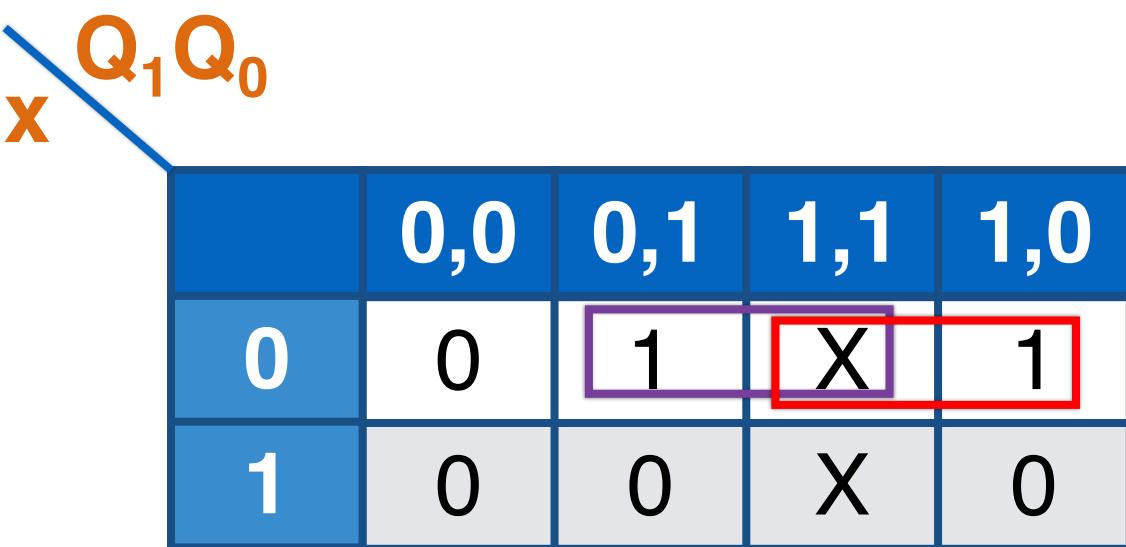


Excitation equation:  $D_1 = x'Q_0 + x'Q_1$

**Step 5: Excitation equation and output equation (K-Map or Boolean algebra for equation simplification)**

# K-Map for $D_0$

**Excitation Table**

NextStateOutput StateInput	$D_1$	$D_0$	y
000	0	1	0
001	0	0	0
010	1	0	0
011	0	0	0
100	1	0	0
101	0	0	1
110	X	X	X
111	X	X	X

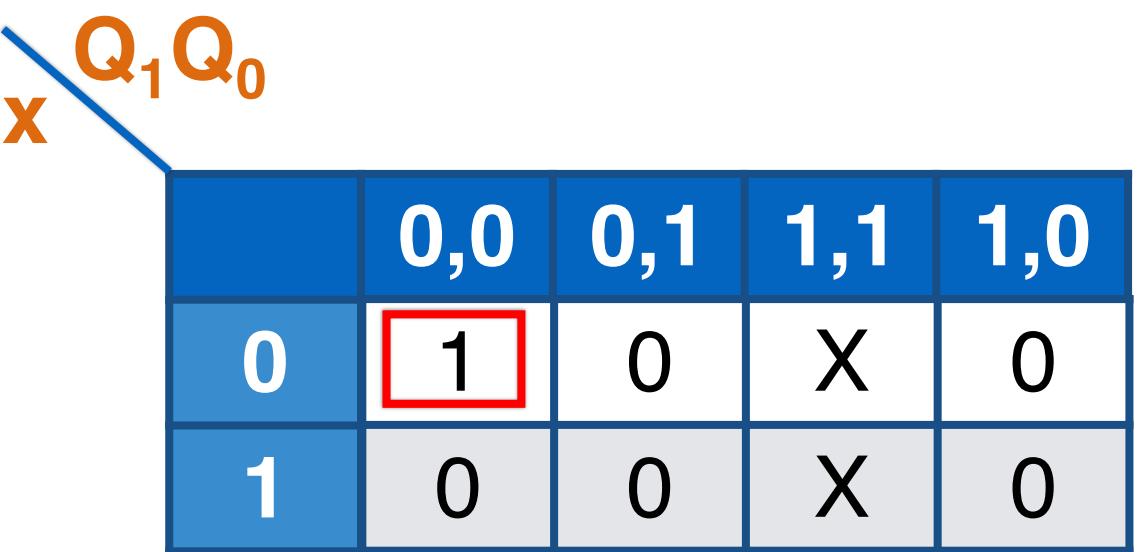


**Excitation equation:**  $D_0 = Q_0'Q_1'x'$

**Step 5: Excitation equation and output equation (K-Map or Boolean algebra for equation simplification)**

# K-Map for y

**Excitation Table**

NextStateOutput StateInput	D <sub>1</sub>	D <sub>0</sub>	y
000	0	1	0
001	0	0	0
010	1	0	0
011	0	0	0
100	1	0	0
101	0	0	1
110	X	X	X
111	X	X	X

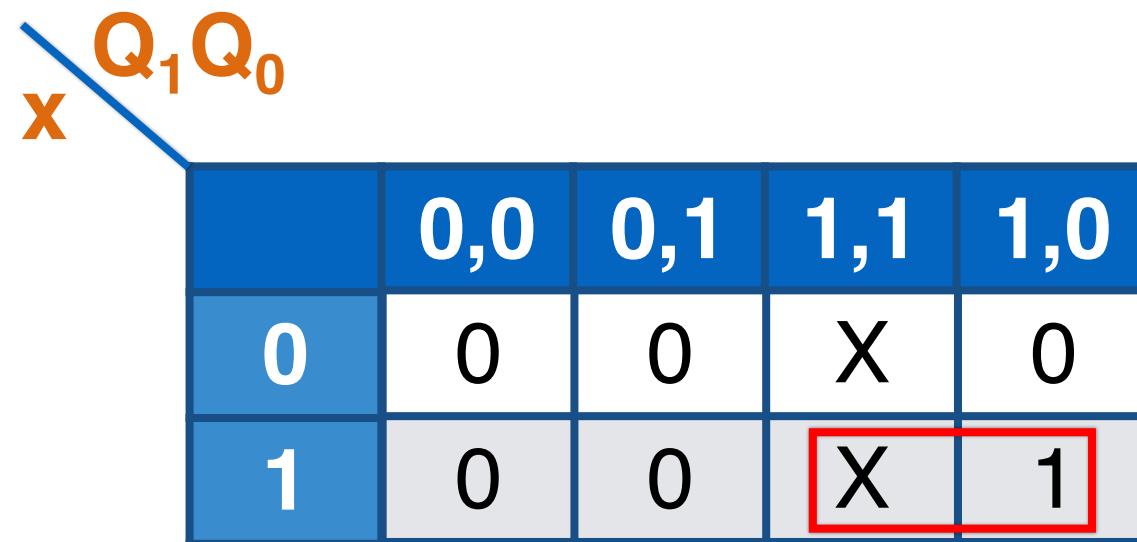

**Output equation:**  $y = Q_1 x$

# Summary

## State Truth Table

State\Input	0	1
00	01, 0	00, 0
01	10, 0	00, 0
10	10, 0	00, 1

## Excitation Table

NextStateOutput State\Input	D <sub>1</sub>	D <sub>0</sub>	y
000	0	1	0
001	0	0	0
010	1	0	0
011	0	0	0
100	1	0	0
101	0	0	1
110	x	x	x
111	x	x	x

K-Map – D<sub>1</sub>

	0,0	0,1	1,1	1,0
0	0	1	x	1
1	0	0	x	0

$$D_1 = x'Q_0 + x'Q_1$$

K-Map – D<sub>0</sub>

	0,0	0,1	1,1	1,0
0	1	0	x	0
1	0	0	x	0


$$D_0 = Q_0'Q_1'x'$$

K-Map – y

	0,0	0,1	1,1	1,0
0	0	0	x	0
1	0	0	x	1

$$y = Q_1x$$

input      output


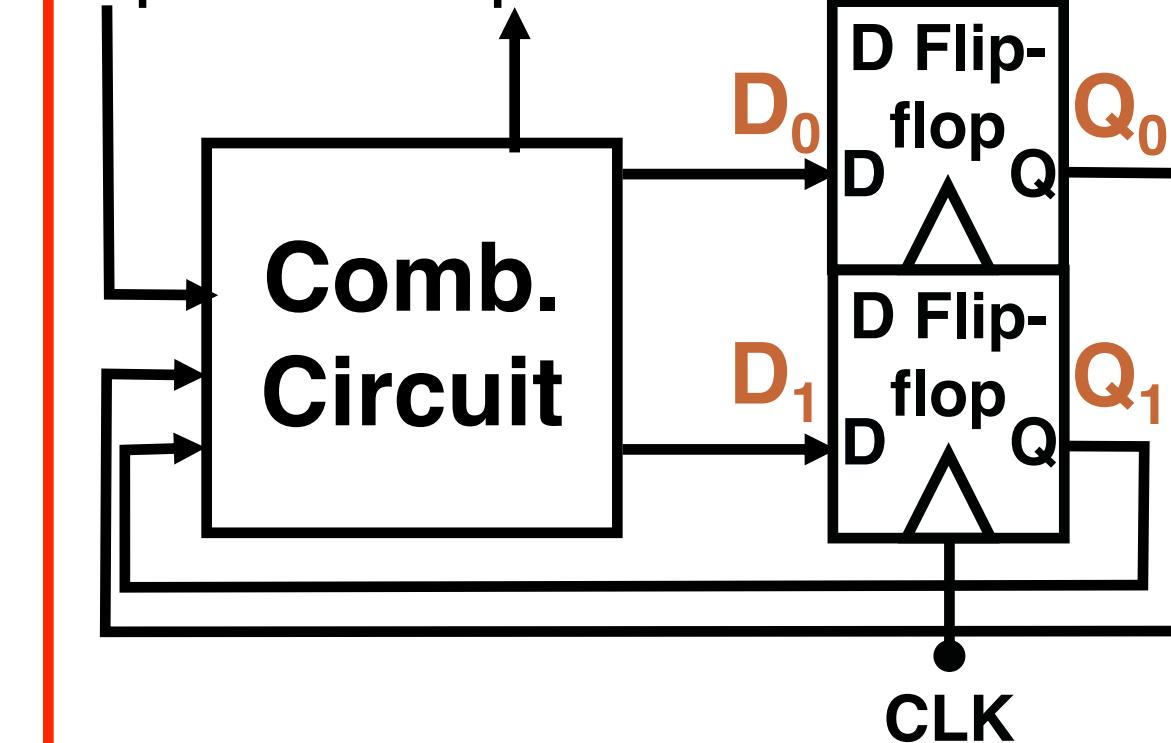


# Circuit – Life on Mars

$$D_1 = x'Q_0 + x'Q_1$$

$$D_0 = Q_0'Q_1'x'$$

$$y = Q_1x$$

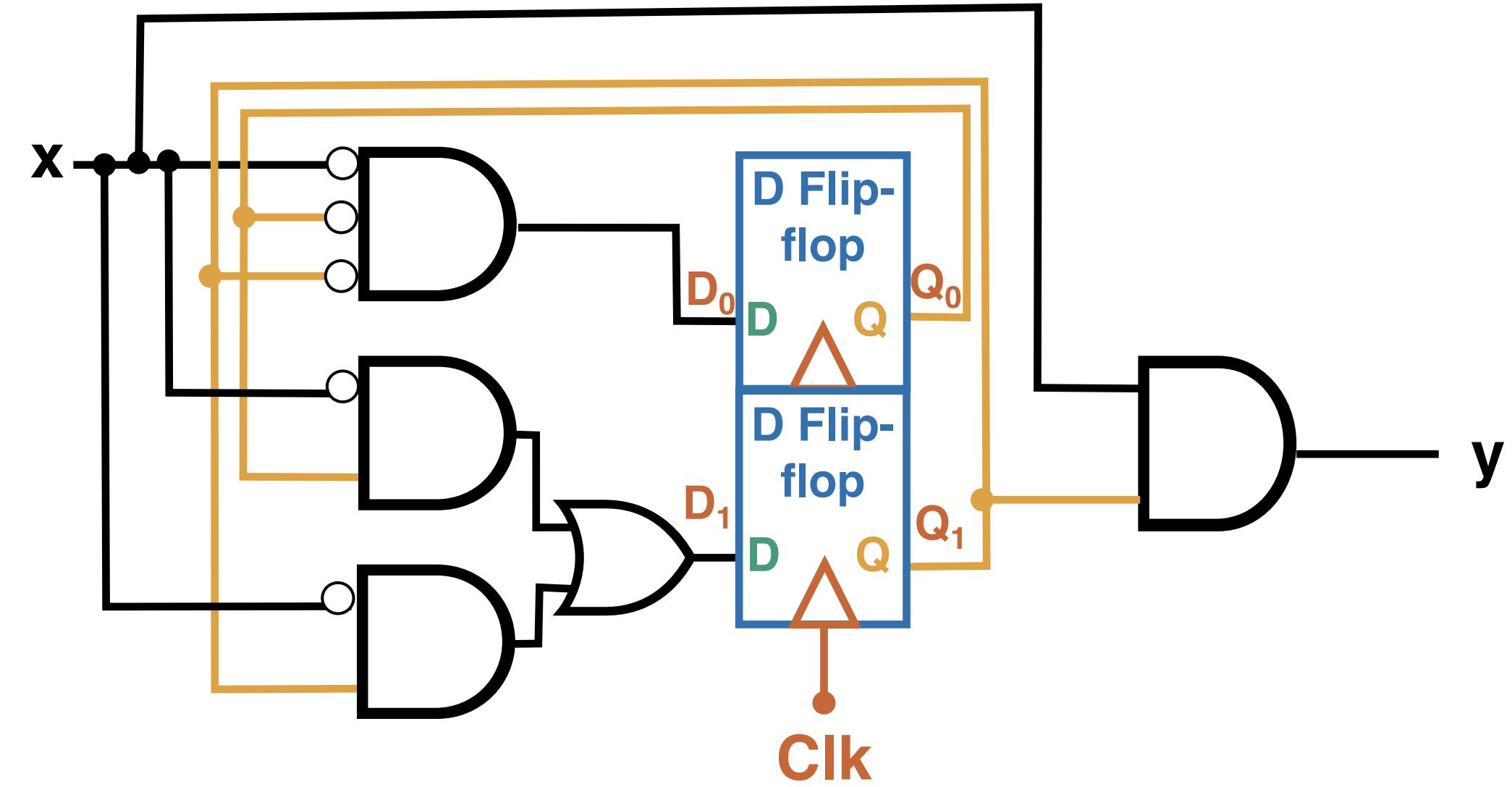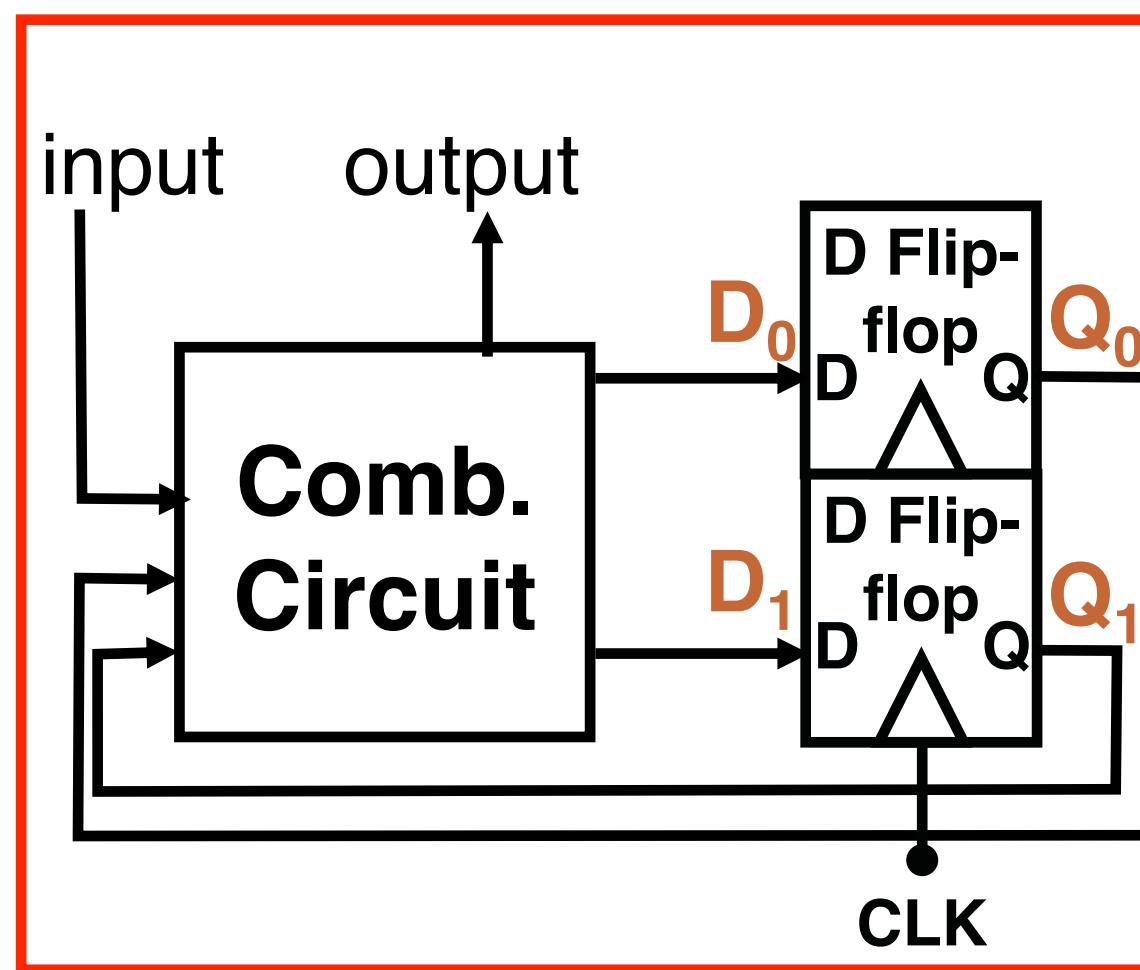

Step 6: Design the circuit using Flip-flops (based on Step 3) and combinational logic (based on Step 5)

# Terminologies - state table & state truth table

## (1) State Table

CurrentState	Next State, Output	
	Input	
	0	1
S0	S1, 0	S0, 0
S1	S2, 0	S0, 0
S2	S2, 0	S0, 1

## (2) State Truth Table

Substitute state names with values



via state assignment

State\Input	0	1
00	01, 0	00, 0
01	10, 0	00, 0
10	10, 0	00, 1

S0	00
S1	01
S2	10

# State table, continue

State Table example 1:

Current State	Next State, Output	
	Input	
	0	1
S0	S1, 0	S0, 0
S1	S2, 0	S0, 0
S2	S2, 0	S0, 1

State Table example 2:

S	XY				Z1 Z2
	00	01	10	11	
A	A	E	B	B	10
B	B	B	D	D	10
C	C	G	A	A	10
D	D	D	C	C	00
E	F	F	F	F	11
F	B	B	B	B	10
G	H	H	H	H	11
H	D	D	D	D	11

S\*

Q: which example represents a Moore machine?

S: current state

S\*: next state

State names: A, B, C, D, E, F, G, H

Inputs: X and Y

Outputs: Z1 and Z2

# Terminologies- excitation table & transition table

## (3) Excitation Table

NextStateOutput StateInput	D <sub>1</sub>	D <sub>0</sub>	y
000	0	1	0
001	0	0	0
010	1	0	0
011	0	0	0
100	1	0	0
101	0	0	1
110	X	X	X
111	X	X	X

## (4) Transition Table

XY			Z <sub>1</sub> Z <sub>2</sub>					
Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	00	01	10	11	Z <sub>1</sub>	Z <sub>2</sub>
000	000	100	001	001	10			
001	001	001	011	011	10			
010	010	110	000	000	10			
011	011	011	010	010	00			
100	101	101	101	101	11			
101	001	001	001	001	10			
110	111	111	111	111	11			
111	011	011	011	011	11			

Q<sub>2</sub>\* Q<sub>1</sub>\* Q<sub>0</sub>\*

### Note:

- Both excitation table and transition table contain truth table for outputs (y in (3) and Z<sub>1</sub>, Z<sub>2</sub> in (4)).
- Excitation table contains the truth table for D<sub>1</sub>, D<sub>0</sub> (inputs of D flip-flops).
- Transition table contains the truth table for next states (Q<sub>2</sub><sup>\*</sup>, Q<sub>1</sub><sup>\*</sup>, Q<sub>0</sub><sup>\*</sup> in (4)).

# Terminology – excitation equation

**(5) Excitation Equation:** Boolean algebra expression(s) for input signals of flip-flops

Example:

$$D_1 = x'Q_0 + x'Q_1$$

$$D_0 = Q_0'Q_1'x'$$

Note:

Input signals of flip-flops ( $D_1, D_0$ ) are functions on current state ( $Q_1, Q_0$ ) and input(s) ( $x$ )

# Terminology – characteristic equation

## (6) Characteristic Equation:

The functional behavior of a latch or flip-flop can be described formally by a characteristic equation that specifies the flip-flop's next state as a function of its current state and inputs.

E.g., Gated SR Latch

**characteristic table**  

Clk	S	R	Q( $t + 1$ )
0	x	x	Q( $t$ ) (no change)
1	0	0	Q( $t$ ) (no change)
1	0	1	0
1	1	0	1
1	1	1	x

**characteristic equation**  
$$Q^* = S + R'Q$$

Alternatively,

$$Q(t+1) = S + R'Q(t)$$

$Q^*$  = next state  
 $Q$  = current state

Previously, we also used  
 $Q(t+1)$  = next state  
 $Q(t)$  = current state

# Terminology – characteristic equation

## (6) Characteristic Equation:

The functional behavior of a latch or flip-flop can be described formally by a characteristic equation that specifies the flip-flop's next state as a function of its current state and inputs.

Device Type	Characteristic Equation
Gated SR Latch	$Q^* = S + R'Q$
D Latch	$Q^* = D$
D Flip-flop	$Q^* = D$
J-K Flip-flop	$Q^* = JQ' + K'Q$
T Flip-flop	$Q^* = Q'$

$Q^*$  = next state  
 $Q$  = current state

Most applicable!  
(our focus)

Not very  
applicable!  
(out of the scope)

# Terminology – transition equation

7) **Transition equation** : Boolean algebra expression(s) of next state as a function of current-state and inputs.

Example:

$$Q_1^* = x'Q_0 + x'Q_1$$

$$Q_0^* = Q_0'Q_1'x'$$

Note:

- Substitute excitation equations into characteristic equations to obtain transition equations.
- Same as excitation equations when using D flip-flops.

# Terminology – output equation

8) output equation : Boolean algebra expression(s) of output(s)

Example 1:  $y = Q_1 x$

Example 2:  $Z_1 = Q_2 + Q_1' + Q_0'$   
 $Z_2 = Q_2 \cdot Q_1 + Q_2 \cdot Q_0'$

Note:


- For Mealy machine, a current output is a function of current state and input(s), e.g., Example 1
- For Moore machine, a current output is only a function of current state, e.g., Example 2

# Converting Mealy to Moore


# Moore or Mealy? – Life on Mars

- Which type of state machine can describe the “Life on Mars” pattern recognizer of “001”.  
**Moore Machine**

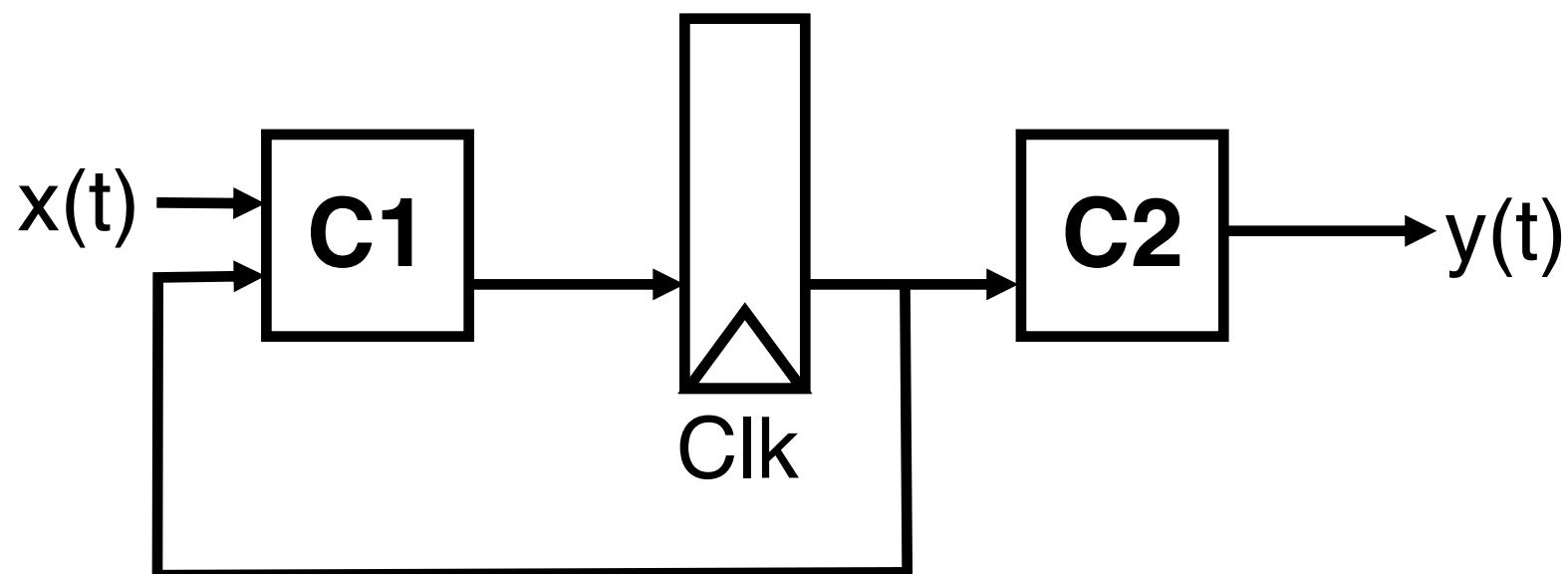- A. Moore machine
- B. Mealy machine
- C. Both
- D. None



**Mealy Machine**

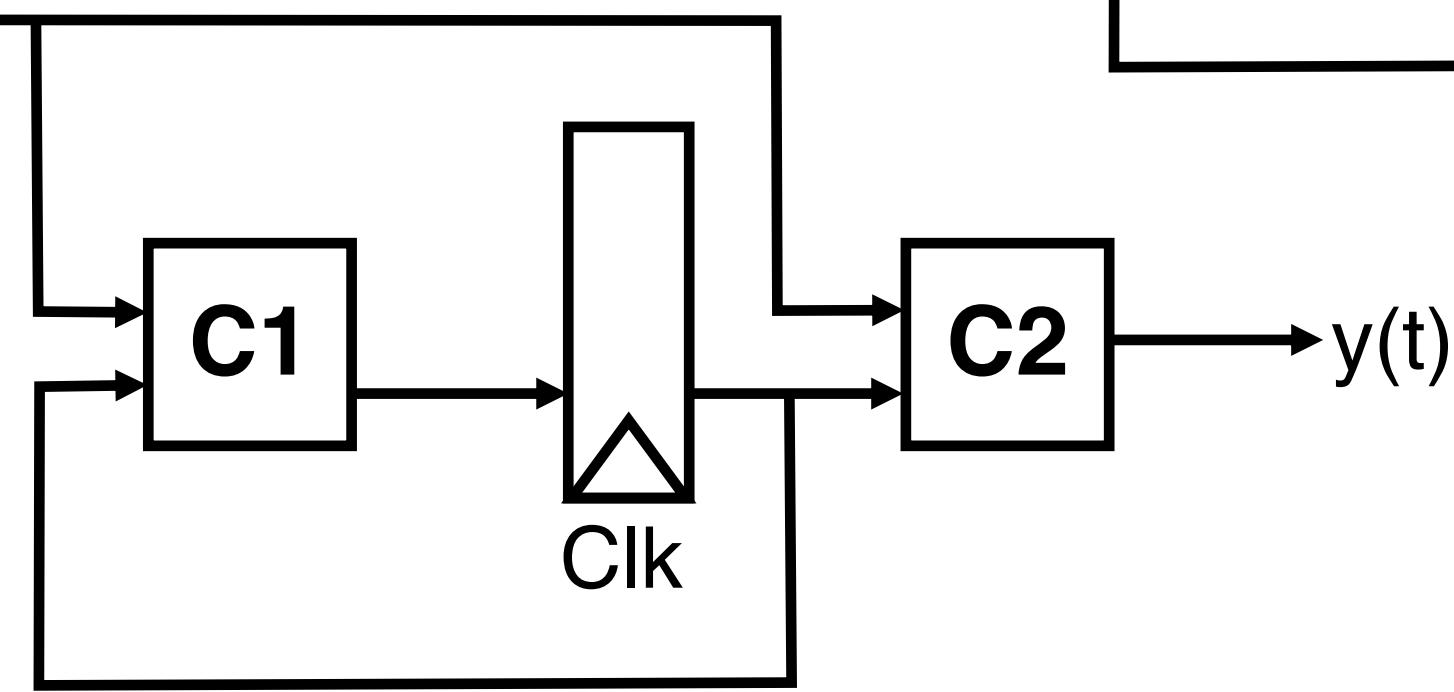


$S(t)$


# Moore or Mealy? – Life on Mars

- Which type of state machine can describe the “Life on Mars” pattern recognizer of “001”.
  - A. Moore machine
  - B. Mealy machine
  - C. Both
  - D. None

**Mealy Machine**

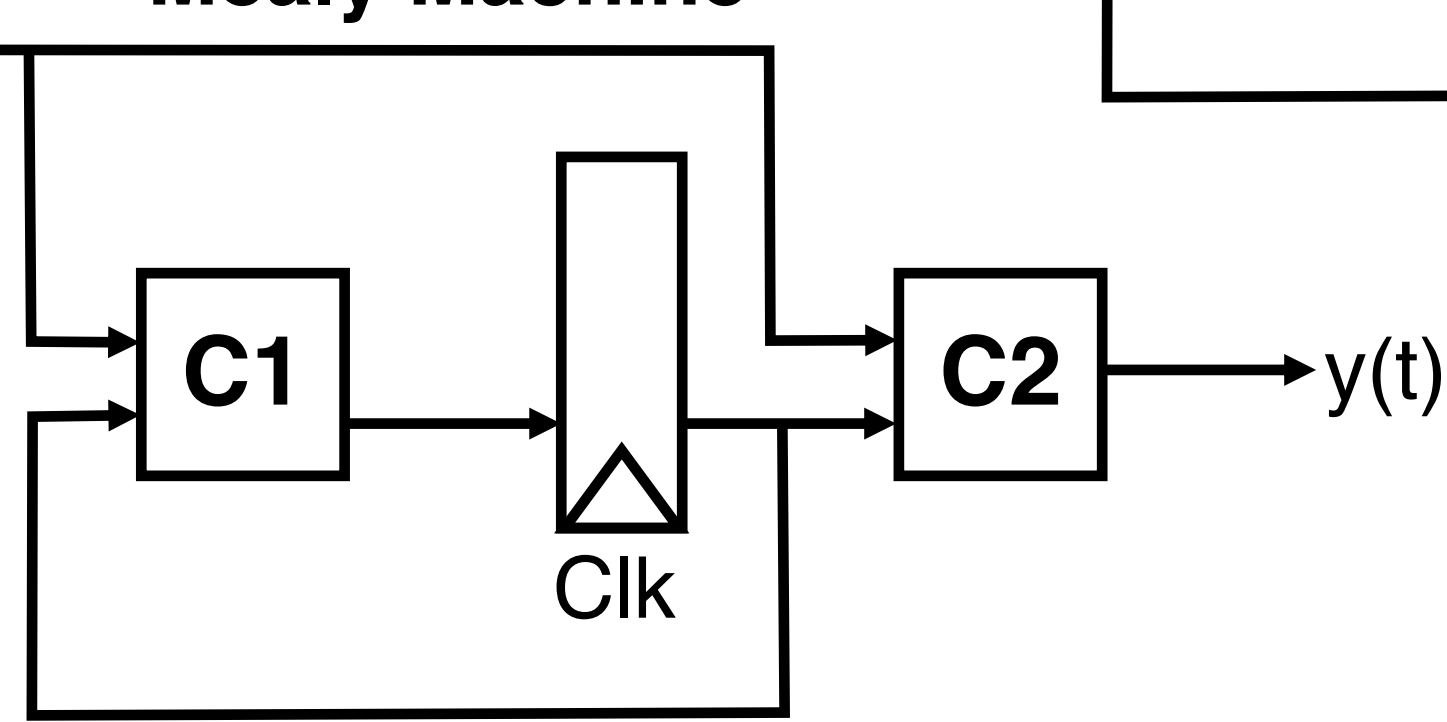


**Moore Machine**

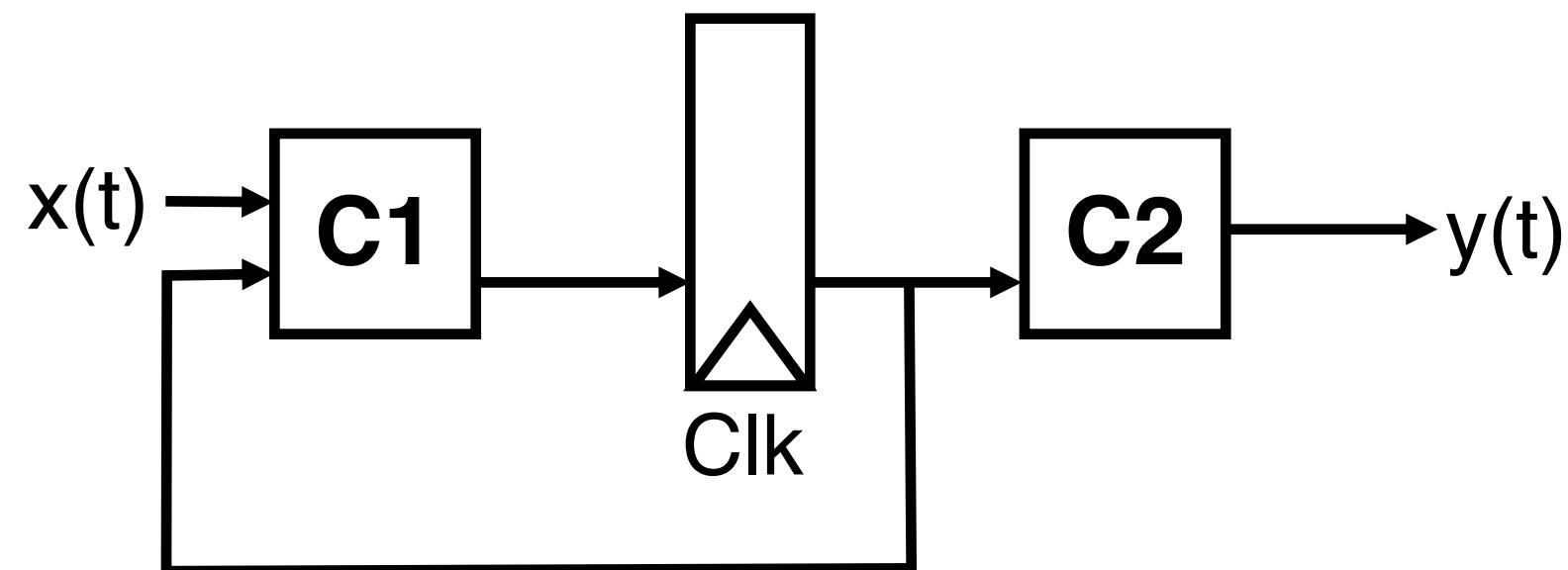
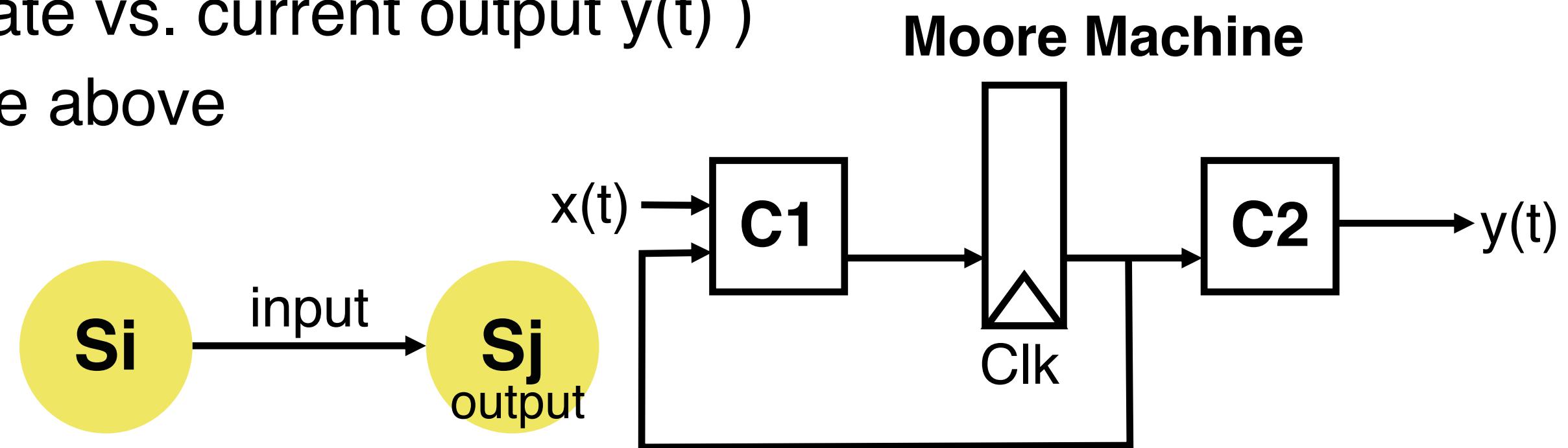
# Moore machine for Life on Mars


- What does state table need to show to design controls of C2 to implement pattern recognizer “001”?
  - (current input  $x(t)$ , current state  $S(t)$  vs. next state  $S(t+1)$ )
  - (current input, current state vs. current output  $y(t)$ )
  - (current state vs. current output  $y(t)$  and next state)
  - (current state vs. current output  $y(t)$  )
  - None of the above



# Moore machine for Life on Mars

- What does state table need to show to design controls of C2 to implement pattern recognizer “001”?
  - (current input  $x(t)$ , current state  $S(t)$  vs. next state,  $S(t+1)$ )
  - (current input, current state vs. current output  $y(t)$ )
  - (current state vs. current output  $y(t)$  and next state)
  - (current state vs. current output  $y(t)$ )
  - None of the above

Moore Machine

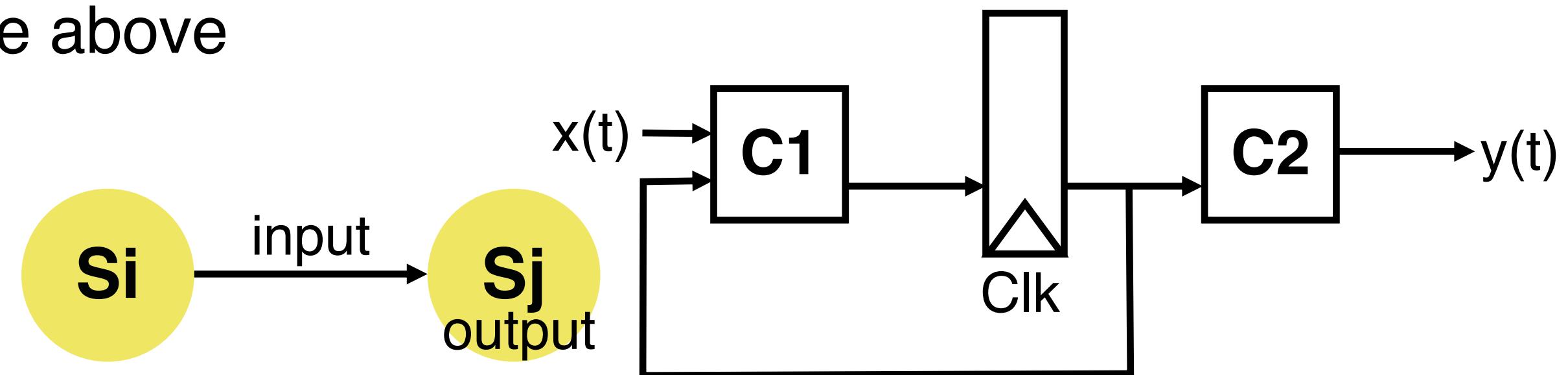

# Conversion from Mealy to Moore

- ① Identify distinct (Next State, y) pair
- ② Replace each distinct (Next State, y) pair with distinct new states
- ③ Insert rows of present state = new states
- ④ Append each present state with its output y

Mealy machine	Current State	Next State	
		Input 0	Input 1
	S0	S1, 0	S0, 0
	S1	S2, 0	S0, 0
	S2	S2, 0	S0, 1

# Conversion from Mealy to Moore

- ① Identify distinct (Next State, y) pair
- ② Replace each distinct (Next State, y) pair with distinct new states
- ③ Insert rows of present state = new states
- ④ Append each present state with its output y

CurrentState	Next State	
	0	1
0	S1, 0	S0, 0
1	S2, 0	S0, 0
2	S2, 0	S0, 1

**Distinct (Next State, y) pairs:**

S0, 0
S1, 0
S2, 0
S0, 1

# Conversion from Mealy to Moore

- ① Identify distinct (Next State, y) pair
- ② Replace each distinct (Next State, y) pair with distinct new states
- ③ Insert rows of present state = new states
- ④ Append each present state with its output y

CurrentState	Next State	
	Input 0	Input 1
S0	S1, 0	S0, 0
S1	S2, 0	S0, 0
S2	S2, 0	S0, 1

Distinct (Next State, y)

pairs:

S0, 0

S1, 0

S2, 0

S0, 1

Distinct new states:

S0

S1

S2

S3

# Conversion from Mealy to Moore

- ① Identify distinct (Next State, y) pair
- ② Replace each distinct (Next State, y) pair with distinct new states
- ③ **Insert rows of present state = new states**
- ④ Append each present state with its output y

CurrentState	Next State	
	Input 0	Input 1
S0	S1, 0	S0, 0
S1	S2, 0	S0, 0
S2	S2, 0	S0, 1

**Distinct (Next State, y)**

**pairs:**

S0, 0 → S0

S1, 0 → S1

S2, 0 → S2

S0, 1 → S3

**Distinct new states:**

# Conversion from Mealy to Moore

3: Insert rows of present state = new states

CurrentState	Next State	
	0	1
Input		
S0	S1, 0	S0, 0
S1	S2, 0	S0, 0
S2	S2, 0	S0, 1

Distinct (Next State, y)  
pairs:



Distinct new states:

CurrentState	Next State	
	0	1
Input		
S0	S1	S0
S1	S2	S0
S2	S2	S3
S3		

# Conversion from Mealy to Moore

- ① Identify distinct (Next State, y) pair
- ② Replace each distinct (Next State, y) pair with distinct new states
- ③ Insert rows of present state = new states
- ④ **Append each present state with its output y**

## Distinct (Next State, y)

pairs:



Current State	Next State		Output
	0	1	
S0	S1	S0	0
S1	S2	S0	0
S2	S2	S3	0
S3			1

# Conversion from Mealy to Moore

- ① Identify distinct (Next State, y) pair
- ② Replace each distinct (Next State, y) pair with distinct new states
- ③ Insert rows of present state = new states
- ④ **Append each present state with its output y**

**Distinct (Next State, y)**

**pairs:**



**Distinct new states:**

Current State	Next State	
	Input 0	Input 1
S0	S1	S0
S1	S2	S0
S2	S2	S3
S3		

# Conversion from Mealy to Moore

**Distinct (Next State, y)**

**pairs:**



CurrentState	Next State	
	0	1
S0	S1	S0
S1	S2	S0
S2	S2	S3
S3	?	?

? For the given Moore machine, what are the next states with respect to present state S3

# Conversion from Mealy to Moore

Distinct (Next State, y)

pairs:



CurrentState	Next State		Output
	0	1	
S0	S1	S0	0
S1	S2	S0	0
S2	S2	S3	0
S3	S1	S0	1

CurrentState

Next State

Input

	0	1
S0	S1, 0	S0, 0
S1	S2, 0	S0, 0
S2	S2, 0	S0, 1

# Summary

- ① Identify distinct (Next State, y) pair
- ② Replace each distinct (Next State, y) pair with distinct new states
- ③ Insert rows of present state = new states
- ④ Append each present state with its output y

CurrentState e	Next State	
	Input 0	1
S0	S1, 0	S0, 0
S1	S2, 0	S0, 0
S2	S2, 0	<b>S0, 1</b>

CurrentState te	Next State		Output
	Input 0	1	
S0	S1	S0	0
S1	S2	S0	0
S2	S2	<b>S3</b>	0
<b>S3</b>	<b>S1</b>	<b>S0</b>	<b>1</b>

# State tables for C1 and C2


Current State	Next State		Output
	Input 0	Input 1	
S0 00	S1	S0	0
S1 01	S2	S0	0
S2 10	S2	S3	0
S3 11	S1	S0	1

C1

Current State-Input	D1	D0
000	0	1
001	0	0
010	1	0
011	0	0
100	1	0
101	1	1
110	0	1
111	0	0

C2

State	y
00	0
01	0
10	0
11	1

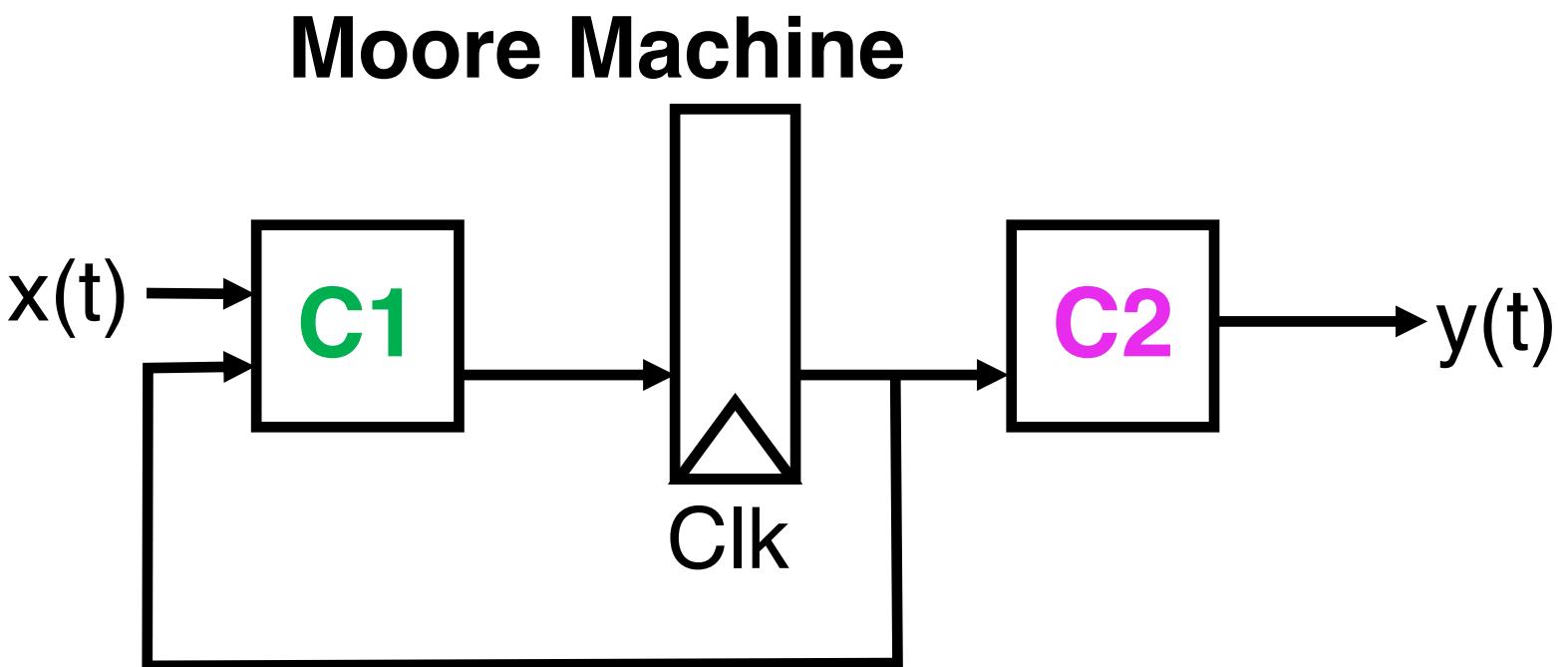

# State tables for C1 and C2

Current State	Next State		Output
	0	1	
S0 00	S1	S0	0
S1 01	S2	S0	0
S2 10	S2	S3	0
S3 11	S1	S0	1

C1

C2

Current State-Input	D1	D0
000	0	1
001	0	0
010	1	0
011	0	0
100	1	0
101	0	0
110	0	1
111	0	0

State	y
00	0
01	0
10	0
11	1

K-Map – D1

	0,0	0,1	1,1	1,0
0	0	1	0	1
1	0	0	0	1

$$D1 = x'Q_1'Q_0 + Q_1Q_0'$$

	0,0	0,1	1,1	1,0
0	1	0	1	0
1	0	0	0	1

$$D0 = Q_0'Q_1'x' + Q_0Q_1x' + Q_0'Q_1x'$$

K-Map – y

	0	1
0	0	0
1	0	1

$$y = Q_0Q_1$$

Moore Machine

