 


Homework 1

1. (10 pts). Assuming an n-type transistor with V_{ds} of 1.8V and V_t of 0.7V, find the ranges of V_{gs} to put the transistor in cutoff, linear, and saturation regions.
2. (10 pt). Assume a NMOS has $V_t = 0.6V$ and $W/L = 5/2$, $k_n = 73\mu A/V^2$. Calculate the drain current I_{ds} for the given V_{ds} and V_{gs} . Assume $\lambda = 0$
 - a. $V_{ds} = 1.5V$, $V_{gs} = 1V$
 - b. $V_{ds} = 1V$, $V_{gs} = 0.5V$
 - c. $V_{ds} = 0.2V$, $V_{gs} = 1V$
3. (15 pts). Compute the parasitic resistance of the following metal wire, where the sheet resistance (R_\square) of metal1 is $0.08\Omega/\square$.




4. (20 pts). Predict how interconnect resistance, interconnect capacitance and RC delay would change for a 90nm processing from the 180nm process: (a) Ideal scaling and (b) Constant dimension scaling. (tip: the scaling factor $S=0.5$).

Table: Interconnect scaling trends (S : scaling factor)

	ideal scaling	constant dimension scaling
line width and spacing	S	1
wire thickness	S	1
interlevel dielectric thickness	S	1
wire length	$1/\sqrt{S}$	$1/\sqrt{S}$
resistance per unit length	$1/S^2$	1
capacitance per unit length	1	1
RC delay	$1/S^3$	$1/S$
current density	$1/S$	S

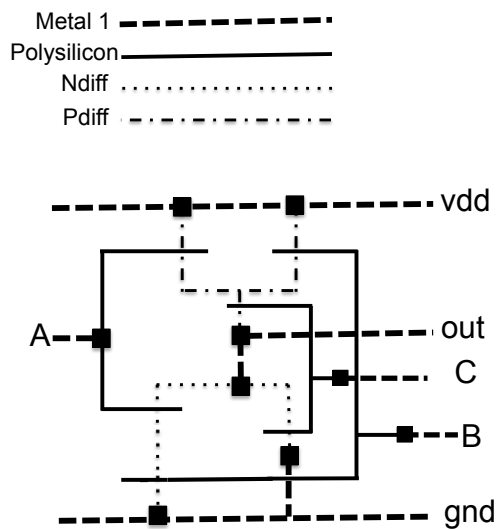5. (20 pts). Consider the following stick diagram. Draw the electrically equivalent transistor-level schematic.



- 6.. (15pt). Draw top-view layouts for:

- a) A metal-1 wire to n-diffusion wire through a via
- b) A poly wire with width of 25λ
- c) A $W/L = 4/3$ n-type MOSFET transistor
- d) A $W/L = 6/2$ p-type MOSFET transistor