

# **HLSM & RTL Design**

## **(High-Level State Machine & Register Transfer Level)**

Jia Chen  
jiac@ucr.edu

# **HLSM — High-Level State Machine**


# Soda dispenser

- Soda dispenser: dispenses a soda when enough money has been inserted

**s**: 8-bit input  
cost of a soda

**a**: 8-bit input  
value of the deposited coin

 
**c**: 1-bit input  
c=1 coin is deposited  
c=0 coin is not deposited



**d**: 1-bit output  
d=1 machine dispenses a soda  
d=0 machine does not dispenses a soda
 
# High-Level State Machine

- An FSM has single-bit inputs and outputs
- Some behaviors may be too complex to describe by using classical FSMs
  - E.g., a sequential system has multibit data input and output, such as a system with 8-bit data input, e.g., **a** and **s** in the soda dispenser machine



- A **high-level state machine (HLSM)** is a form of extended FSM that supports multi-bit data input/output and data operations.

# HLSMs v.s. FSMs

## □ Similarity

- Sequential circuit
- Transitions happen at the edge of a clock
- Store states
- Need registers

## □ Dissimilarity


- HLSM stores multibit data, but FSM stores single bit data

# HLSM for soda dispenser

HLSM supports: inputs, outputs, & variables.


A **variable** is a data item that maintains a value, and can be read or assigned.

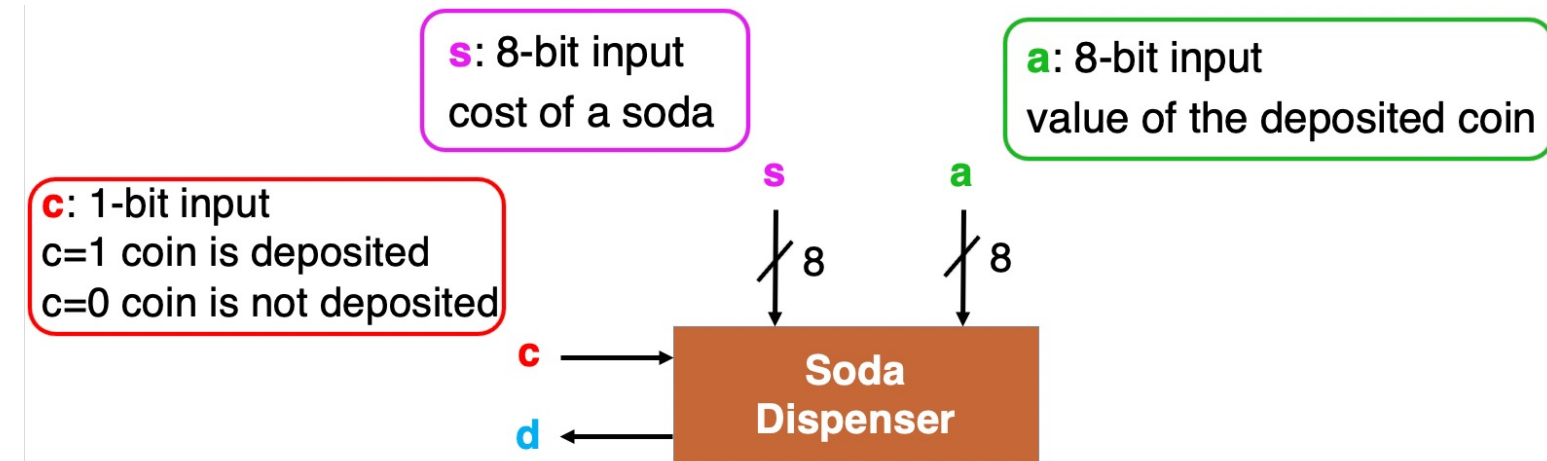E.g., “**tot**”: the total money deposited




**d**: 1-bit output  
d=1 machine dispenses a soda  
d=0 machine does not dispenses a soda

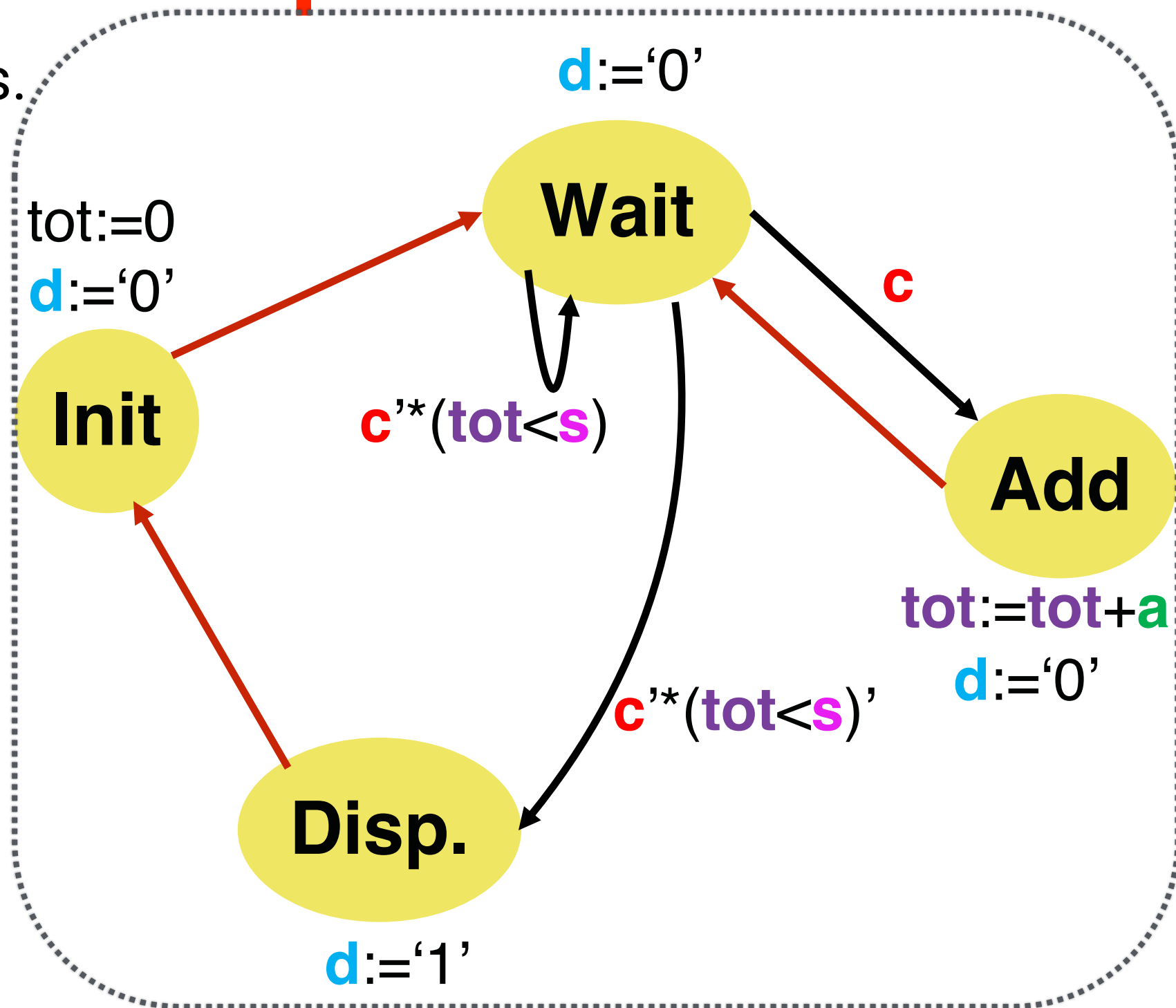→  
Move to next state  
regardless of inputs


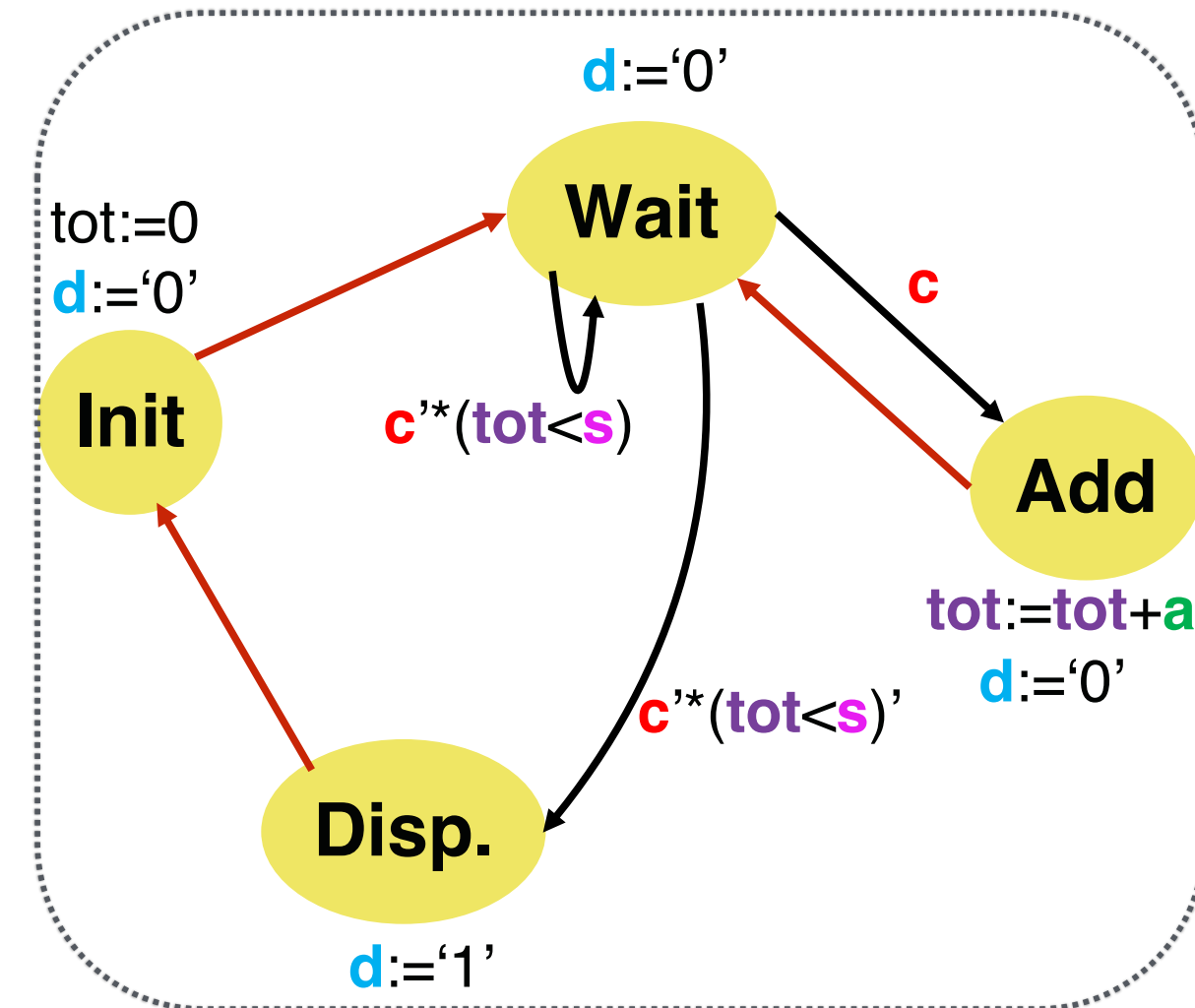
# Benefits of HLSMs


- High-level state machine (HLSM) extends FSM with:
  - Multi-bit input/output (e.g., **a**, **s**)
  - Local storage (e.g., store **tot**)
  - Arithmetic operations (e.g., **tot** < **s** and **tot** + **a**)
- Conventions
  - Each transition is implicitly ANDed with a rising edge of the clock
  - Any bit output not explicitly assigned a value in a state is implicitly assigned to 0. This convention does not apply for multibit outputs  
(e.g., **d**:=**'0'** can be omitted in “Wait” and “Add”)
  - Every HLSM multibit output is registered (stored)



# Conventions
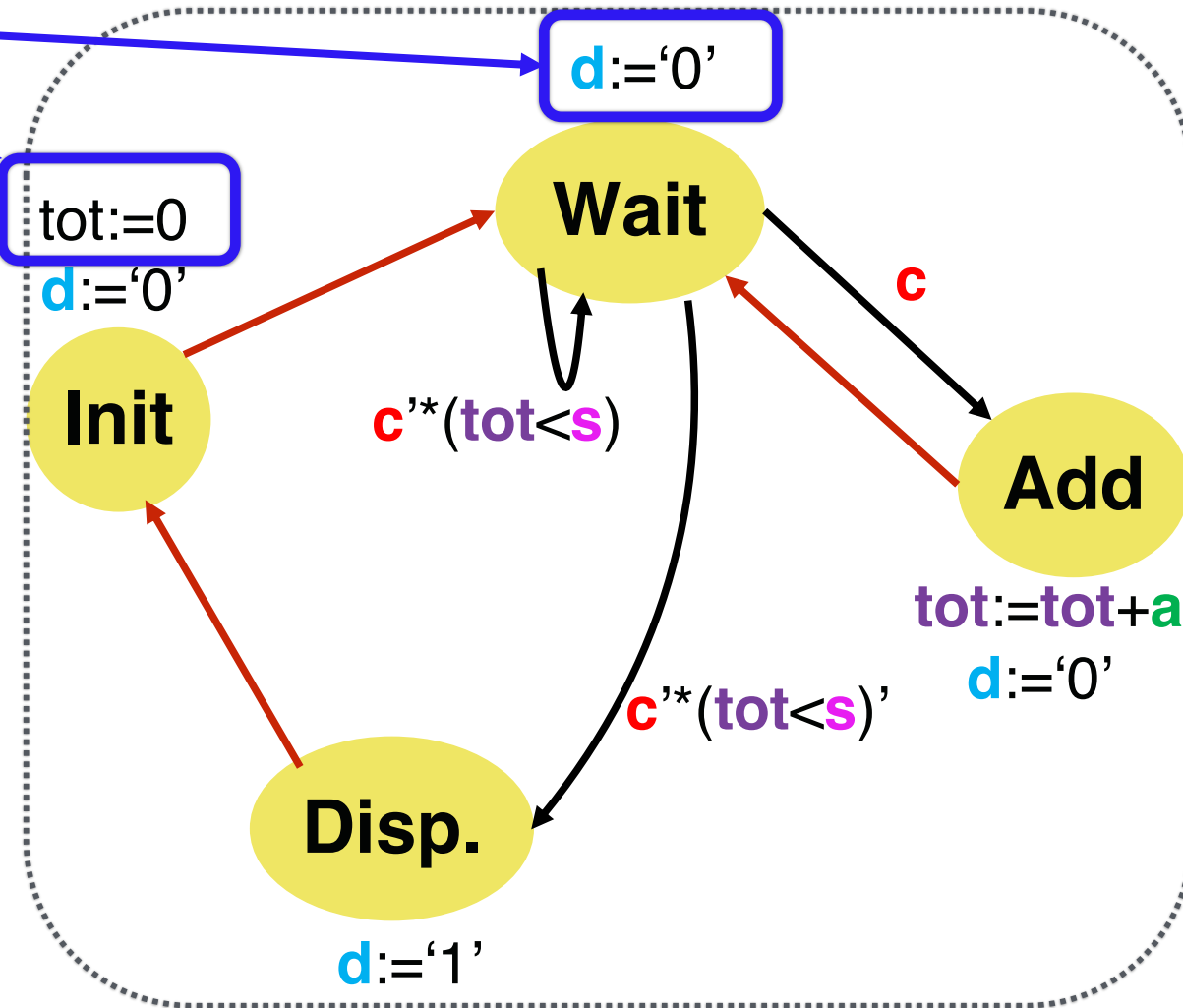
## ❑ Numbers:

- Single-bit: '0' (single quotes)
- Integer: 0 (no quotes)
- Multi-bit: "0000" (double quotes)



❑ `==` for comparison equal

❑ `//` precedes a comment



# Challenges in High-Level State Machines


- ❑ Factors that make the FSM design of this problem difficult
  - 8-bit input/output
  - Tracking the current total
  - Multibit comparison

# RTL (Register Transfer Level) Design
 
# RTL Design Process

- ❑ The process of capturing behavior as an HLSM and converting to a circuit is known as *register-transfer-level (RTL) design*

Step 1: Capture a high-level state machine



Step 2: Convert it to a circuit

# RTL Design

## □ Controllers

- Control input/output: single bit (or just a few) representing event or state
- FSM describes behavior; implementation

## □ Datapath components

- Data input/output: Multiple bits collectively representing single entity
- Datapath components included registers, adders, comparators, multipliers, etc.

## □ This Lecture: custom **processors**

- Processor: Controller and datapath components working together to implement an algorithm

# RTL Design Process

## □ Step 1: Capture a high-level state machine

- Describe the system's desired behavior as a high-level state machine. The state machine consists of states and transitions. The state machine is high level because the **transition conditions** and the **state actions** are more than just Boolean operations on single-bit input and outputs
- Recommendations:
  - ✓ Always list all inputs, outputs and local registers on top of your HLSM diagram
  - ✓ Clearly specify the size in bits of each of them
  - ✓ On states: update the value of registers, update of outputs
  - ✓ On transitions: express conditions in terms of the HLSM inputs or state of the internal values and arithmetic operations between them.

# RTL Design Process

- Step 2: Convert it to a circuit
  - Create a datapath
    - Create a datapath to carry out the data operations of the high level state machine
    - Elements of your datapaths can be registers, adders, comparators, multipliers, dividers, etc.
  - Connect the datapath to a controller
    - Connect the datapath to a controller block.
    - Connect the external control inputs and outputs to the controller block.
    - Clearly label all control signals that are exchanged between the datapath and the controller
  - Derive the controller's FSM
    - Convert the high-level state machine to a finite state machine (FSM) for the controller, by replacing data operations with setting and reading of control signals to and from the datapath
  - Implement the controller

# RTL Design Summary

## □ Recall

### ✓ Combinational Logic Design

- First step: Capture behavior (using equation or truth table)
- Remaining steps: Convert to circuit

### ✓ Sequential Logic Design

- First step: Capture behavior (using FSM)
- Remaining steps: Convert to circuit



## □ RTL Design - the method for creating custom processors

- First step: Capture behavior (using high-level state machine)
- Remaining steps: Convert to circuit
  - High-level architecture (datapath and control path)
  - Datapath capable of HLSM's data operations
  - Design controller to control the datapath
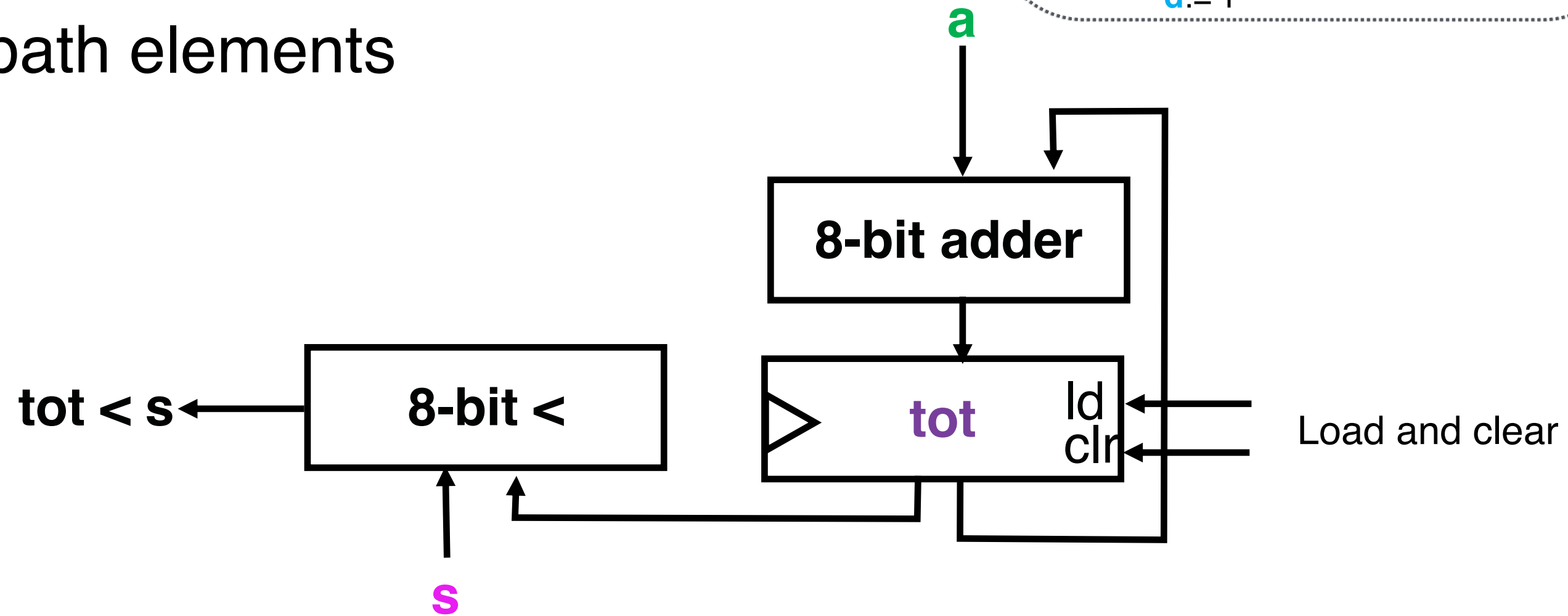 
# Create Datapath for Soda Dispenser

- s**: 8-bit input cost of a soda;
- a**: 8-bit input value of the deposited coin;
- c**: 1-bit input;
- d**: 1-bit output

- Register: **tot**
- Comparator: to compare **tot** and **s**
- Adder: to update **tot = tot + a**
- Connect datapath elements
- I/O interface






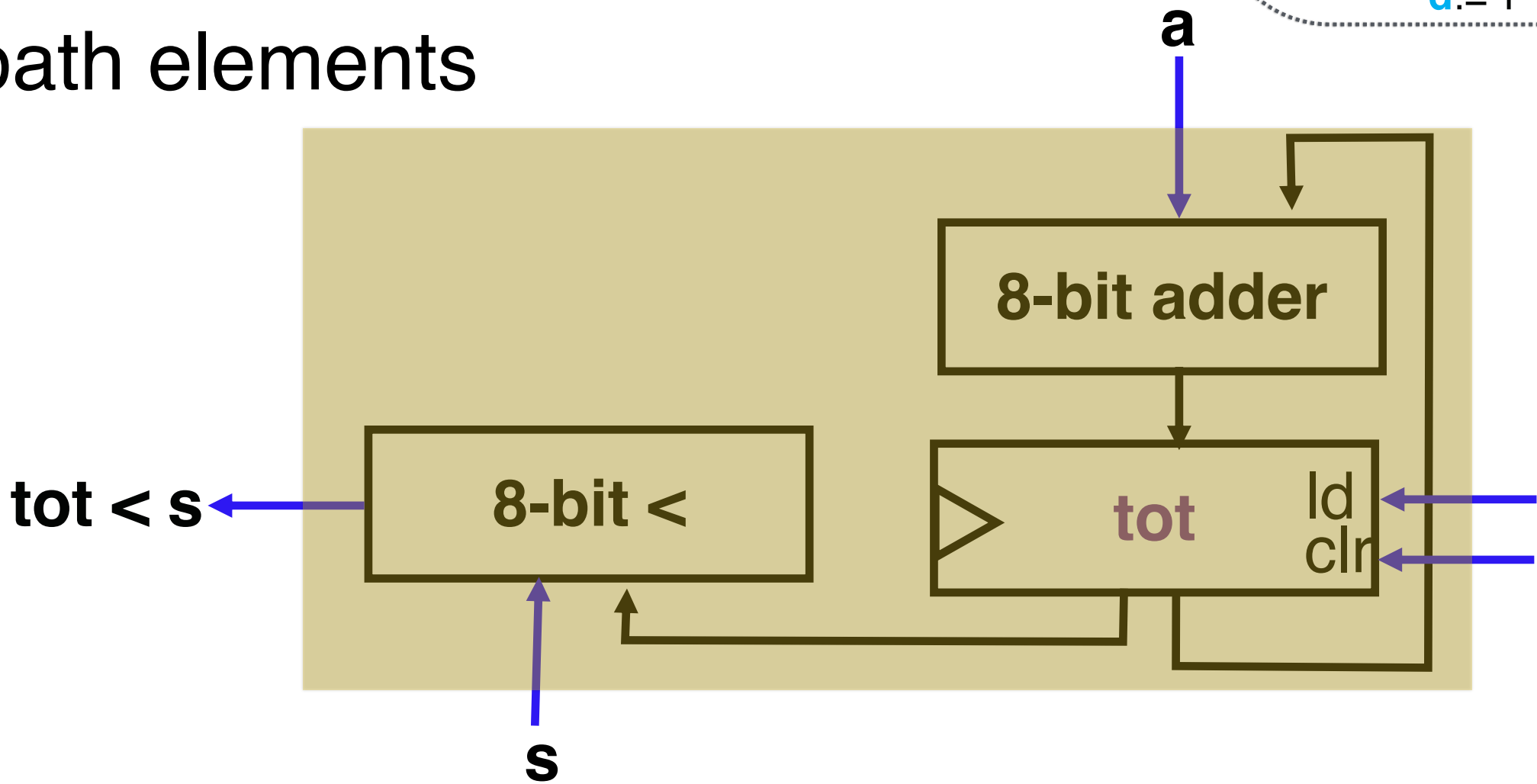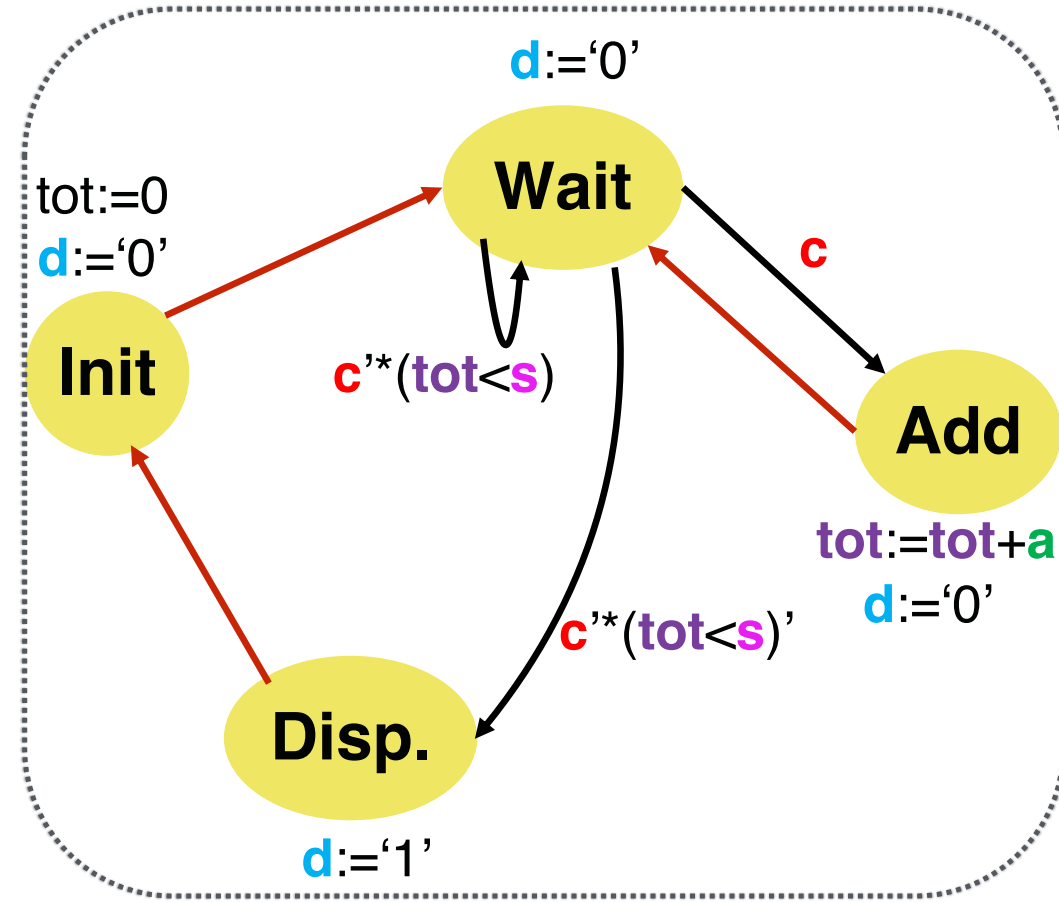
# Create Datapath for Soda Dispenser


- s**: 8-bit input cost of a soda;
- a**: 8-bit input value of the deposited coin;
- c**: 1-bit input;
- d**: 1-bit output

- Register: **tot**
- Comparator: to compare **tot** and **s**
- Adder: to update **tot = tot + a**
- Connect datapath elements
- I/O interface




**Datapath**  
(4 inputs and 1 output)

# Connect Datapath to a Controller

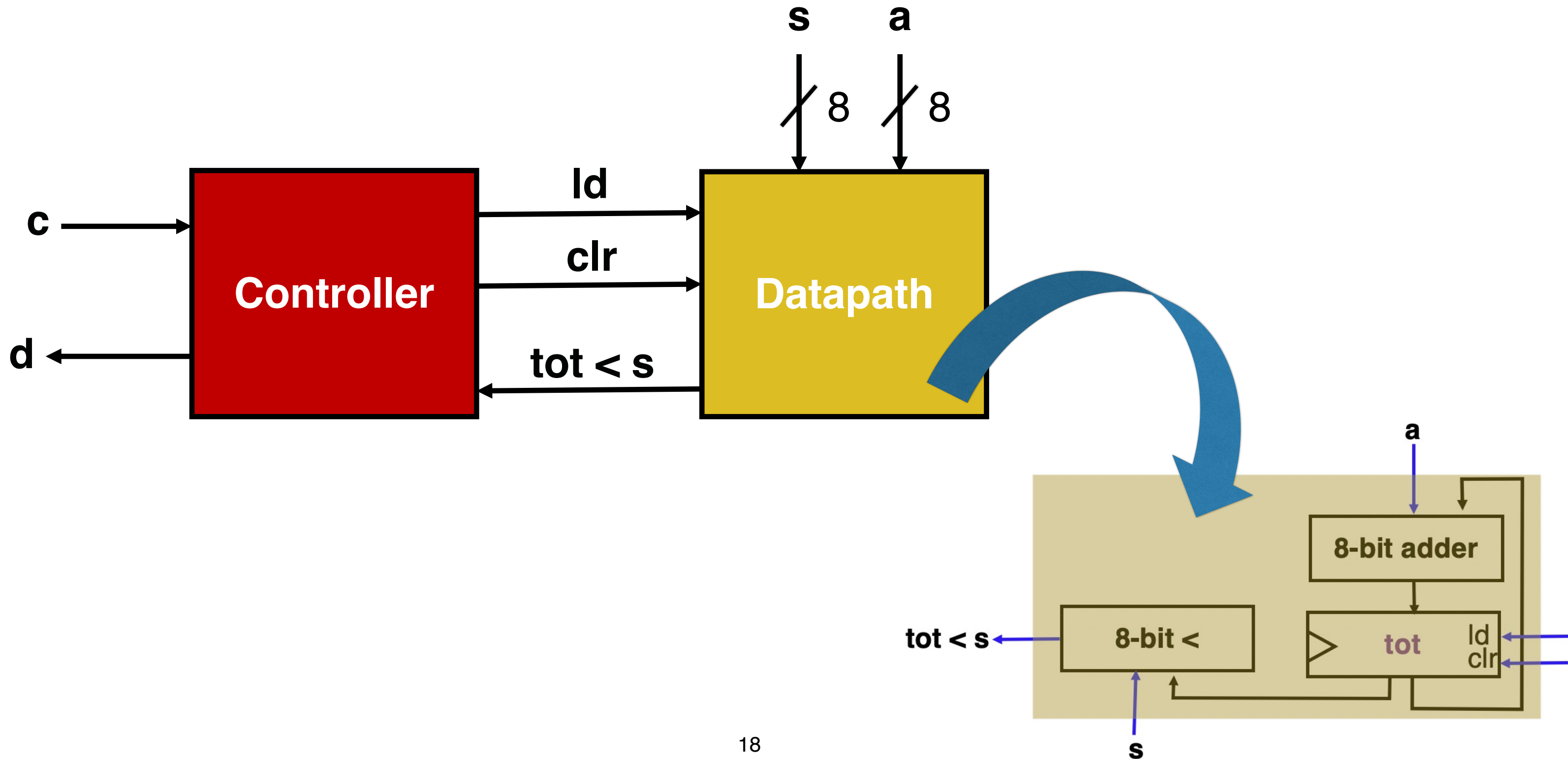
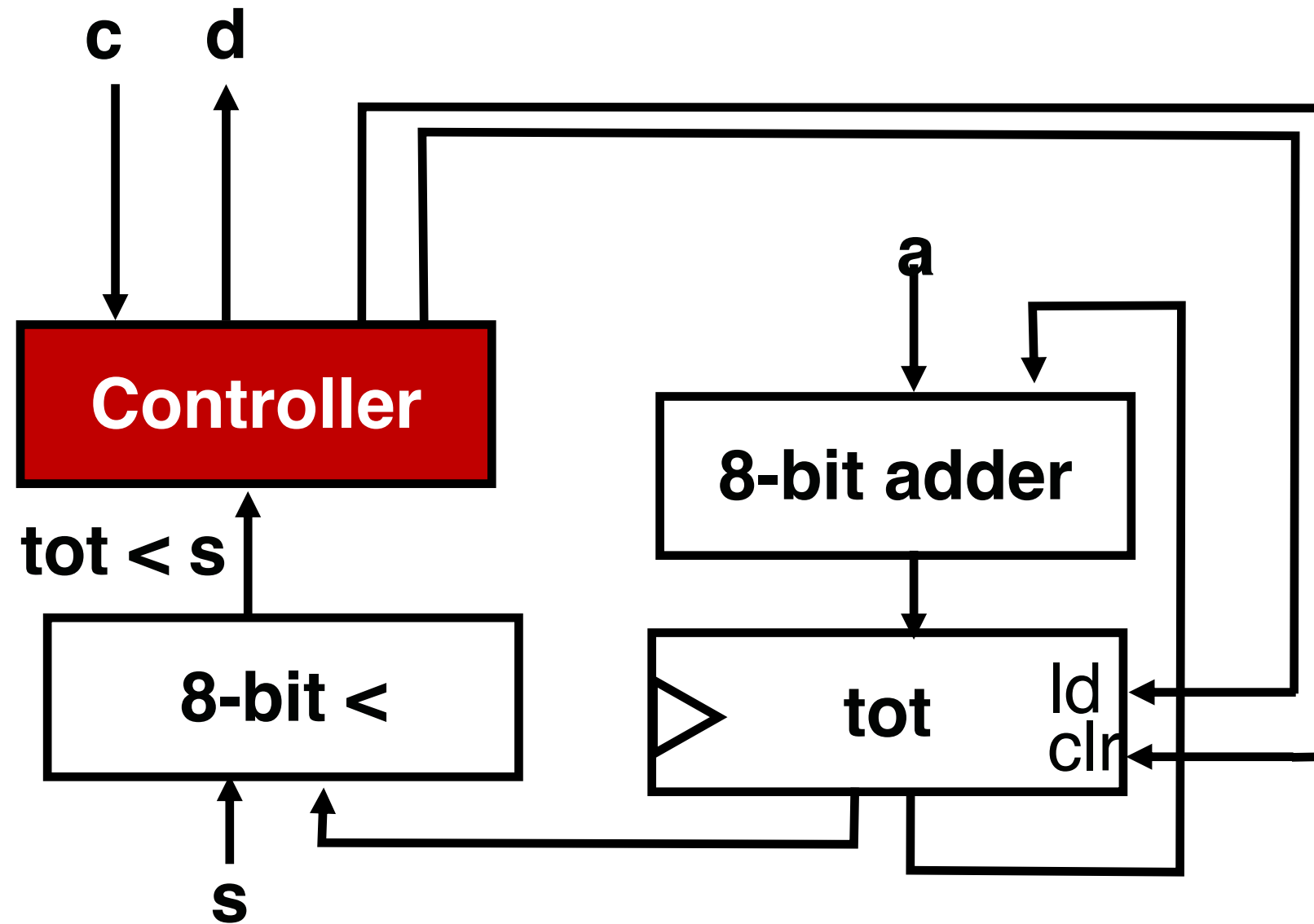
# Connect Datapath to a Controller



- Controller's inputs
  - External input c (coin detected)
  - Input from datapath comparator's output, which we named  $\text{tot} < s$
- Controller's outputs
  - External output d (dispense soda)
  - Outputs to datapath to load and clear the tot register






So far, only the design of the Controller is missing!
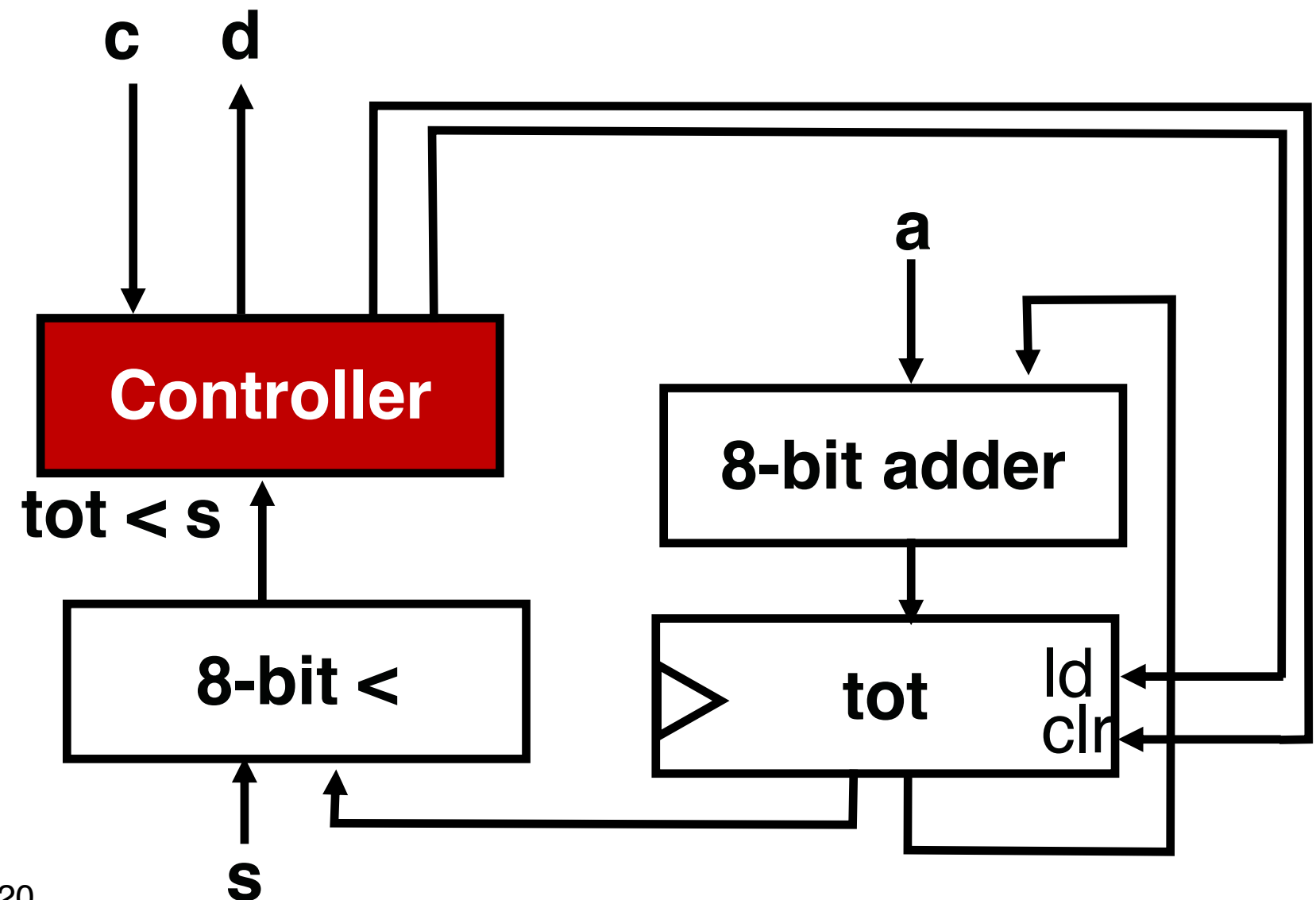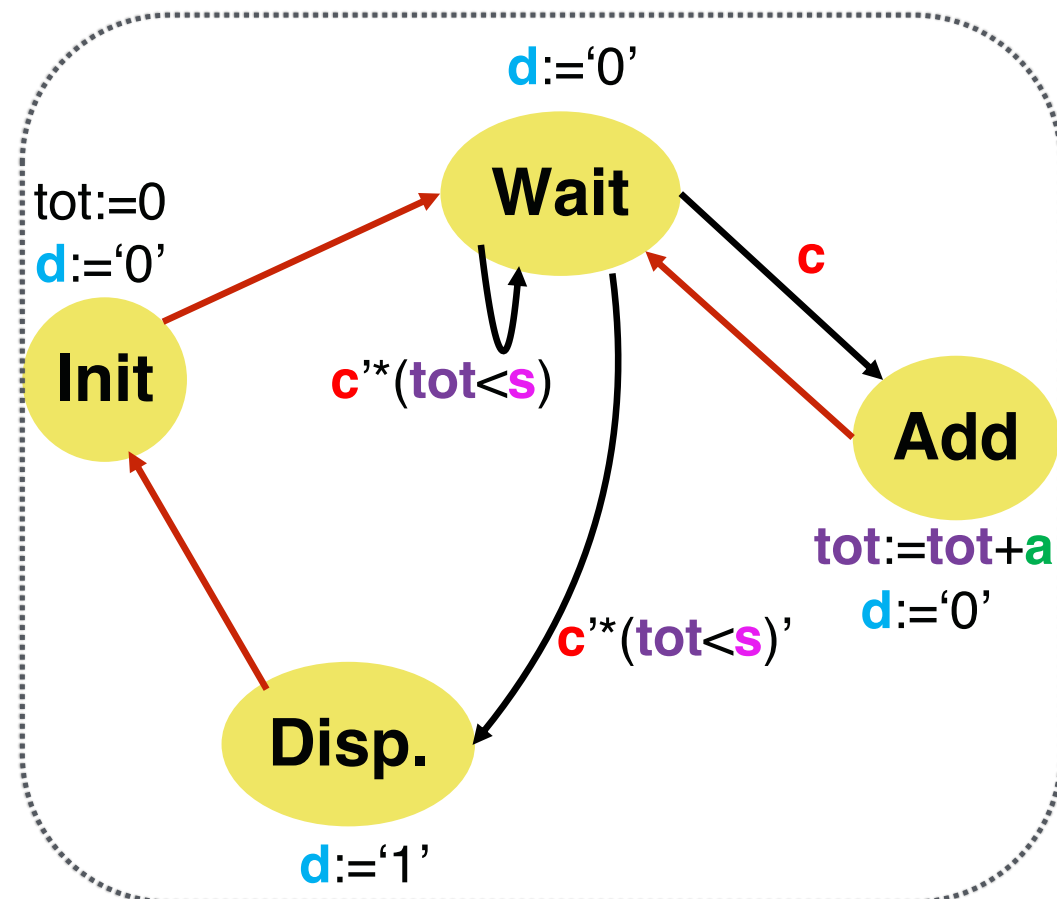
# Derive the Controller's FSM


- FSM has the same states and arcs as HLSM
- But set/read datapath control signals (signals connected to the controller) for all datapath operations and conditions




# Derive the Controller's FSM

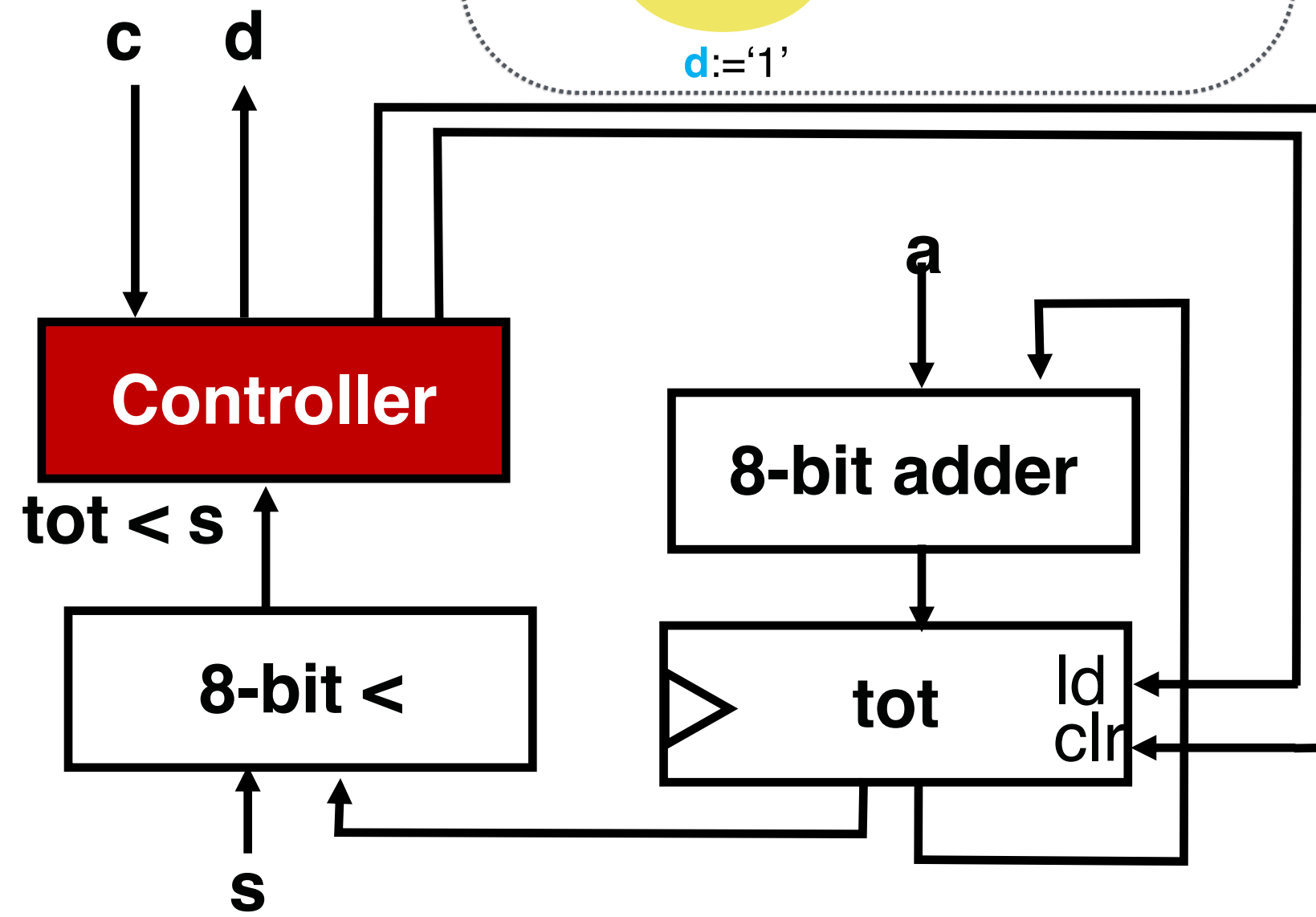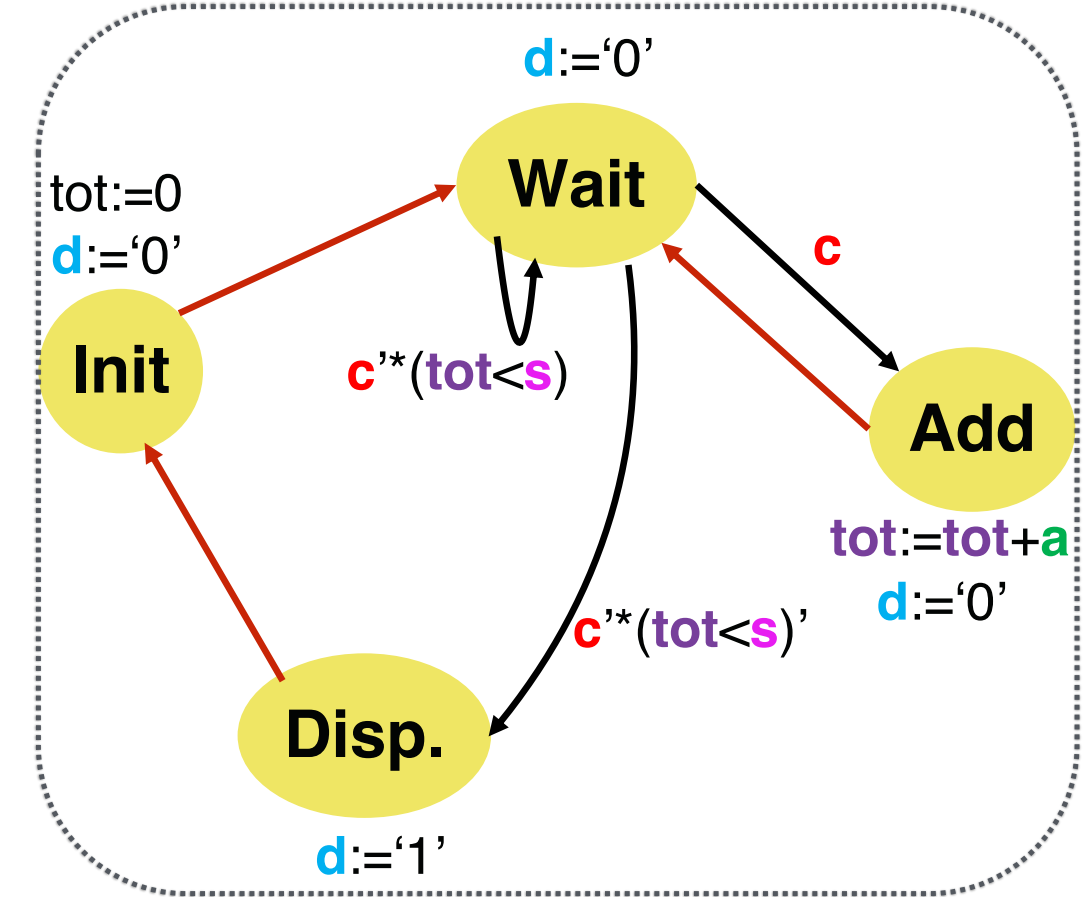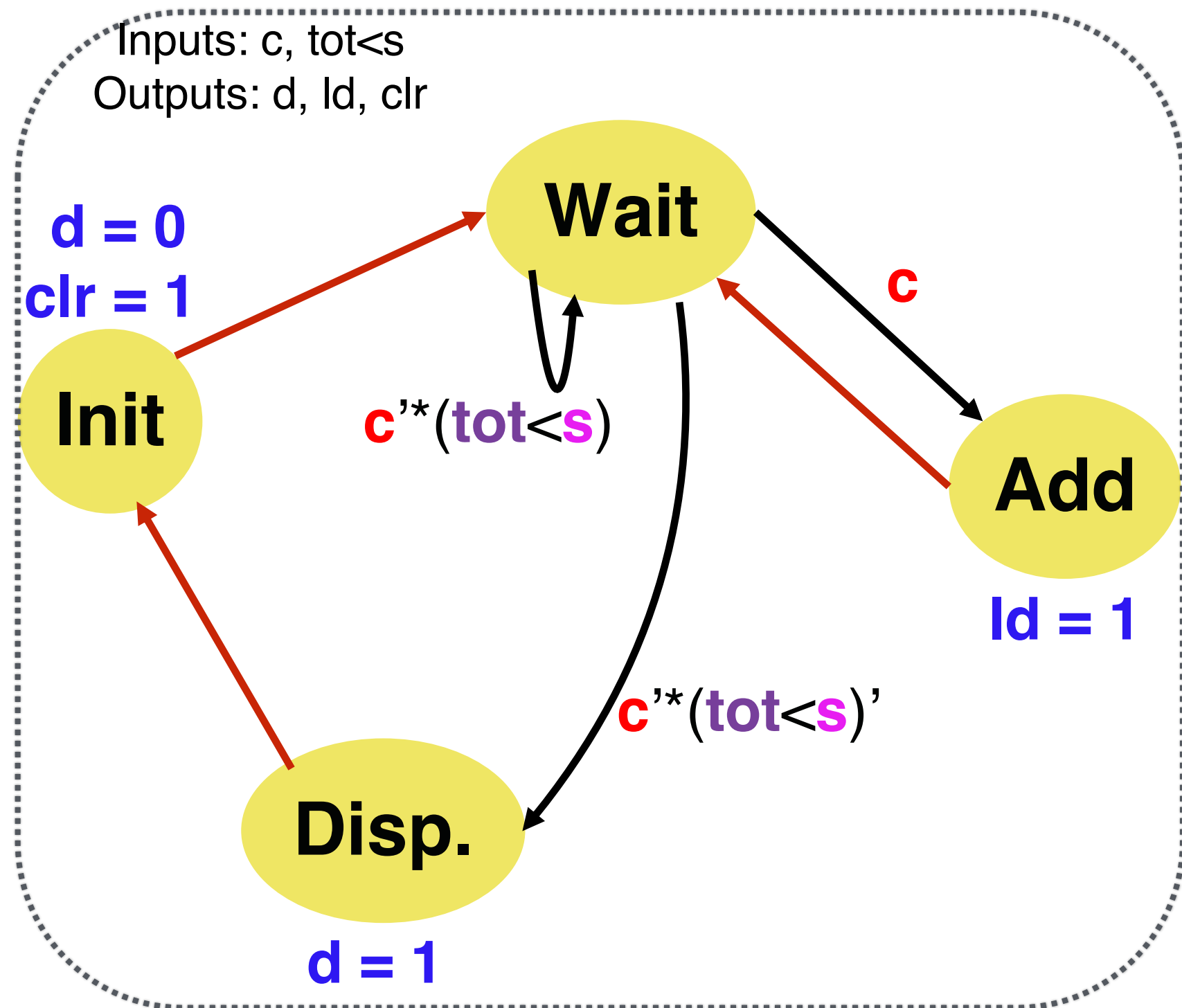
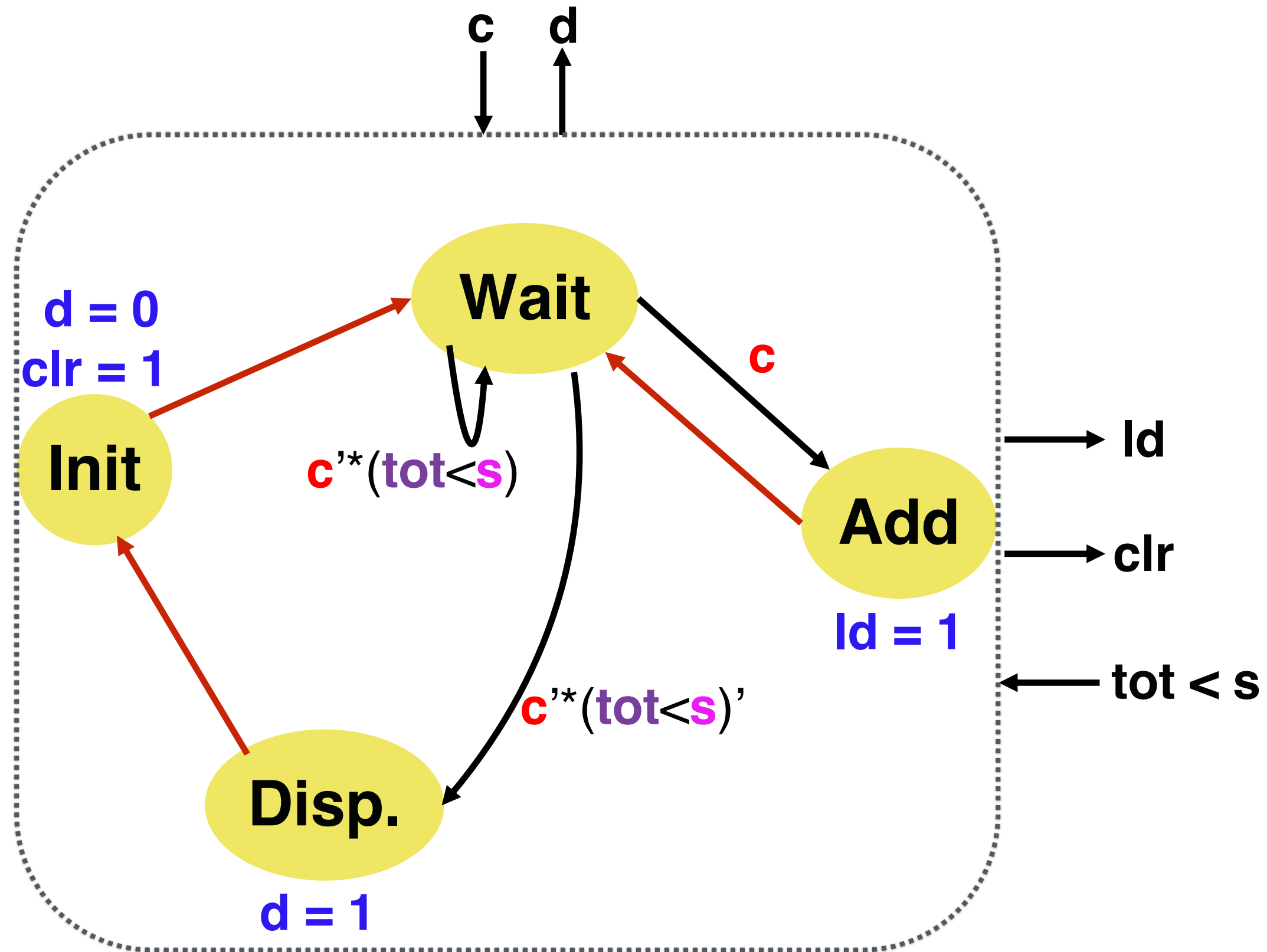
# Final Step: Implement the controller FSM


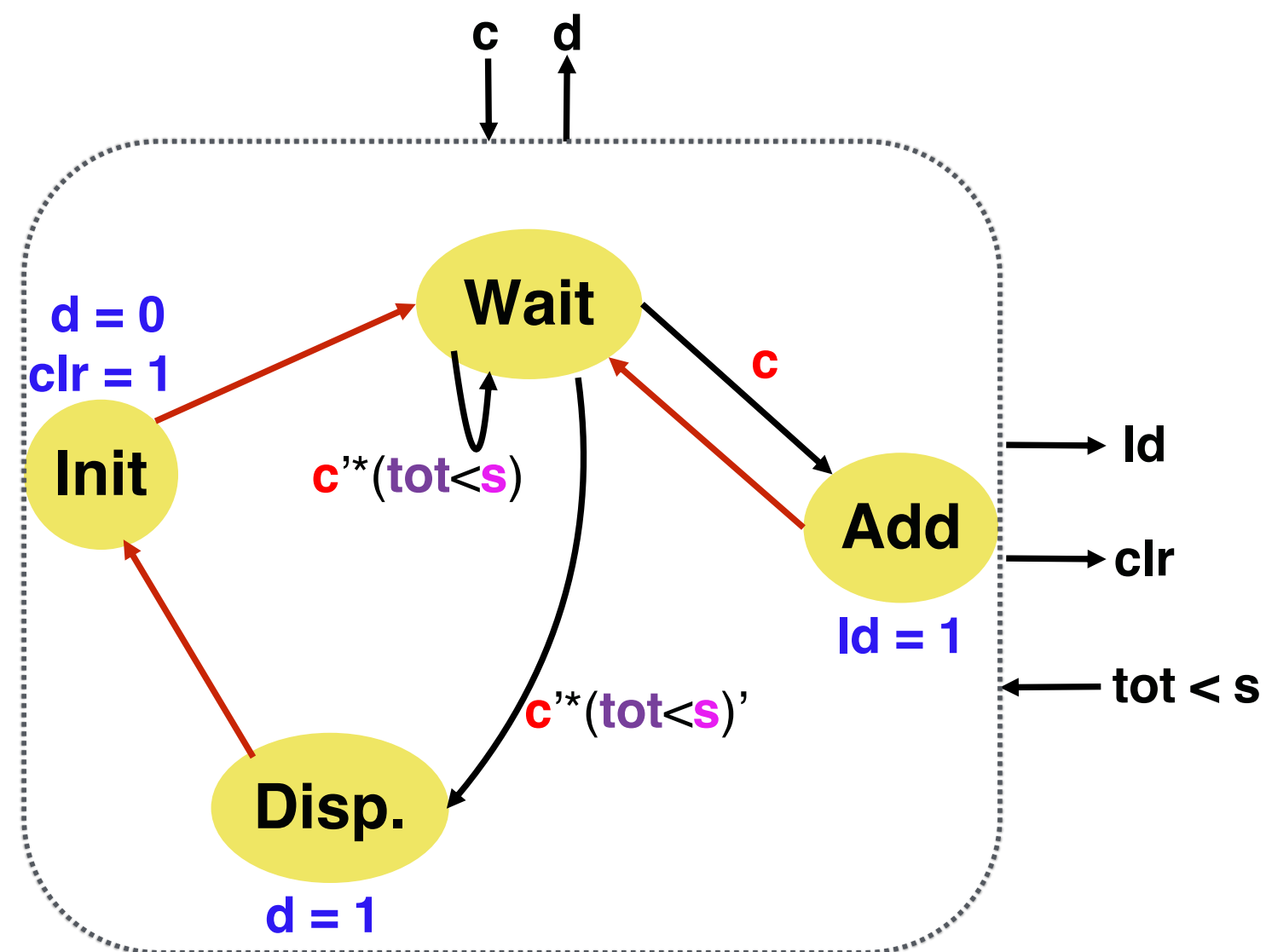
# Final Step: Implement the controller FSM



Excitation table

Current state Inputs					Next state Outputs				
	Q1	Q0	c	tot<s	D1	D0	d	ld	clr
Init	0	0	0	0	0	1	0	0	1
	0	0	0	1	0	1	0	0	1
	0	0	1	0	0	1	0	0	1
	0	0	1	1	0	1	0	0	1
Wait	0	1	0	0	1	1	0	0	0
	0	1	0	1	0	1	0	0	0
	0	1	1	0	1	0	0	0	0
	0	1	1	1	1	0	0	0	0
Add	1	0	0	0	0	1	0	1	0
			...				...		
Disp	1	1	0	0	0	0	1	0	0
			...				...		

... means the other 3 rows have the same outputs

# Soda dispenser example

□ Not an FSM because:

- ✓ Multi-bit (data) inputs  $a$  and  $s$
- ✓ Local register  $tot$
- ✓ Data operations  $tot=0$ ,  $tot < s$ ,  $tot=tot+a$ .

□ Useful high-level state machine:

- ✓ Data types beyond just bits
- ✓ Local registers
- ✓ Arithmetic equations/expressions