

## Homework 4 Solution

**Problem 1:** What is the simplest SOP and POS expressions for  $F = \Sigma_{A,B,C}(0, 1, 3, 4, 6) + D(2, 5)$ , where “D” represents “Don’t care”; see the K-map of F below.

		A'B'	A'B	AB	AB'
		0,0	0,1	1,1	1,0
c'	0	1	X	1	1
c	1	1	1	0	X

**Answer:**

		A'B'	A'B	AB	AB'
		0,0	0,1	1,1	1,0
c'	0	1	X	1	1
c	1	1	1	0	X

$A'$

$C'$

**The simplest SOP:  $F = A' + C'$**

		A'B'	A'B	AB	AB'
		0,0	0,1	1,1	1,0
c'	0	1	X	1	1
c	1	1	1	0	X

$A' + C'$

**The simplest POS:  $F = A' + C'$**

**Problem 2:** Sketch the outputs Q and QN (aka, draw the output waveforms for Q and QN) of an SR-Latch (the basic latch) of the type shown in Figure 1 for the input waveforms shown below. Assuming that initially  $Q=0$  and  $QN=1$ . In your solution, please include the waveforms of R and S so that the alignment between inputs and outputs is clear.



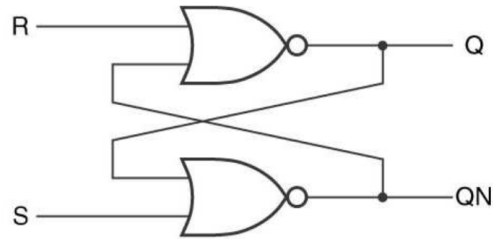


Figure 1: Circuit of the SR-Latch

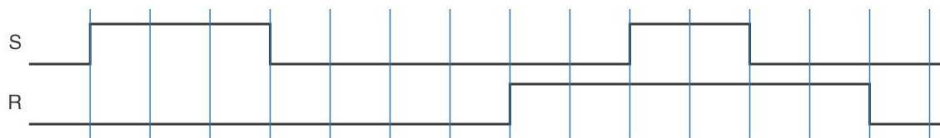

**Answer:**

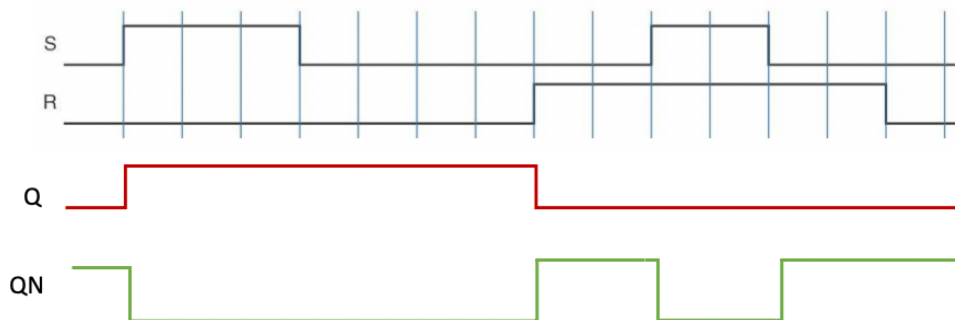

**Problem 3:** For the circuit in Figure 2, please draw the waveforms for  $Q_a$ ,  $Q_b$ , and  $Q_c$  given the timing diagrams of Clock and D signals in Figure 3, where the initial values of  $Q_a$ ,  $Q_b$ , and  $Q_c$  are zeros.

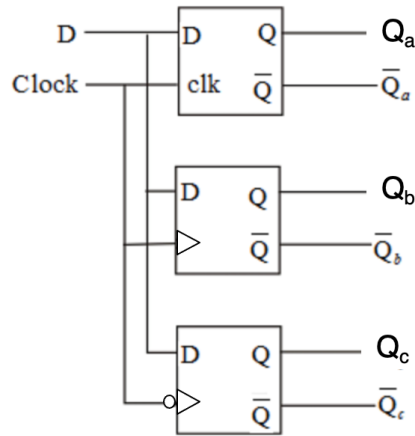


Figure 2


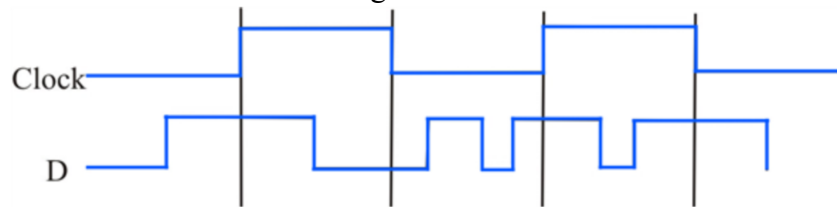


Figure 3

**Answer:**

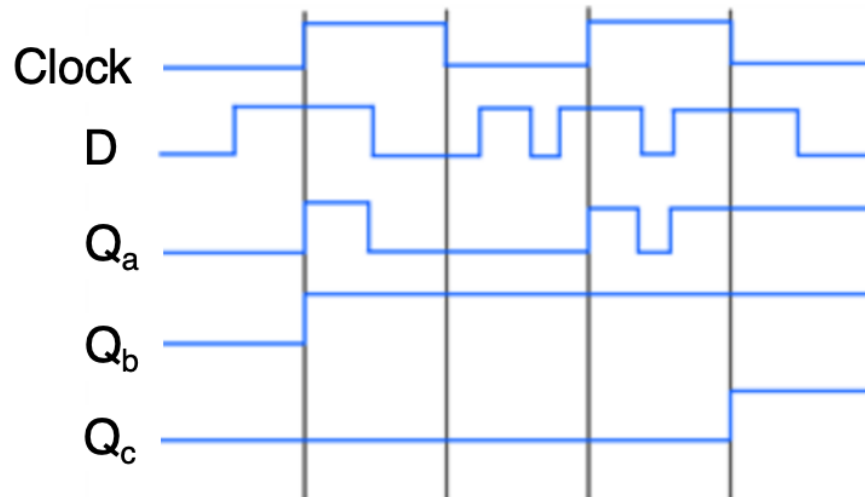

**Problem 4:** Please find the state table for the state diagram in Figure 4. What is the minimum number of states in the state table? Does the state diagram represent a Mealy or Moore FSM?

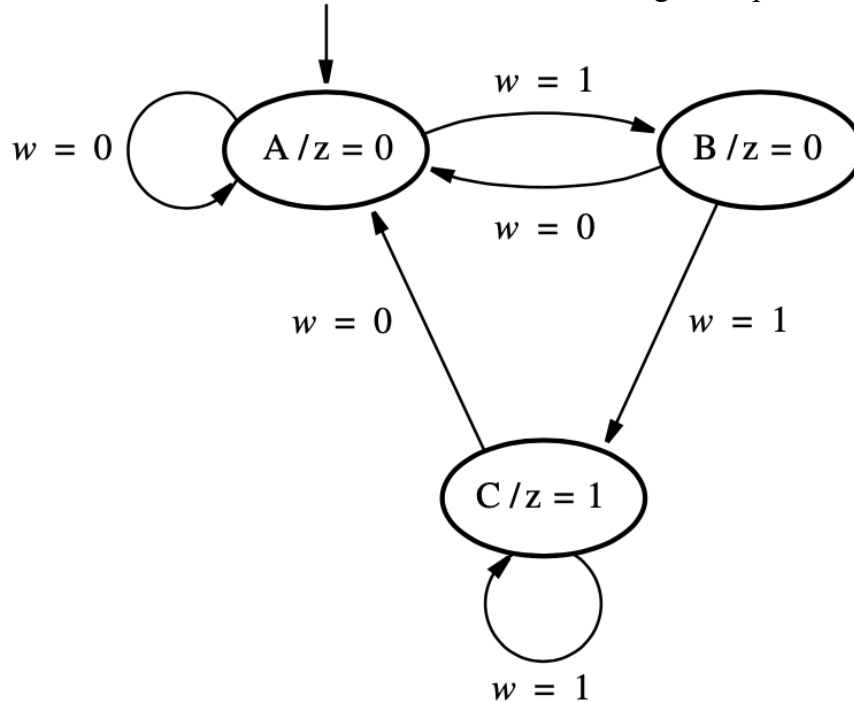



Figure 4

**Answer:**


The state table is as follows. The minimum number of states is 3 as there are no equivalent states. The state diagram represents a Moore machine as the output  $z$  depends only on the current state.

Present state	Next state		Output $z$
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

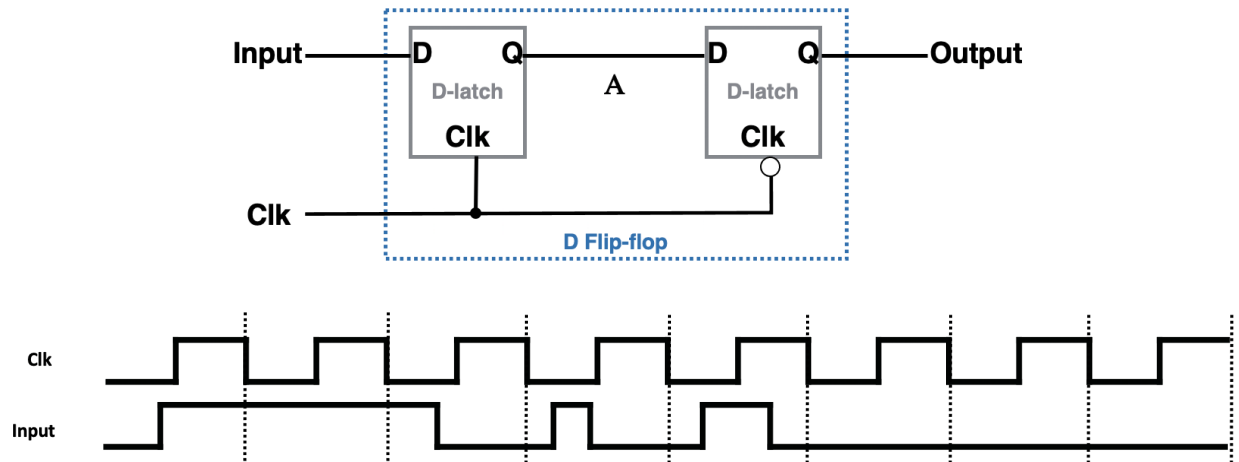
**Problem 5:** Sketch/draw the Output waveform of a D Flip-flop for the input waveforms shown below. Assuming that initially Output=0.



**Answer:**

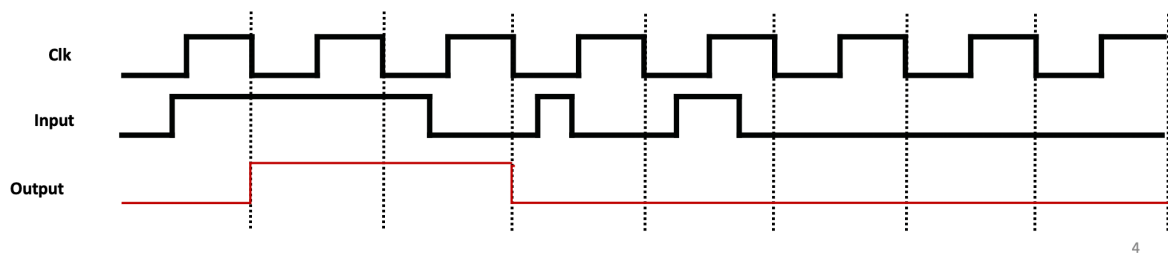

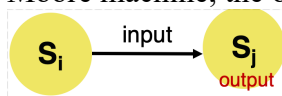**Problem 6:** Draw a state diagram for the Moore state machine described by Table 1. Hint: for Moore machine, the output depends only on the current state and an example of state transition is



where  $S_i$  and  $S_j$  are the starting and ending states of such a transition.

Current State	Next State				Output Z
	Inputs A and B				
	00	01	11	10	
INIT	A0	A0	A1	A1	0
A0	OK0	OK0	A1	A1	0
A1	A0	A0	OK1	OK1	0
OK0	OK0	OK0	OK1	A1	1
OK1	A0	OK0	OK1	OK1	1

Table 1

Method 1: Directly draw each transition where the two numbers on top of each transition represent the values of A and B.

