

Homework 4

● Graded

Student

Adithya Chander

Total Points

5.6 / 6 pts

Question 1

P1

1 / 1 pt

The rubric is hidden for this question.

Question 2

P2

1 / 1 pt

The rubric is hidden for this question.

Question 3

P3

0.8 / 1 pt

The rubric is hidden for this question.

Question 4

P4

0.9 / 1 pt

The rubric is hidden for this question.

Question 5

P5

0.9 / 1 pt

The rubric is hidden for this question.

Question 6

P6

1 / 1 pt

The rubric is hidden for this question.

Questions assigned to the following page: [6](#), [2](#), [3](#), [1](#), [4](#), and [5](#)

HW4-CS120A

1. Simplify SOP and POS expressions for lamp with don't cares

$$F = \sum_{A,B,C} (0,1,3,4,6) + D(2,5)$$

| AB \ C | 0 | 1 |
|--------|---|---|
| 0 | 1 | 1 |
| 1 | 1 | 0 |
| 2 | 1 | 1 |
| 3 | 1 | 0 |
| 4 | 1 | 1 |
| 5 | 1 | 0 |
| 6 | 1 | 1 |
| 7 | 1 | 0 |

$$\bar{A} + AB = \bar{A} + B$$


$$\text{SOP: } A' + AC' = A' + C'$$

3. draw waveforms for Q_a, Q_b, Q_c given the timing


D-latch

| D | Q |
|---|---|
| 0 | 0 |
| 1 | 1 |


diagrams of Clock and D waveforms

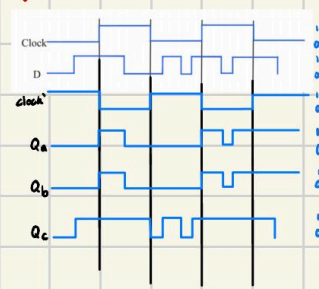

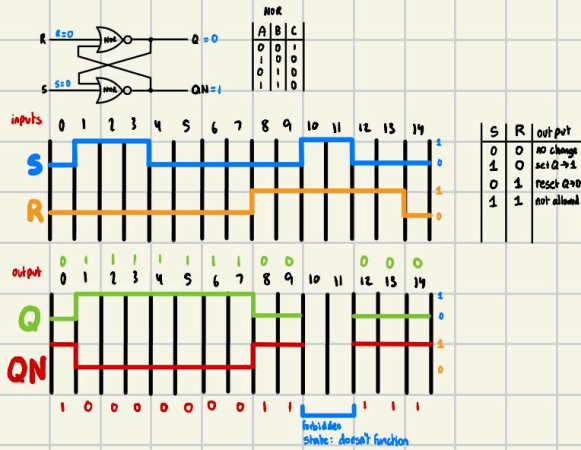
2. Sketch the output waveforms for Q and QN of the SR Latch




5. Sketch the waveform

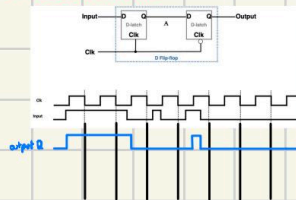

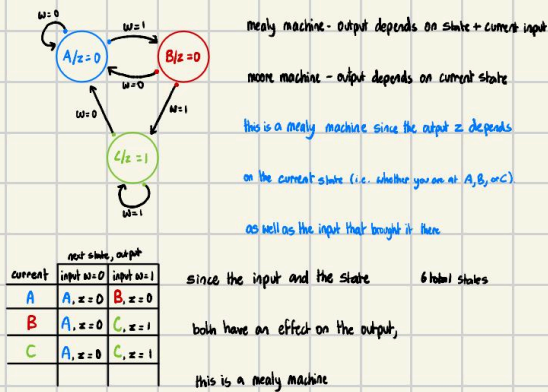4. Find the state table for the state diagram. is it a mealy or moore?



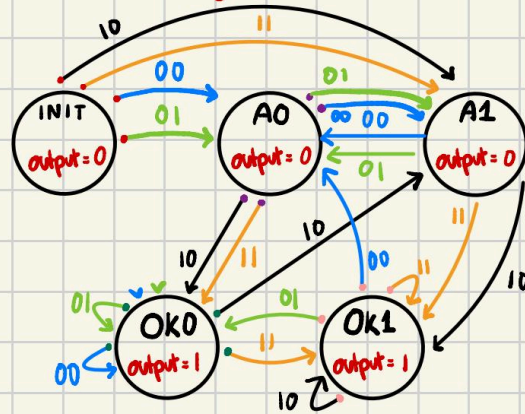6. draw a state diagram for the moore machine



Adithya Chander

Section 001/025

20 November 2024