

EE168 Homework 4

Kaushik Vada

Problem 1

(a) No buffer inserted:

$$T_0 = \min_i (T_i - D_i) = \min\{T_1 - D_{01}, T_2 - D_{02}\}.$$

$$\begin{aligned} D_{01} &= R_1(C_1 + C_2 + C_3 + C_4 + C_5 + C_6 + C_7 + C_8) \\ &\quad + R_2(C_2 + C_3 + C_4 + C_5) + R_3(C_3 + C_4 + C_5) \\ &\quad + R_4(C_4 + C_5) + R_5C_5 \\ &= 10 \times 19 + 60 \times 12 + 60 \times 9 + 60 \times 6 + 60 \times 3 \\ &= 1990 \text{ ps}, \end{aligned}$$

$$\begin{aligned} D_{02} &= R_1(C_1 + C_2 + C_3 + C_4 + C_5 + C_6 + C_7 + C_8) \\ &\quad + R_6(C_6 + C_7 + C_8) + R_7(C_7 + C_8) + R_8C_8 \\ &= 10 \times 19 + 80 \times 6 + 80 \times 4 + 80 \times 2 \\ &= 1150 \text{ ps}, \end{aligned}$$

$$T_1 - D_{01} = 2000 - 1990 = 10 \text{ ps},$$

$$T_2 - D_{02} = 1200 - 1150 = 50 \text{ ps},$$

$$T_0 = \min\{10 \text{ ps}, 50 \text{ ps}\} = 10 \text{ ps}.$$

(b) With the buffer inserted:

$$T_0 = \min\{T_1 - D'_{01}, T_2 - D'_{02}\}.$$

$$\begin{aligned} D'_{01} &= R_1(C_1 + C_6 + C_7 + C_8 + C_{\text{buf}}) + R_2C_{\text{buf}} + D_{\text{buf}} \\ &\quad + R_{\text{buf}}(C_2 + C_3 + C_4 + C_5) + R_3(C_3 + C_4 + C_5) \\ &\quad + R_4(C_4 + C_5) + R_5C_5 \\ &= 10 \times 9 + 60 \times 2 + 5 + 10 \times 12 + 60 \times 9 + 60 \times 6 + 60 \times 3 \\ &= 1415 \text{ ps}, \end{aligned}$$

$$\begin{aligned} D'_{02} &= R_1(C_1 + C_6 + C_7 + C_8 + C_{\text{buf}}) \\ &\quad + R_6(C_6 + C_7 + C_8) + R_7(C_7 + C_8) + R_8C_8 \\ &= 10 \times 9 + 80 \times 6 + 80 \times 4 + 80 \times 2 \\ &= 1050 \text{ ps}, \end{aligned}$$

$$T_1 - D'_{01} = 2000 - 1415 = 585 \text{ ps},$$

$$T_2 - D'_{02} = 1200 - 1050 = 150 \text{ ps},$$

$$T_0 = \min\{585 \text{ ps}, 150 \text{ ps}\} = 150 \text{ ps}.$$


Problem 2

Primary-input settings to detect each marked stuck-at fault (one at a time).

- (a) Two NANDs $\rightarrow$ AND. Faults: n_1 S-A-1 (upper NAND out), n_2 S-A-1 (lower NAND out).
- n_1 S-A-1: $a = b = 1, c = d = 0$.
 - n_2 S-A-1: $c = d = 1, a = b = 0$.
- (b) Two NORs $\rightarrow$ OR (n_3), then AND with inverted leg n_4 . Faults: n_1 S-A-0, n_3 S-A-0, n_4 S-A-1.
- n_1 S-A-0: $a = b = 0, c = d = 1, e = 0$.
 - n_3 S-A-0: set one NOR high (e.g., $a = b = 0$) and the other low, $e = 0$.
 - n_4 S-A-1: $e = 1$, force $n_3 = 1$ (e.g., $a = b = 0$).
- (c) NAND (a, b) $\rightarrow$ OR with c . Faults: n_1 S-A-1, OR-output S-A-0.
- n_1 S-A-1: $a = b = 1, c = 0$.
 - OR S-A-0: drive OR high (e.g., $a = 0$ or $b = 0$, or $c = 1$).

Problem 3

- (a) Given circuit schematic:

 

- (b) Critical path and delay:
The critical path from primary input to output is

$$a \rightarrow \text{xor} \rightarrow \text{not} \rightarrow \text{and} \rightarrow \text{or} \rightarrow y$$

Total delay: 9 unit delays.

Problem 4

(a) Part-logic and whole-logic modules:

Part-logic module

```
module part-logic(x,y,a,b,c);
    input a,b,c;
    output y,x;
    wire t1;
    not n1(t1,b);
    and a1(x,a,t1);
    or o1(y,x,c);
endmodule
```

Whole-logic module

```
module whole-logic(x,y,a,c,b);
    input [2:0] a;
    input [2:0] b;
    input c;
    output [2:0] x;
    output y;
    wire c1,c2;
    part-logic p11(x[0],c1,a[0],b[0],c);
    part-logic p12(x[1],c2,a[1],b[1],c1);
    part-logic p13(x[2],c,a[2],b[2],c2);
endmodule
```

(b) Using continuous assignment statement:

```
module part-logic(x,y,a,b,c);
    input a,b,c;
    output x,y;
    assign x = a & (~b);
    assign y = x | c;
endmodule
```

Problem 5

SECDED (13,8) Hamming: positions 1,2,4,8 are parity; positions 3,5,6,7,9,10,11,12 are data; position 13 is overall parity p_0 .

Encoder

```
// data[7:0] -> code[12:0] (1-based positions noted)
module hamming13_enc(input [7:0] data, output [12:0] code);
    wire p1 = data[0]^data[1]^data[3]^data[4]^data[6]; // pos1
    wire p2 = data[0]^data[2]^data[3]^data[5]^data[6]; // pos2
    wire p4 = data[1]^data[2]^data[3]^data[7]; // pos4
    wire p8 = data[4]^data[5]^data[6]^data[7]; // pos8
    assign code = {
        ^{data,p1,p2,p4,p8}, // pos13 = p0 (overall even parity)
        data[7], data[6], data[5], data[4], // pos12..9
        p8, // pos8
        data[3], data[2], data[1], // pos7..5
        data[0], // pos3
        p4, // pos4
        p2, // pos2
        p1 // pos1 (LSB)
    };
endmodule
```

Decoder with single-error correction + double-error detect

```
module hamming13_dec(
    input  [12:0] code_in,
    output [7:0]  data_out,
    output          err_single, err_double
);
    // unpack per position (1-based for clarity)
    wire p1 = code_in[0], p2 = code_in[1], d0 = code_in[2], p4 = code_in[3];
    wire d1 = code_in[4], d2 = code_in[5], d3 = code_in[6], p8 = code_in[7];
    wire d4 = code_in[8], d5 = code_in[9], d6 = code_in[10], d7 = code_in[11];
    wire p0 = code_in[12];

    wire s1 = p1 ^ d0 ^ d1 ^ d3 ^ d4 ^ d6;
    wire s2 = p2 ^ d0 ^ d2 ^ d3 ^ d5 ^ d6;
    wire s4 = p4 ^ d1 ^ d2 ^ d3 ^ d7;
    wire s8 = p8 ^ d4 ^ d5 ^ d6 ^ d7;
    wire [3:0] syndrome = {s8,s4,s2,s1}; // 1..12
    wire parity_err = ^code_in; // overall parity check (even)

    reg [12:0] corrected;
    always @* begin
        corrected = code_in;
        if (syndrome != 0 && parity_err) // single-bit error in 1..12
            corrected[syndrome-1] = ~code_in[syndrome-1];
        else if (syndrome == 0 && parity_err) // error only in p0
            corrected[12] = ~code_in[12];
    end

    assign err_single = (syndrome != 0 && parity_err) || (syndrome == 0 && parity_err);
    assign err_double = (syndrome != 0 && !parity_err); // detected, not corrected

    assign data_out = {corrected[11],corrected[10],corrected[9],corrected[8],
                      corrected[6],corrected[5],corrected[4],corrected[2]};
endmodule
```